



| | | | |
|---------------------------------|----------------------------------|---------------------|--------------------|
| Course Name: | Digital Design Laboratory | Semester: | III |
| Date of Performance: | 29 / 07 / 2024 | Batch No: | D3 |
| Faculty Name: | Mansi Kambli | Roll No: | 16010123294 |
| Faculty Sign & Date: | | Grade/Marks: | ___/25 |

Experiment No: 2

Title: Binary Adders and Subtractors

Aim and Objective of the Experiment:

To implement half and full adder–subtractor using gates and IC 7483

COs to be achieved:

CO2: Use different minimization technique and solve combinational circuits.

Tools used:

Trainer kits

Theory:

Adder: The addition of two binary digits is the most basic operation performed by the digital computer. There are two types of adder:

- Half adder
- Full adder

Half Adder: Half adder is a combinational logic circuit with two inputs and two outputs. It is the basic building block for the addition of two single-bit numbers.

Full adder: A half adder has a provision not to add a carry coming from the lower order bits when multi-bit addition is performed. for this purpose, a third input terminal is added and this circuit is to add A, B, and C where A and B are the nth order bits of the number A and B respectively and C is the carry generated from the addition of (n-1) order bits. This circuit is referred to as full adder.

Subtractor: Subtraction of two binary digits is one of the most basic operations performed by digital computer .there are two types of subtractors:

- Half subtractor

- Full subtractor

Half subtractor: Logic circuit for the subtraction of B from A where A,B are 1 bit numbers is referred to as half subtract or .the subtract or process has two input and difference and borrow are the two outputs.

Full subtractor: As in the case of the addition using logic gates, a full subtractor is made by combining two half-sub tractors and an additional OR-gate. A full subtractor has the borrow in capability (denoted as BOR_{IN}) and so allows cascading which results in the possibility of multi-bit subtraction.

IC 7483

For subtraction of one binary number from another, we do so by adding 2's complement of the former to the latter number using a full adder circuit.

IC 7483 is a 16 pin, 4-bit full adder. This IC has a provision to add the carry output to transfer and end around carry output using Co and C4 respectively.

2's complement: 2's complement of any binary no. can be obtained by adding 1 in 1's complement of that no.


e.g. 2's complement of $+(10)_{10} = 1010$ is

| | |
|---------------------|-------|
| 1C of | 01 |
| 1010 | 01 |
| | + 1 |
| | <hr/> |
| | 01 |
| -(10) ₁₀ | 10 |

In 2's complement subtraction using IC 7483, we are representing negative number in 2's complement form and then adding it with 1st number.

Implementation Details:

Half Adder Block Diagram & circuit

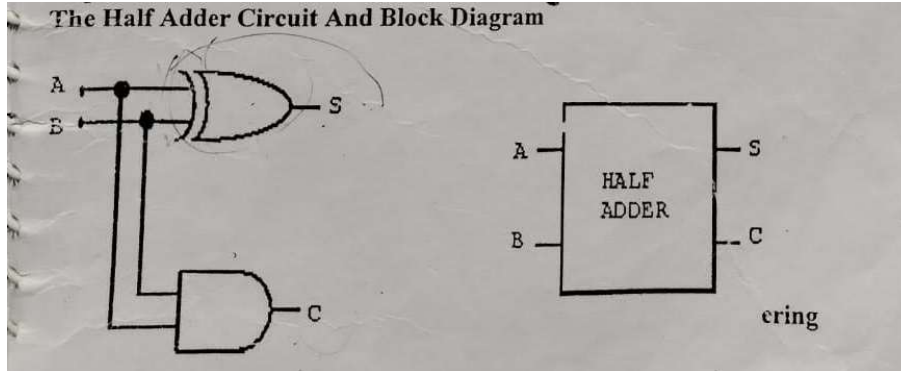


Truth Table for Half Adder

| Inputs | | Outputs | |
|--------|---|---------|---|
| A | B | A | B |
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

From the truth table (with steps):

| A | B | Sum (S) | Carry (C) | Steps for Calculation |
|---|---|---------|-----------|----------------------------------|
| 0 | 0 | 0 | 0 | $0 + 0 = 0$, Sum = 0, Carry = 0 |
| 0 | 1 | 1 | 0 | $0 + 1 = 1$, Sum = 1, Carry = 0 |
| 1 | 0 | 1 | 0 | $1 + 0 = 1$, Sum = 1, Carry = 0 |
| 1 | 1 | 0 | 1 | $1 + 1 = 2$, Sum = 0, Carry = 1 |

Full Adder Block Diagram & Circuit

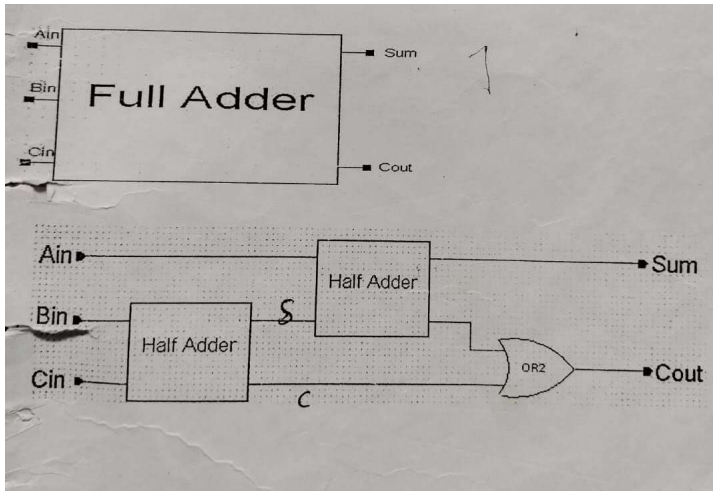

Truth Table for Full Adder


| A | B | C _{in} | S | C _{out} |
|---|---|-----------------|---|------------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

From the truth table (with steps):

| A | B | C _{in} | Sum (S) | Carry-out (C _{out}) | Steps for Calculation |
|---|---|-----------------|---------|-------------------------------|---------------------------------------|
| 0 | 0 | 0 | 0 | 0 | 0 + 0 + 0 = 0, Sum = 0, Carry-out = 0 |
| 0 | 0 | 1 | 1 | 0 | 0 + 0 + 1 = 1, Sum = 1, Carry-out = 0 |
| 0 | 1 | 0 | 1 | 0 | 0 + 1 + 0 = 1, Sum = 1, Carry-out = 0 |
| 0 | 1 | 1 | 0 | 1 | 0 + 1 + 1 = 2, Sum = 0, Carry-out = 1 |
| 1 | 0 | 0 | 1 | 0 | 1 + 0 + 0 = 1, Sum = 1, Carry-out = 0 |
| 1 | 0 | 1 | 0 | 1 | 1 + 0 + 1 = 2, Sum = 0, Carry-out = 1 |
| 1 | 1 | 0 | 0 | 1 | 1 + 1 + 0 = 2, Sum = 0, Carry-out = 1 |
| 1 | 1 | 1 | 1 | 1 | 1 + 1 + 1 = 3, Sum = 1, Carry-out = 1 |

When the sum of the input is 2 or more then carry out is set to 1.

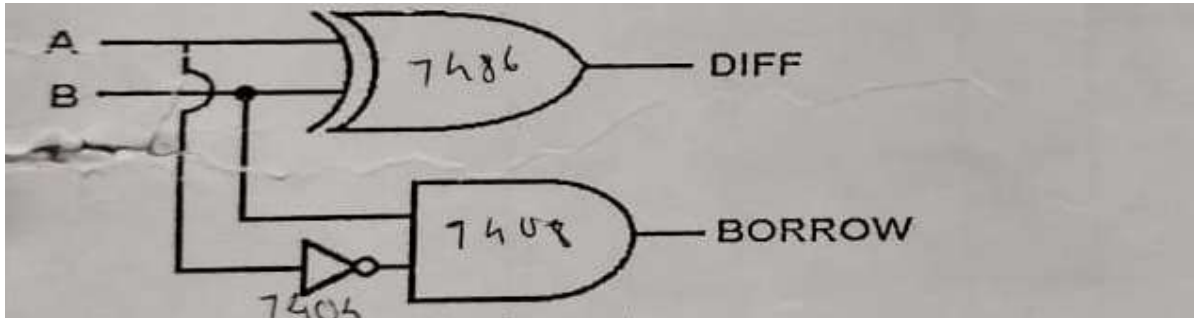Half Subtractor Block Diagram & Half Subtractor Circuit




Truth Table for Half Subtractor

| A | B | DIFFERENCE (D) | BORROW(B ₀) |
|---|---|----------------|-------------------------|
| 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 |

From the truth table (with steps) :

| A | B | Difference (D) | Borrow (B _{out}) | Steps for Calculation |
|---|---|----------------|----------------------------|---|
| 0 | 0 | 0 | 0 | 0 - 0 = 0, Difference = 0, Borrow = 0 |
| 0 | 1 | 1 | 1 | 0 - 1 = -1 (borrow 1), Difference = 1, Borrow = 1 |
| 1 | 0 | 1 | 0 | 1 - 0 = 1, Difference = 1, Borrow = 0 |
| 1 | 1 | 0 | 0 | 1 - 1 = 0, Difference = 0, Borrow = 0 |

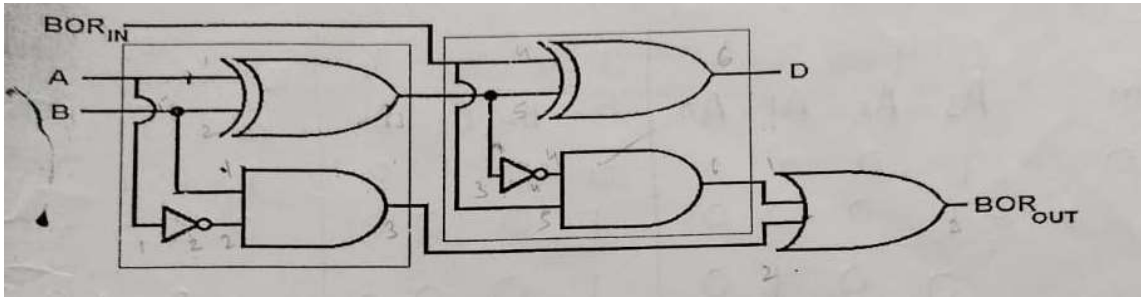Full Subtractor Block Diagram & Full Subtractor Circuit



Truth Table for Full subtractor

| A | B | B _{IN} | D | BOR _{OUT} |
|---|---|-----------------|---|--------------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

From the truth table (with steps):

| A | B | B_{in} | Difference (D) | Borrow (B_{out}) | Steps for Calculation |
|---|---|----------|----------------|----------------------|---|
| 0 | 0 | 0 | 0 | 0 | $0 - 0 - 0 = 0$, Difference = 0, Borrow = 0 |
| 0 | 0 | 1 | 1 | 1 | $0 - 0 - 1 = -1$ (borrow 1), Difference = 1, Borrow = 1 |
| 0 | 1 | 0 | 1 | 1 | $0 - 1 - 0 = -1$ (borrow 1), Difference = 1, Borrow = 1 |
| 0 | 1 | 1 | 0 | 1 | $0 - 1 - 1 = -2$ (borrow 1), Difference = 0, Borrow = 1 |
| 1 | 0 | 0 | 1 | 0 | $1 - 0 - 0 = 1$, Difference = 1, Borrow = 0 |
| 1 | 0 | 1 | 0 | 0 | $1 - 0 - 1 = 0$, Difference = 0, Borrow = 0 |
| 1 | 1 | 0 | 0 | 0 | $1 - 1 - 0 = 0$, Difference = 0, Borrow = 0 |
| 1 | 1 | 1 | 1 | 1 | $1 - 1 - 1 = -1$ (borrow 1), Difference = 1, Borrow = 1 |

Example:

1) $7_{10} - 2_{10} = 5_{10}$

7 0111

2 0010

1'C of 2 1101

+ 1


2'C of 2 1110

1110


0111 + 1110 1

0101


Pin Diagram IC7483

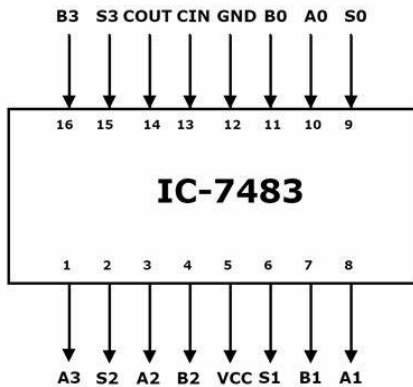

Adder

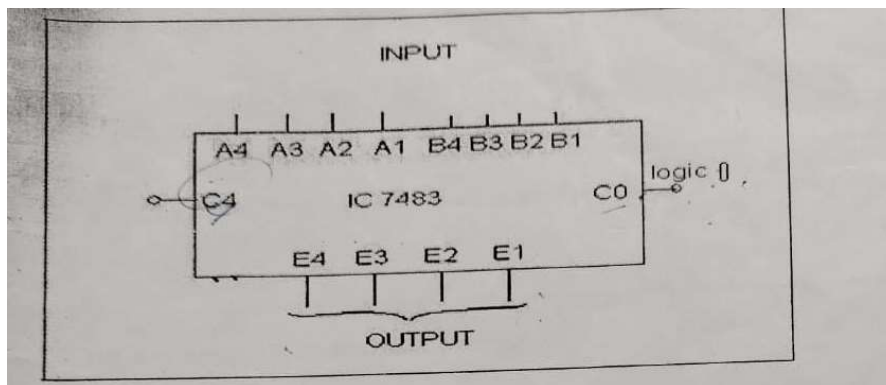

Subtractor

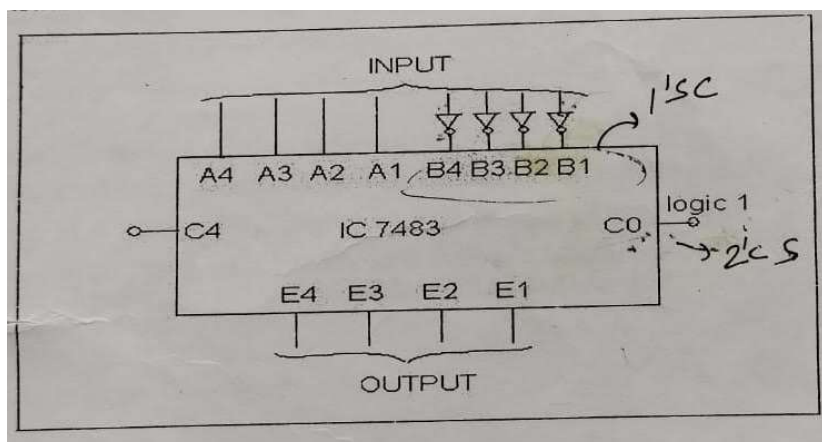


Implementation Details

Procedure:

- 1) Locate the IC 7483 and 4-not gates block on trainer kit.
- 2) Connect 1st input no. to A4-A1 input slot and 2nd (negative) no. to B4-B1 through 4-not gates (1C of 2nd no.)
- 3) Connect high input to Co so that it will get added with 1C of 2nd no. to get 2C.
- 4) Connect 4-bit output to the output indicators.
- 5) Switch ON the power supply and monitor the output for various input combinations.

Post Lab Subjective/Objective type Questions:

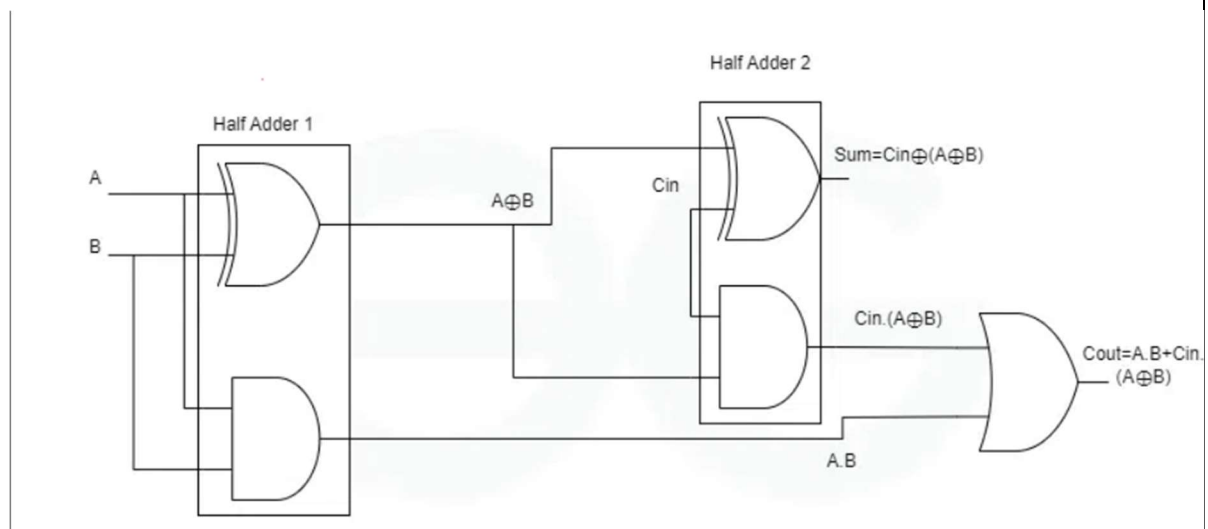1. Design a full adder using two half adders.



2. Perform the following Binary subtraction with the help of appropriate ICs:

- 6-4
- 5-8
- 7-9

a) 6-4
 $6 = (0110)_2$, $4 = (0100)_2$
 2^{nd} complement of 4 = ~~101~~ $\rightarrow 1^{\text{st}}$ complement = $(1011)_2$
 2^{nd} complement = $(1100)_2$
 on adding

$$\begin{array}{r} 0110 \\ + 1100 \\ \hline 10010 \end{array}$$
 $\rightarrow 2$

b) 5-8
 $5 = (0101)_2$, $8 = (1000)_2$
 2^{nd} complement of 8 $\rightarrow 1^{\text{st}}$ complement = 0111
 2^{nd} complement = 1000
 adding

$$\begin{array}{r} 0101 \\ + 1000 \\ \hline 1101 \end{array}$$
 $\rightarrow 2^{\text{nd}}$ complement of -3

c) 7-9
 $7 = 0111$, $9 \rightarrow 1001$
 2^{nd} complement of 9 = 0111
 on adding

$$\begin{array}{r} 111 \\ 0111 \\ + 0111 \\ \hline 1100 \end{array}$$
 $\rightarrow 2^{\text{nd}}$ complement of 2

Conclusion:

Learned about binary adder and subtractor and also verified using the 7483 ic and learned its connections and application on the DDL kit.

Signature of faculty in-charge with Date: