
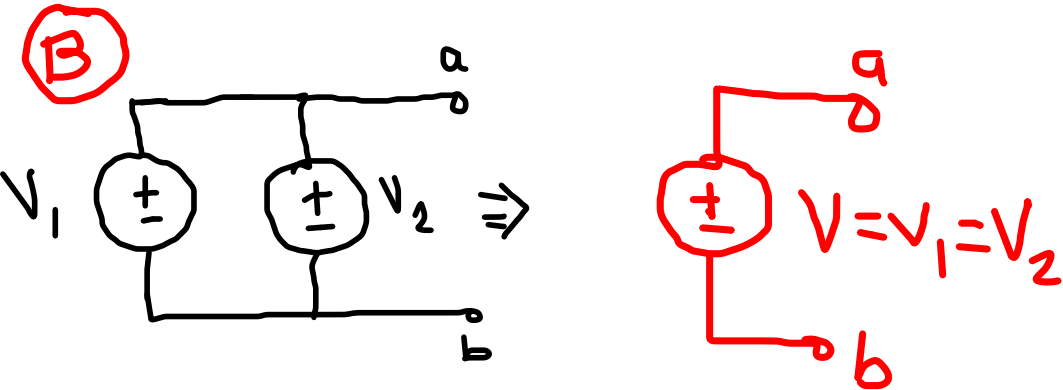




# Interconnection of Voltage and Current sources

## ① Voltage Sources

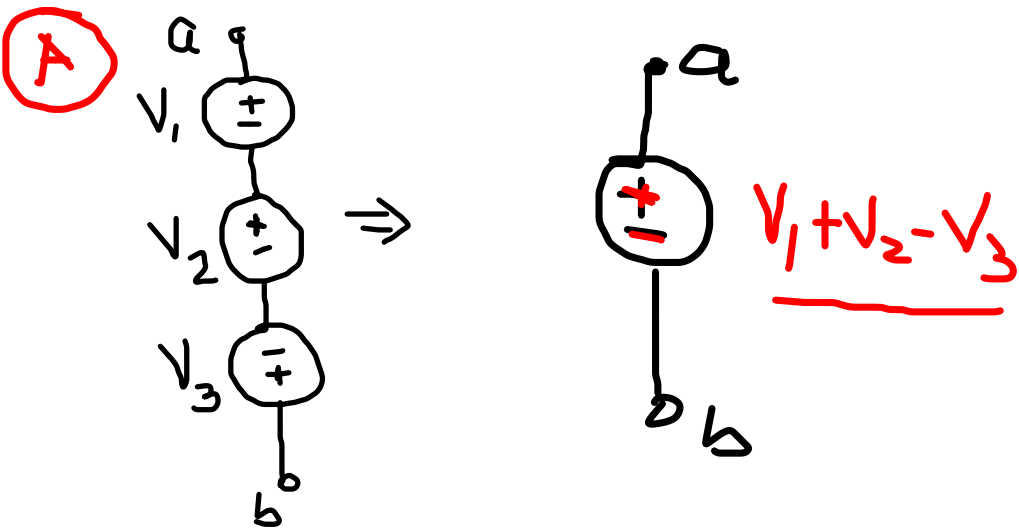


if  $V_1 \neq V_2$  parallel connection not allowed

## ② Current Sources

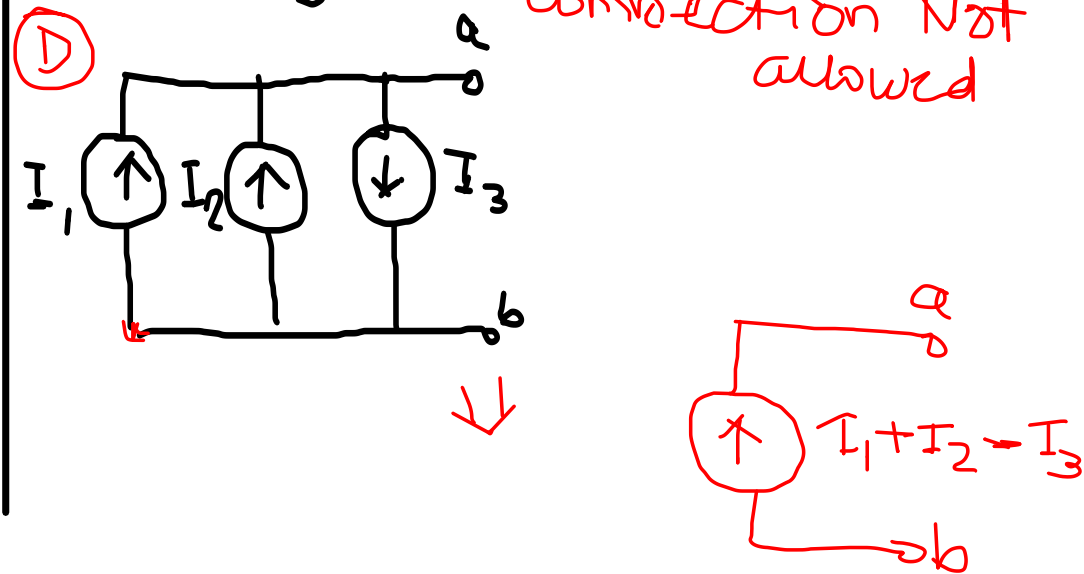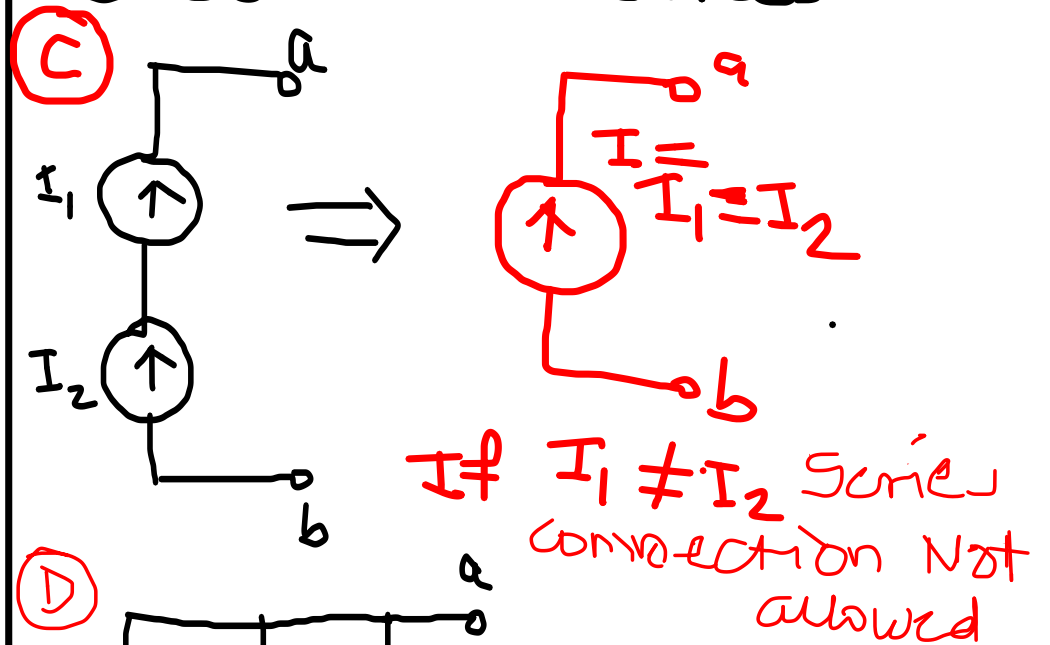

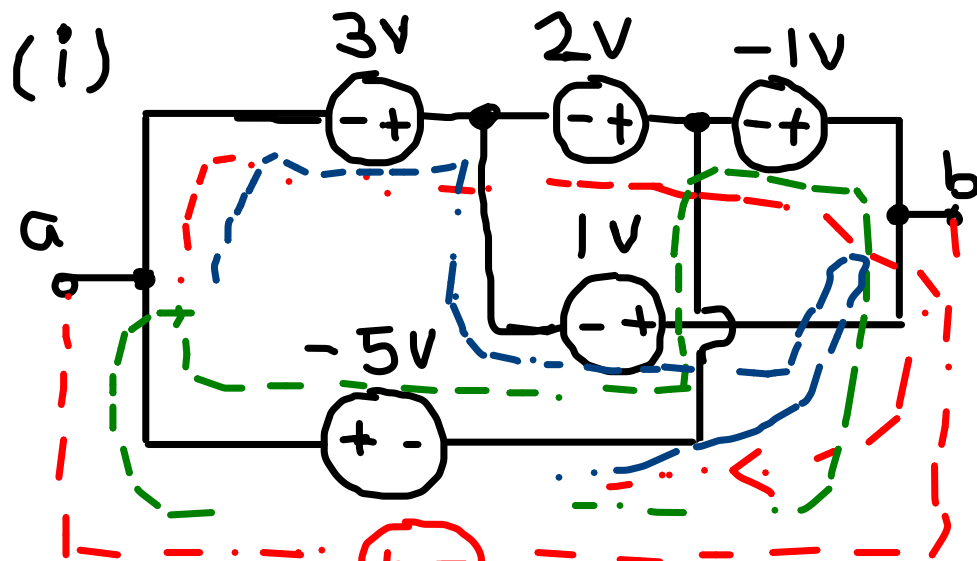Example-1: Replace the following network with (i)  $V_{ab}$  (ii)  $I_{ab}$



$V_{ab}$   
Voltmeter

$$V_{ab} + 3 + 1 = 0 \quad \cdot \quad V_{ab} = -4V$$




$$V_{ab} + 3 + 2 + (-1) = 0$$

$$\underline{V_{ab} = -4V}$$


$$V_{ab} - (-5) + (-1) = 0$$

$$V_{ab} = -4V$$


(ii)

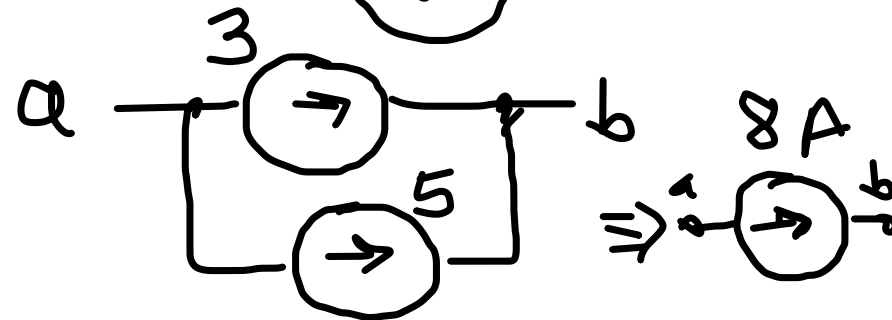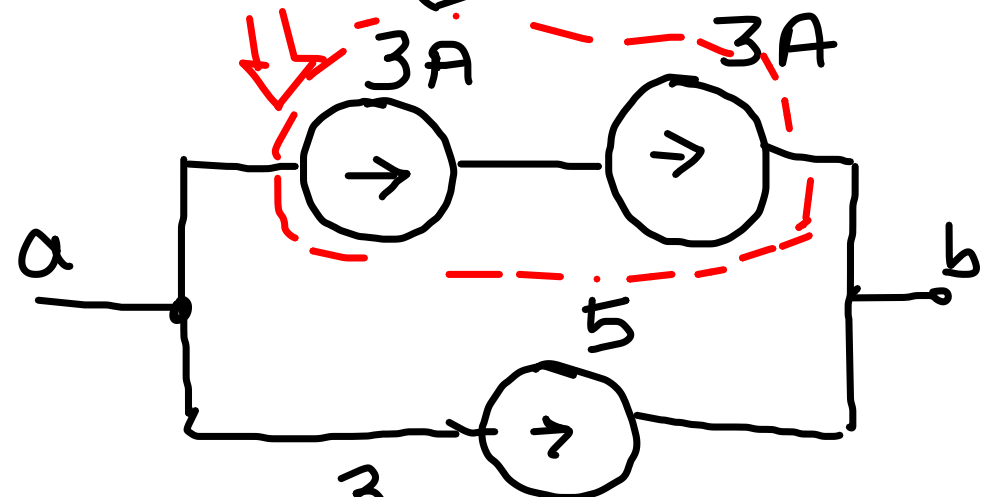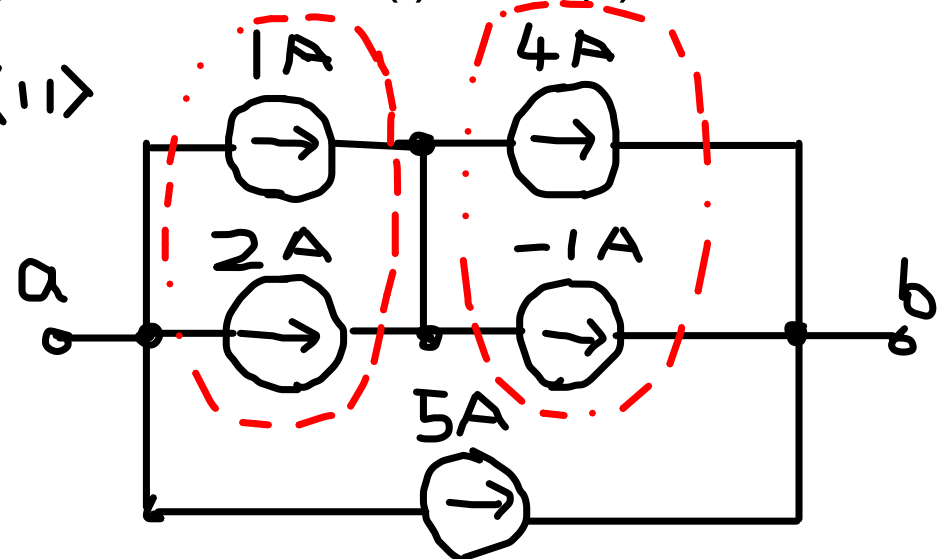
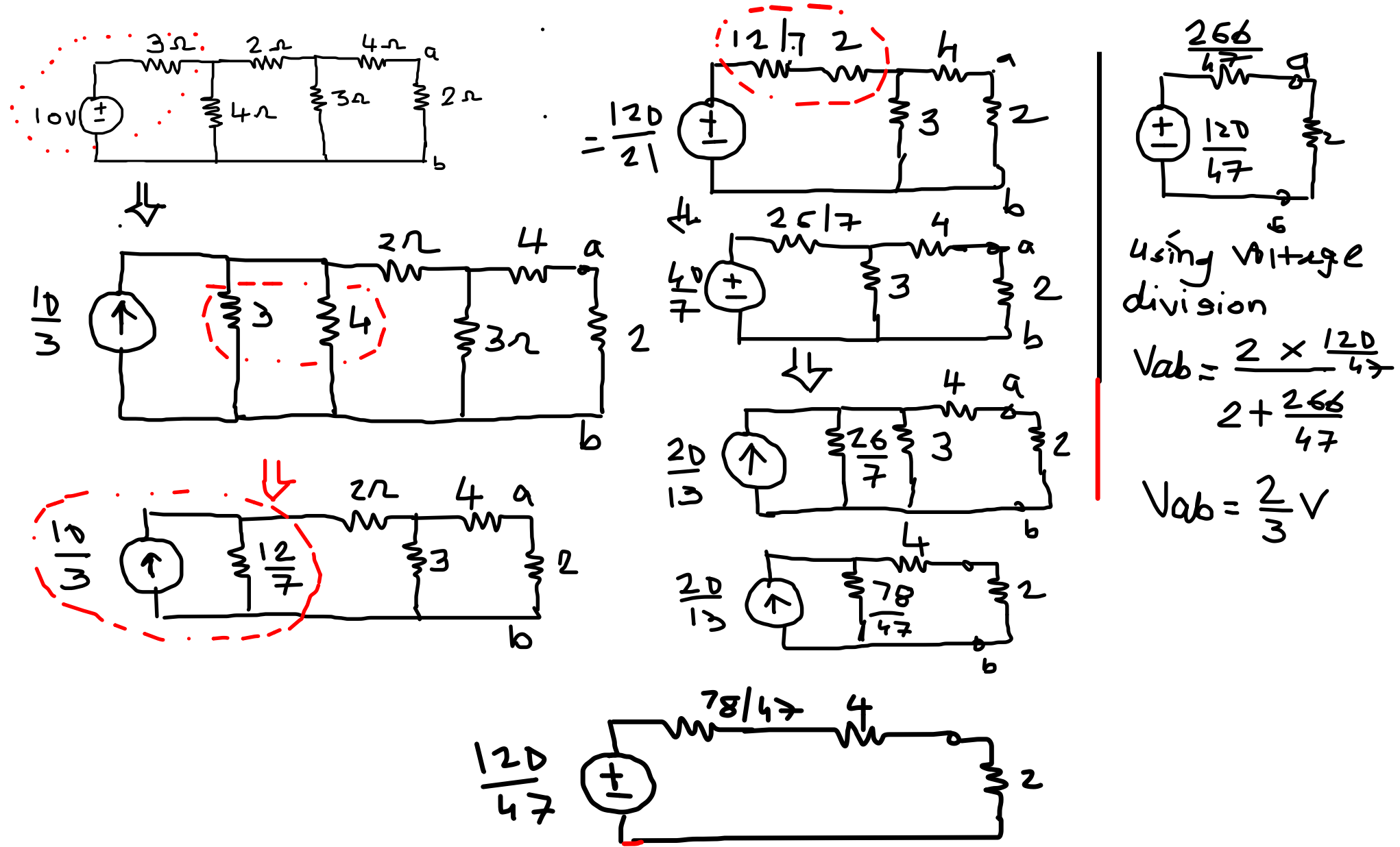
# Example-2: Find Voltage $V_{ab}$ using Source Transformation



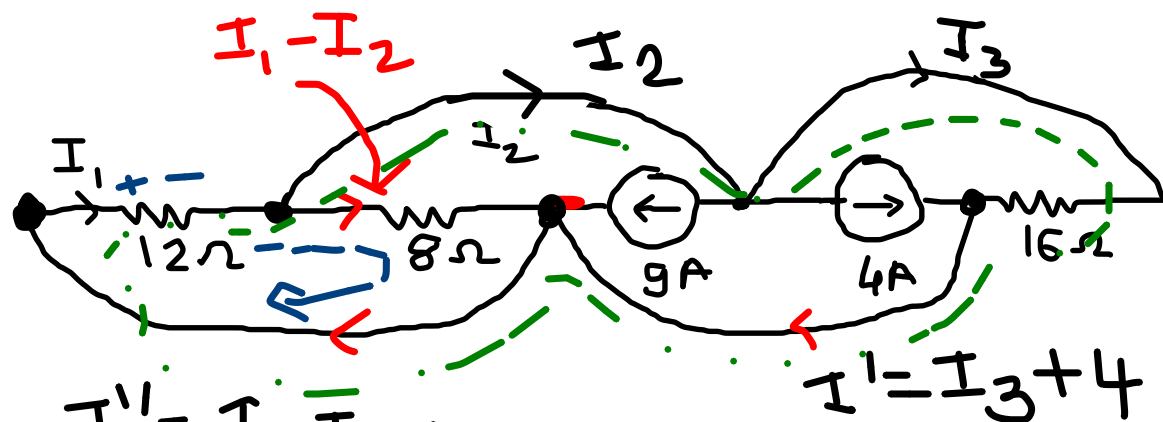Example-3: Determine currents  $I_1$ ,  $I_2$  and  $I_3$



$$I' = I_1 - I_2 + 9 + I_3 + 4$$

$$I'' = I_1$$

$$\cancel{I_1} - I_2 + 9 + I_3 + 4 = \cancel{I_1}$$

$$I_2 - I_3 = 13 \quad \text{--- (1)}$$

Solving eqn (1) (2) & (3)

$$\begin{cases} I_1 = 4 \text{ A} \\ I_2 = 10 \text{ A} \\ I_3 = -3 \text{ A} \end{cases}$$

$$\Delta = \quad \Delta_2 =$$

$$\Delta_1 = \quad \Delta_3 =$$

using KVL  $I_1 = \frac{\Delta_1}{\Delta}$

$$-12I_1 - 8(I_1 - I_2) = 0$$


$$-20I_1 + 8I_2 = 0 \quad \text{--- (II)}$$

using KVL




$$-12I_1 - 16I_3 = 0 \quad \text{--- (III)}$$

$$\begin{bmatrix} 0 & 1 & -1 \\ -20 & 8 & 0 \\ -12 & 0 & -16 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 13 \\ 0 \\ 0 \end{bmatrix}$$

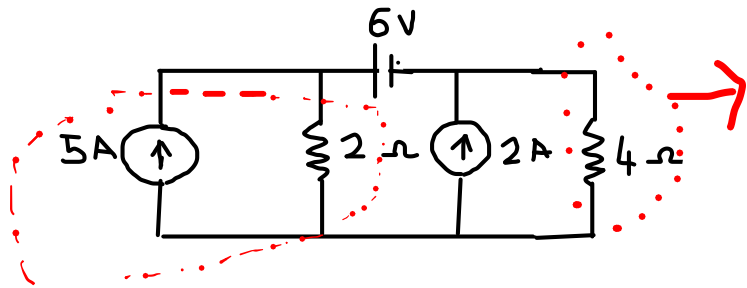Example-4: Find voltage across 4ohm resistor using Source Transformation.



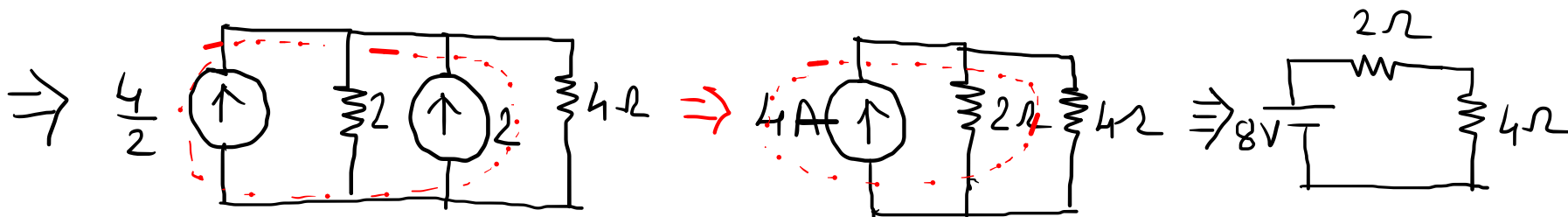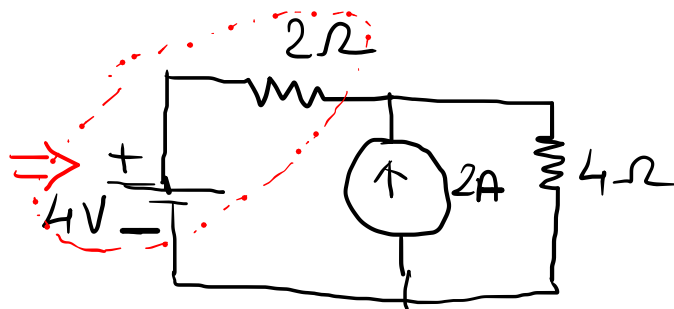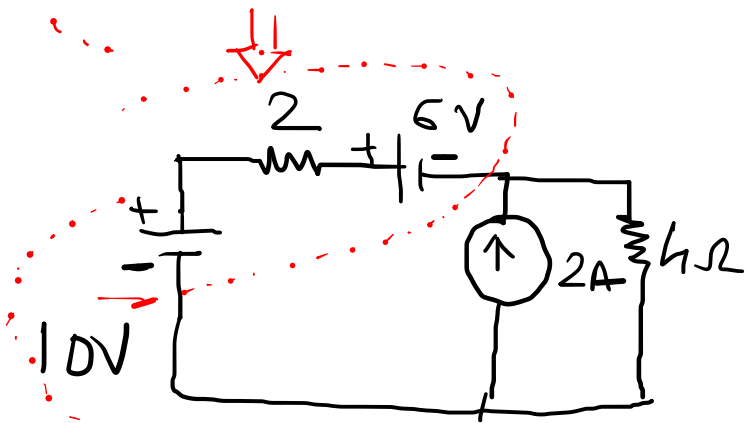Do not take the resistor into source transformation across which Voltage/current is to be found.







using Voltage division Rule


$$\rightarrow V_{4\Omega} = \frac{4 \times 8}{4 + 2} = \frac{32}{6} = 5.33 \text{ V}$$

Example-5: Replace the following network with single current source and a resistor

13.33 6

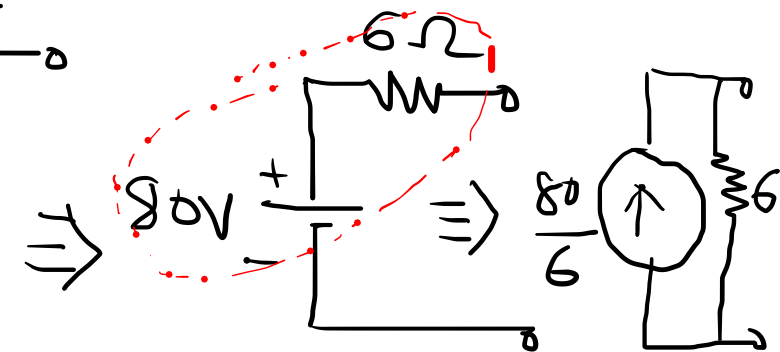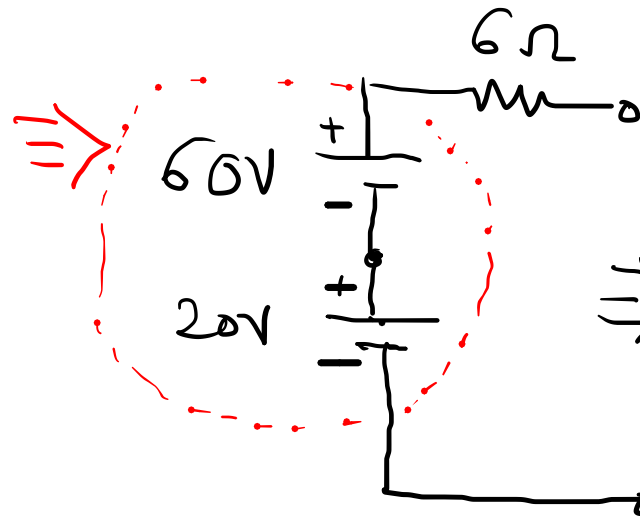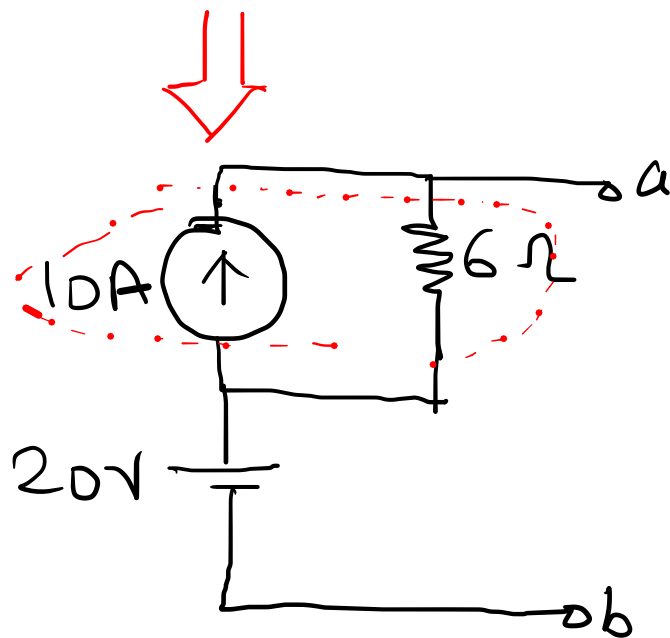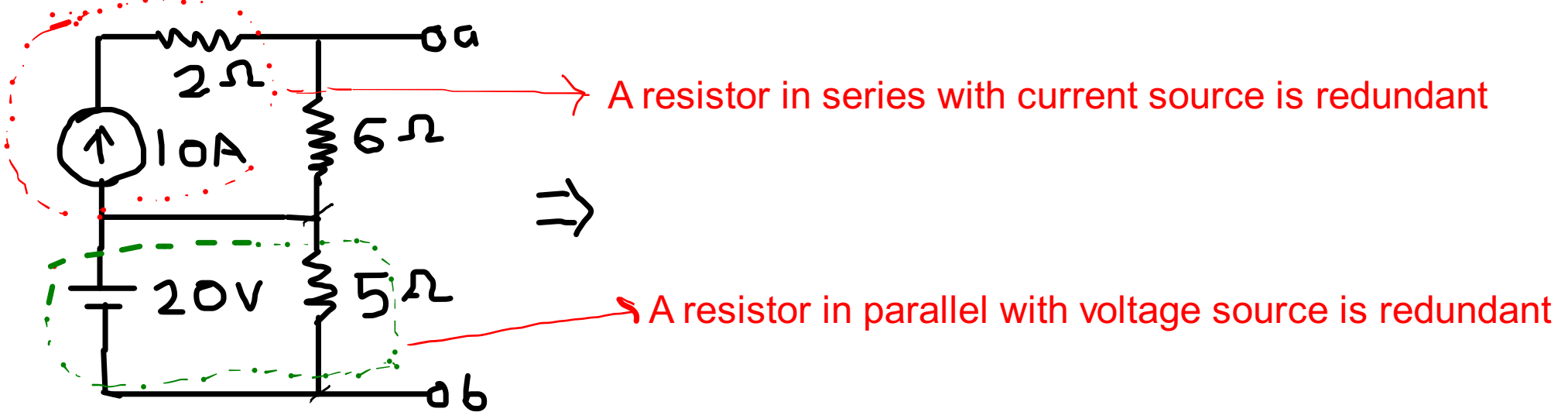

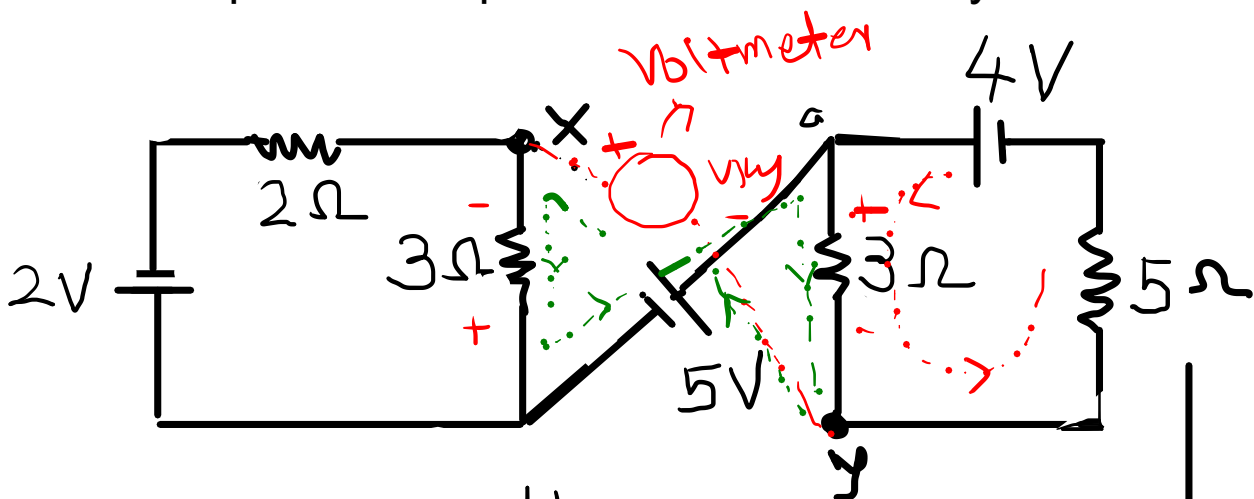Example-6: Find potential difference  $V_{xy}$ .




KVL to closed loop.

$$V_{xy} + (V'_{3\Omega}) + (5) + V''_{3\Omega} = 0$$

$$V_{xy} + \frac{6}{5} + 5 - \frac{12}{8} = 0$$


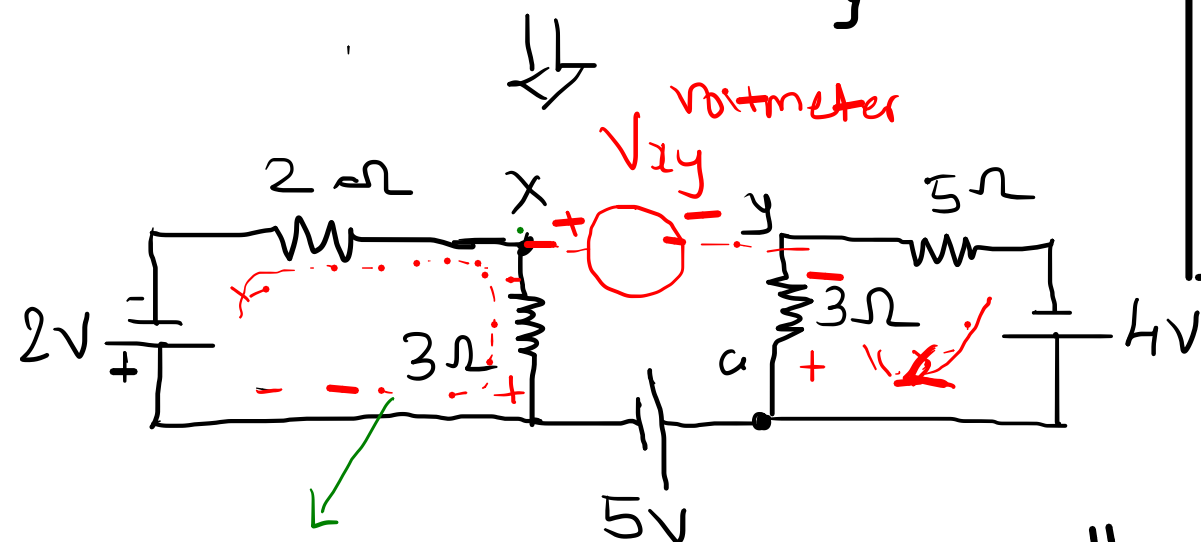
$$V_{xy} = \underline{\underline{-4.7V}}$$



$$V'_{3\Omega} = \frac{3 \times 2}{2 + 3} = \frac{6}{5} V$$

$$V''_{3\Omega} = \frac{3 \times 4}{3 + 5} = \frac{12}{8} V$$

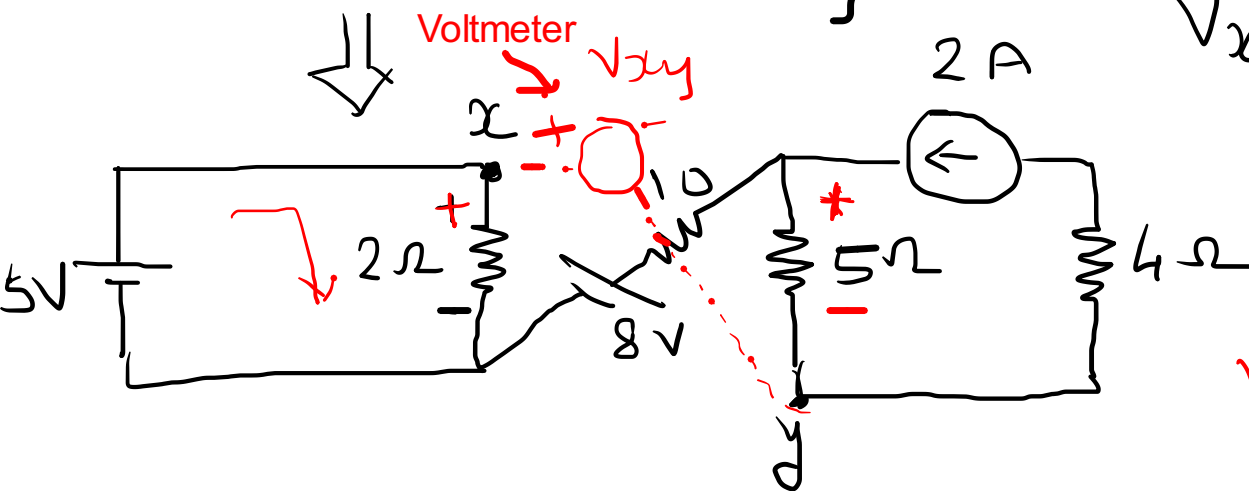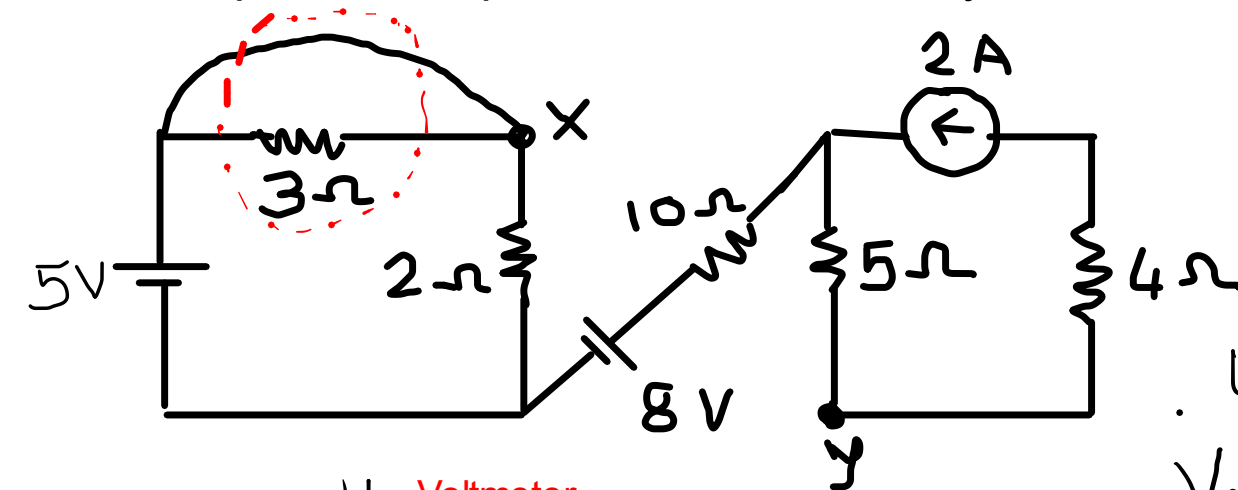Example-6: Find potential difference  $V_{xy}$ .



Potential drop across 10 ohm resistor is zero because no current flows through it. No close path for current through 10ohm

Using KVL from  $V_{xy}$

$$V_{xy} + (V_{2\Omega}) + 8 + (V_{10\Omega}) + V_{5\Omega} = 0$$


$$V_{xy} - 5 + 8 + 0 - (5 \times 2) = 0$$

$$V_{xy} - 5 + 8 - 10 = 0$$


$$\underline{V_{xy} = 7V}$$



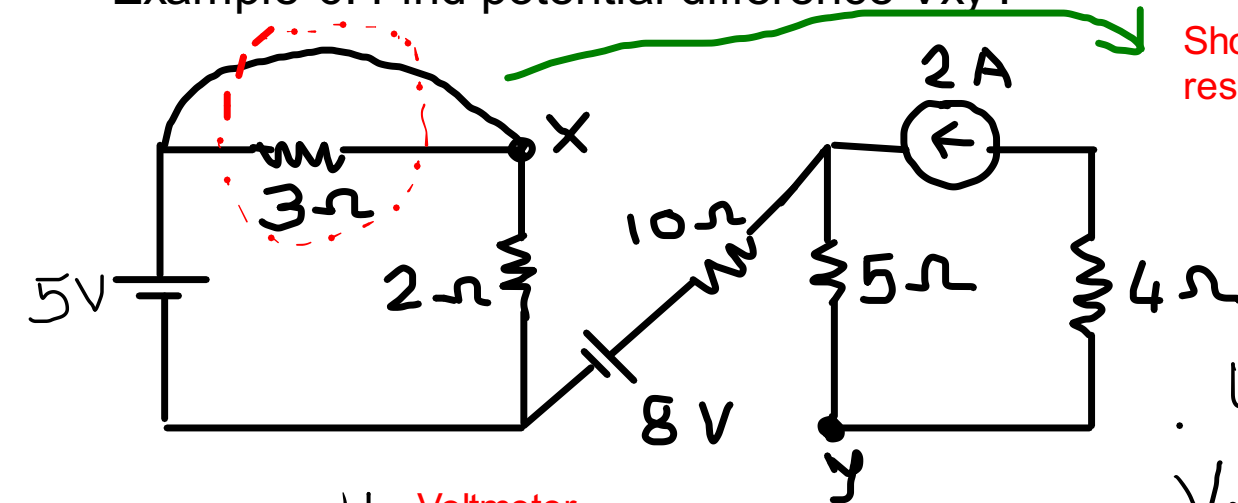Example-6: Find potential difference  $V_{xy}$ .



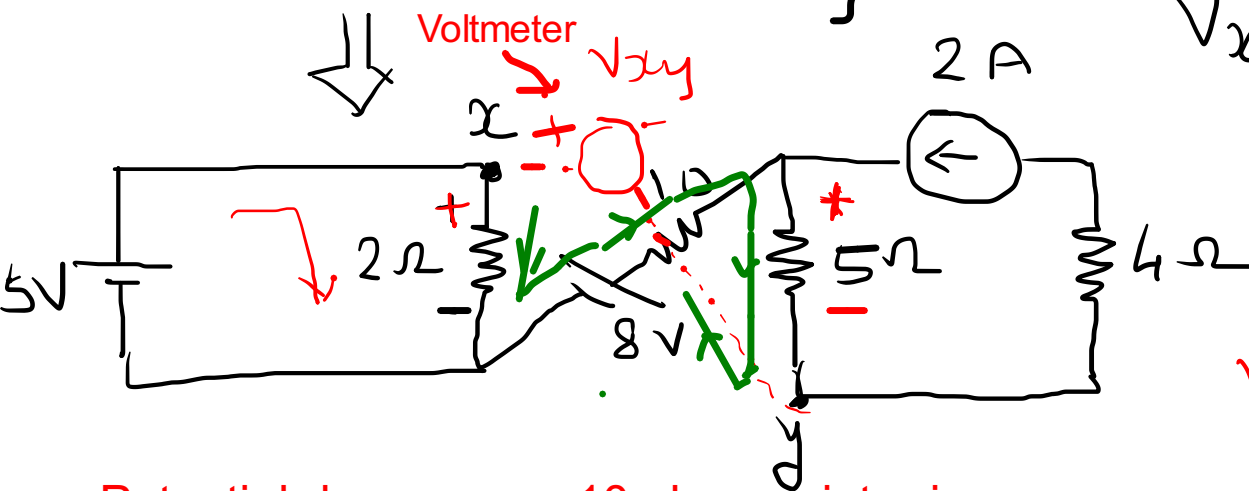Short circuit across 3 ohm resistor. so equivalent resistance is zero.  $R_{eq} = (3 \times 0) / (3 + 0)$ .



Using KVL from  $V_{xy}$

$$V_{xy} + (V_{2\Omega}) + 8 + (V_{10\Omega}) + (V_{5\Omega}) = 0$$

Potential drop across 10 ohm resistor is zero because no current flows through it. No close path for current to flow through 10 ohm.

$$V_{xy} - 5 + 8 + 0 - (5 \times 2) = 0$$

$$V_{xy} - 5 + 8 - 10 = 0$$

$$\underline{V_{xy} = 7V}$$