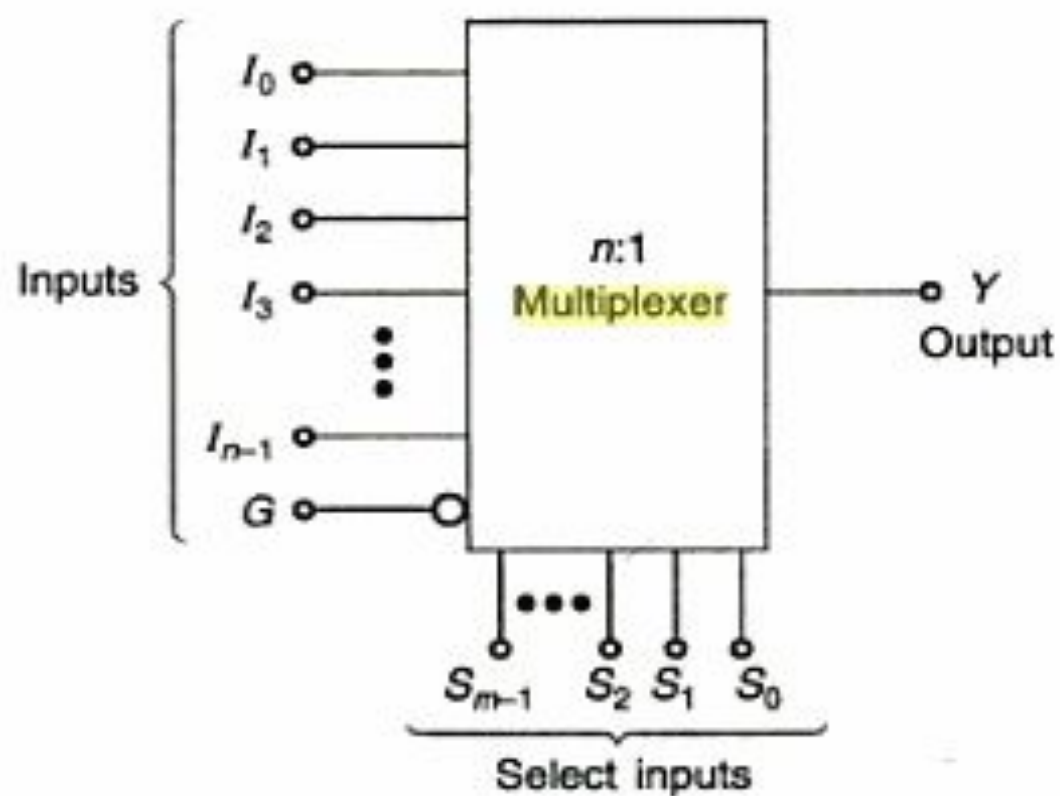



# Multiplexer

- A **multiplexer** (or mux) is a device that selects one of several analog or digital input signals and forwards the selected input into a single line.



**Fig. 6.1**

Block diagram of a digital **multiplexer**.

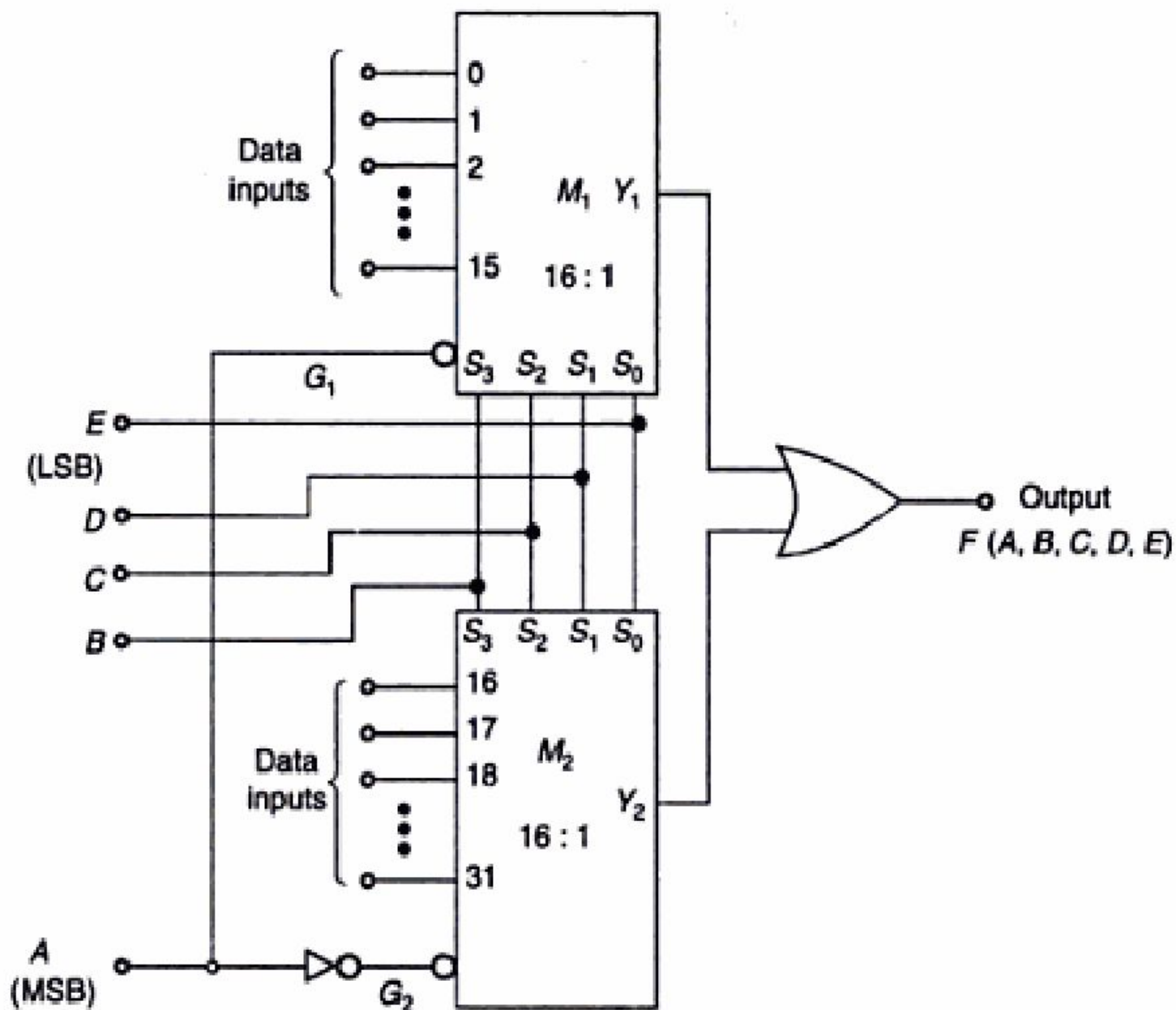

**Fig. 6.5**


32:1 multiplexer using two 16:1 multiplexers and one OR gate.

# Applications of Mux

- Boolean function implementation circuit
- Pulse train generator.
- Encoders

# Demultiplexer

- Demultiplex (DEMUX) is the reverse of the multiplex (MUX) process – combining multiple unrelated analog or digital signal streams into one signal over a single shared medium, such as a single conductor of copper wire or fiber optic cable. Thus, demultiplex is reconverting a signal containing multiple analog or digital signal streams back into the original separate and unrelated signals.

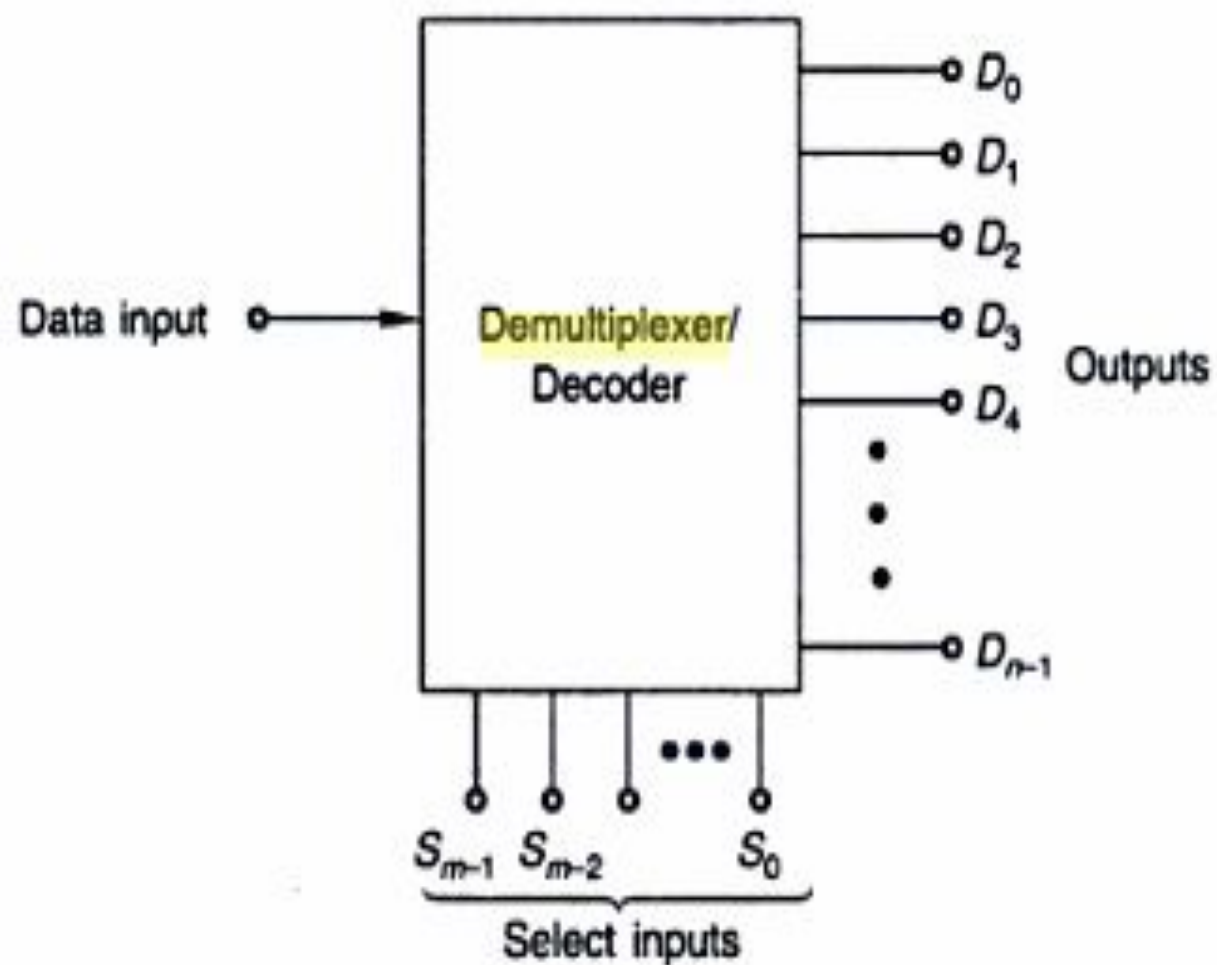

**Fig. 6.7**

Block diagram of a demultiplexer.

# 1:8 demux using two 1:4 demux

