

<b>Course Name:</b>	<b>Digital Design Laboratory</b>	<b>Semester:</b>	<b>III</b>
<b>Date of Performance:</b>	<b>07/10 /2024</b>	<b>Batch No:</b>	<b>D3</b>
<b>Faculty Name:</b>	<b>Mansi Kambli</b>	<b>Roll No:</b>	<b>16010123294</b>
<b>Faculty Sign &amp; Date:</b>		<b>Grade/Marks:</b>	<b>___/25</b>

## **Experiment No: 7** **Title: Asynchronous Counter**

### **Aim and Objective of the Experiment:**

To design and implement 3 bit Asynchronous up counter using JK Flip Flop

### **COs to be achieved:**


**CO3:** Design synchronous and asynchronous sequential circuits.

### **Tools used:**


Trainer kits

### **Theory:**

 **Circuit diagram of 3 bit Asynchronous Up counter using JK FF (IC 7476)**



### Pin diagram of JK FF (IC 7476)

 

**IC 7476 Pinout Diagram**

### Implementation Details

#### Procedure


- 1) Locate IC 7476 JK FF on Digital trainer kit
- 2) Apply various inputs to appropriate pins as per the circuit diagram of the 3 bit Asynchronous up counter with reference to the pin configuration of the IC.
- 3) Make sure of Reset and Clear Pins connections with reference to data sheet information.
- 4) Connect a pulsar switch to the clock input.
- 5) Verify the working and prepare a truth table.

### Post Lab Subjective/Objective type Questions:

 1. How JK FF need to be configured to use for counter operation?  
 To configure a JK flip-flop (FF) for counter operation:  
 J and K inputs: Set both  $J = 1$  and  $K = 1$  for toggling.  
 Clock: Connect the flip-flops in a series, with the clock pulse triggering each one.  
 Output: Use the Q output of one flip-flop as the clock input for the next to create a ripple counter.  
 This setup makes the JK flip-flop toggle states with each clock pulse, counting binary numbers.

- What changes are required to use the same counter as 3 bit asynchronous down counter?  
 To modify a 3-bit asynchronous counter to function as a down counter:  
**Invert Q outputs:** Instead of feeding the Q output to the clock of the next flip-flop, use the **Q'** (NOT Q) output for the clock input of the next flip-flop.  
**Initial state:** Set the counter to the maximum value (e.g., 111 for a 3-bit counter) to count down.  
 This makes the counter decrement with each clock pulse.

- Draw the timing diagram of 3 bit Asynchronous up counter.



- What is mod n concept used in counters?  
 The mod-n concept in counters refers to a counter that cycles through **n distinct states** (0 to n-1) before resetting to zero. For example, a mod-4 counter counts 0, 1, 2, 3, and then resets to 0 on the next clock pulse.
- For Mod-5 counter how many JK FFs are required?  
 For a Mod-5 counter, **3 JK flip-flops** are required. This is because  $2^3 = 8$  is the smallest number of states greater than or equal to 5, and the extra states (5 to 7) can be reset using additional logic.

### Conclusion:

We learned about the working of 3 bit Asynchronous up counter using JK Flip Flop and implemented it using IC on the kit.

**Signature of faculty in-charge with Date:**