



Course Name:	Digital Design Laboratory	Semester:	III
Date of Performance:	26 / 08 / 2024	Batch No:	D3
Faculty Name:	Mansi Kambli	Roll No:	16010123294
Faculty Sign & Date:		Grade/Marks:	___/25

Experiment No: 4

Title: 4-bit magnitude comparator

Aim and Objective of the Experiment:

To design and implement 1-bit comparator using logic gates and verify 4-bit magnitude comparator using IC 7485

COs to be achieved:


CO2: Use different minimization techniques and solve combinational circuits.

Tools used:

Trainer kits

Theory:

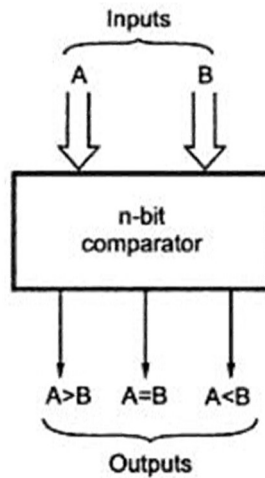Comparator: The comparison of two numbers is an operator that determines one number is greater than, less than (or) equal to the other number. A magnitude comparator is a combinational circuit that compares two numbers A and B and determines their relative magnitude. The outcome of the comparator is specified by three binary variables that indicate whether $A > B$, $A = B$ (or) $A < B$.



1-bit Comparator Implementation Details: Truth Table

A	B	A>B	A<B	A=B
0	0	0	0	1
0	1	0	1	0
1	0	1	0	0
1	1	0	0	1


From the Truth Table:

$$(A < B) = A \cdot \bar{B}$$

$$(A = B) = A \cdot B + \bar{A} \cdot \bar{B} \Rightarrow (A \oplus B)$$


$$(A > B) = \bar{A} \cdot B$$

Logic Diagram of 1-bit Comparator

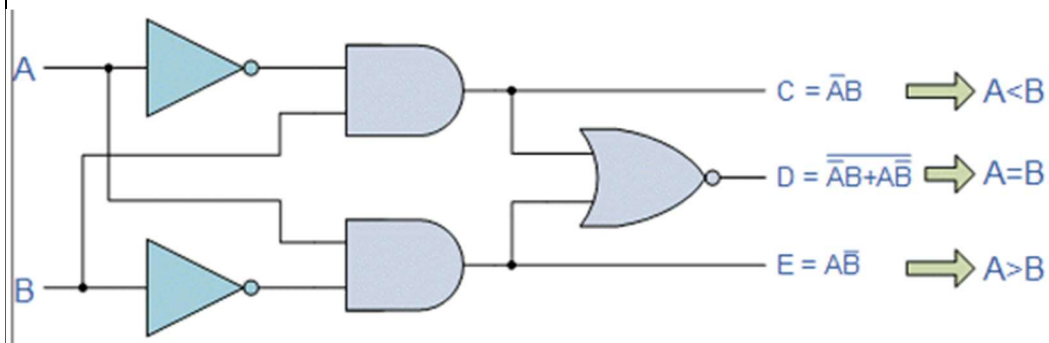


Four Bit Magnitude Comparator Implementation Details:

Pin Diagram of IC 7485

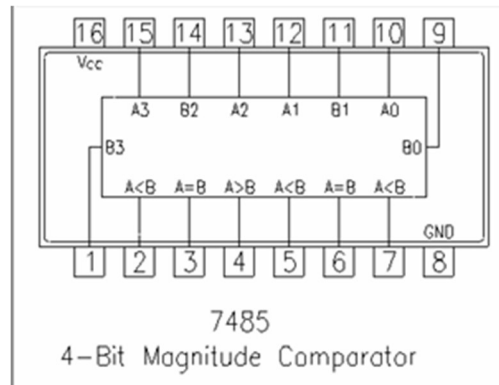

Logic Diagram of IC 7485

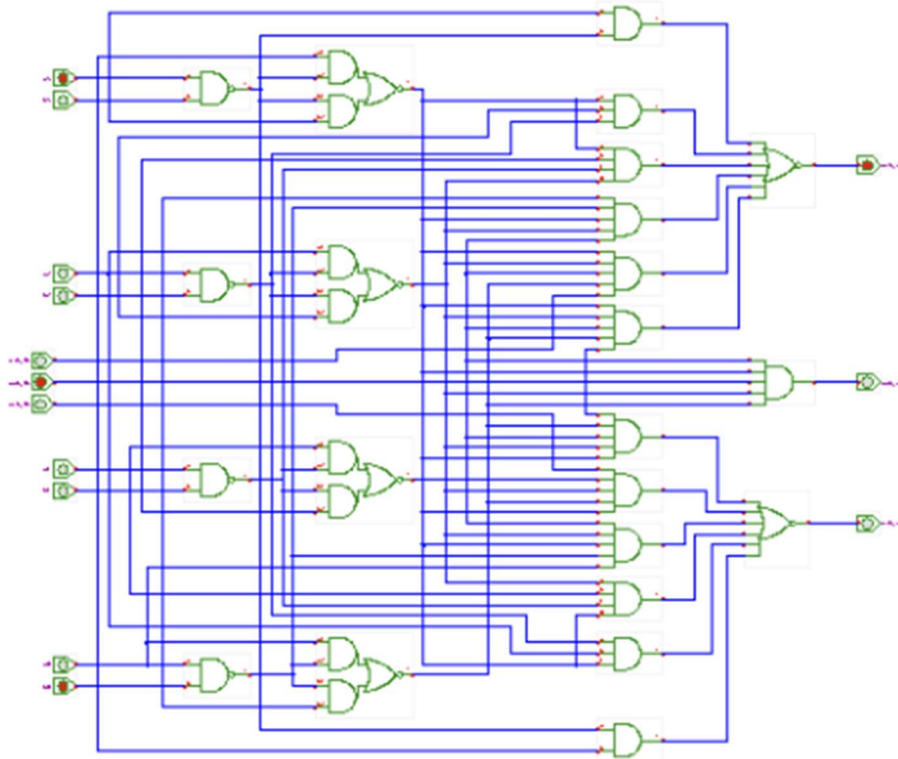


Comparing Table


Comparing inputs								Cascading inputs			Outputs		
A_3	B_3	A_2	B_2	A_1	B_1	A_0	B_0	$A > B$	$A < B$	$A = B$	$A > B$	$A < B$	$A = B$
$A_3 > B_3$		x		x		x		x	x	x	1	0	0
$A_3 < B_3$		x		x		x		x	x	x	0	1	0
$A_3 = B_3$	$A_2 > B_2$			x		x		x	x	x	1	0	0
$A_3 = B_3$	$A_2 < B_2$			x		x		x	x	x	0	1	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 > B_1$				x		x	x	x	1	0	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 < B_1$				x		x	x	x	0	1	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 > B_0$					x	x	x	1	0	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 < B_0$					x	x	x	0	1	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$					1	0	0	1	0	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$					0	1	0	0	1	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$					0	0	1	0	0	1
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$					x	x	1	0	0	1
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$					1	1	0	0	0	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$					0	0	0	1	1	0

Implementation Details

Procedure:

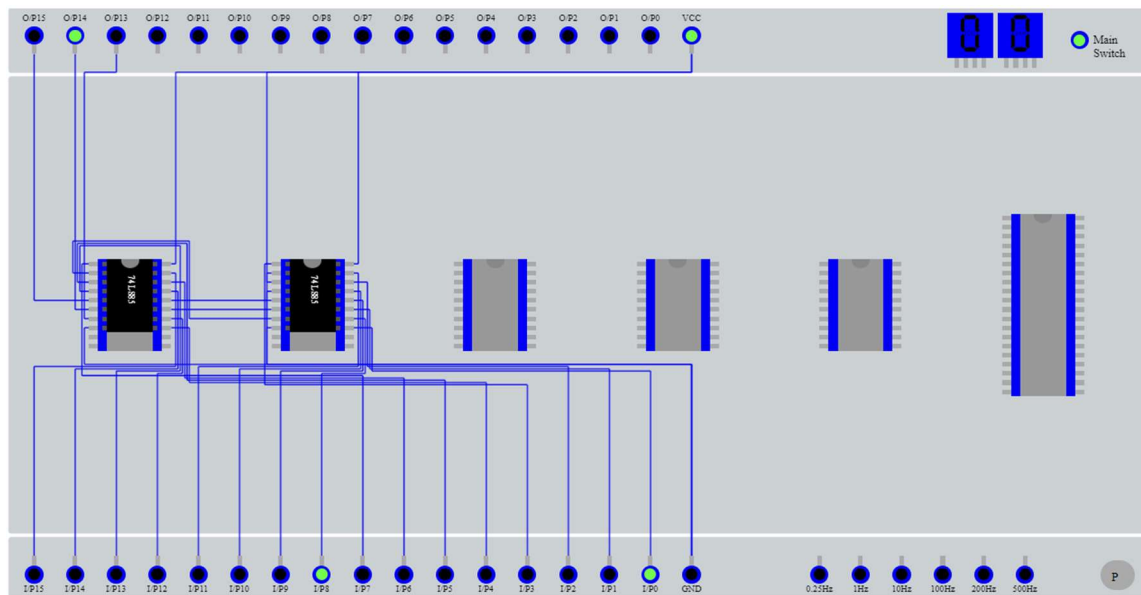- 1) Locate the IC 7485 on the trainer kit.
- 2) Connect 1st input no. to A3-A0 input slot and 2nd to B3-B0.
- 3) Connect the output $Y_{A>B}$, $Y_{A<B}$ and $Y_{A=B}$ to the output indicators.
- 4) Switch ON the power supply and monitor the output for various input combinations.



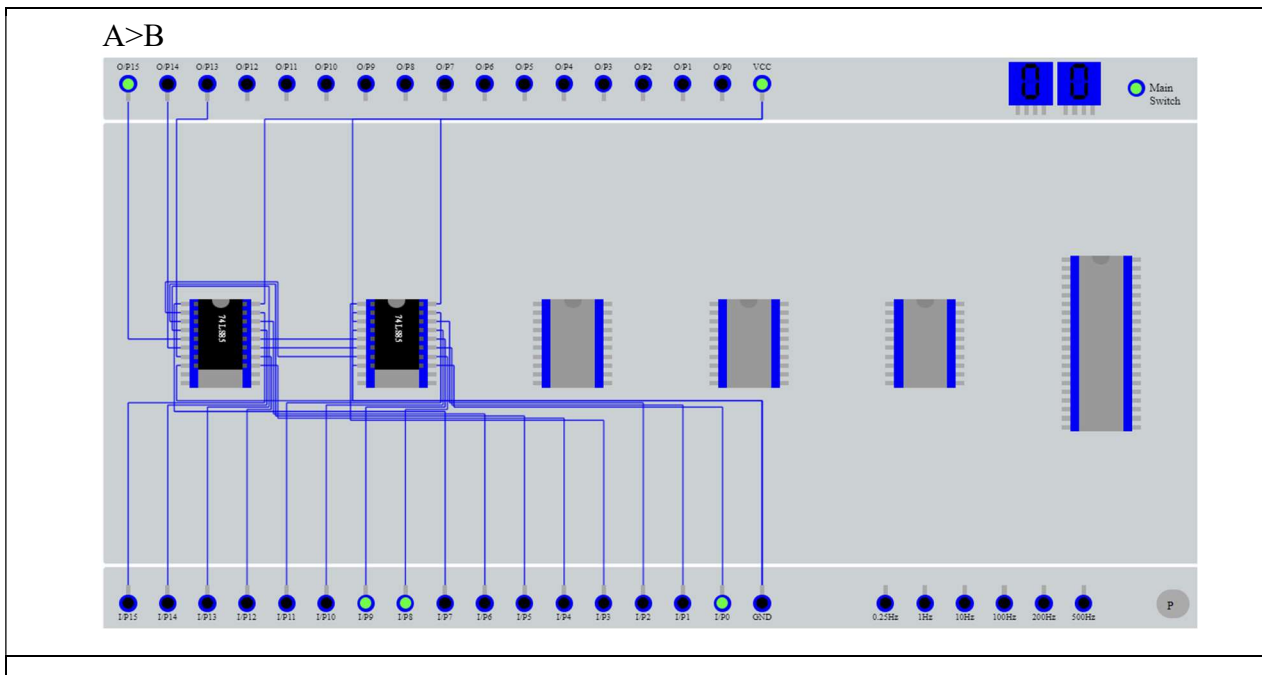

Conclusion:

Learned about the logic of bit comparator and also made circuit on circuit verse also used virtual lab for the same.

Signature of faculty in-charge with Date: