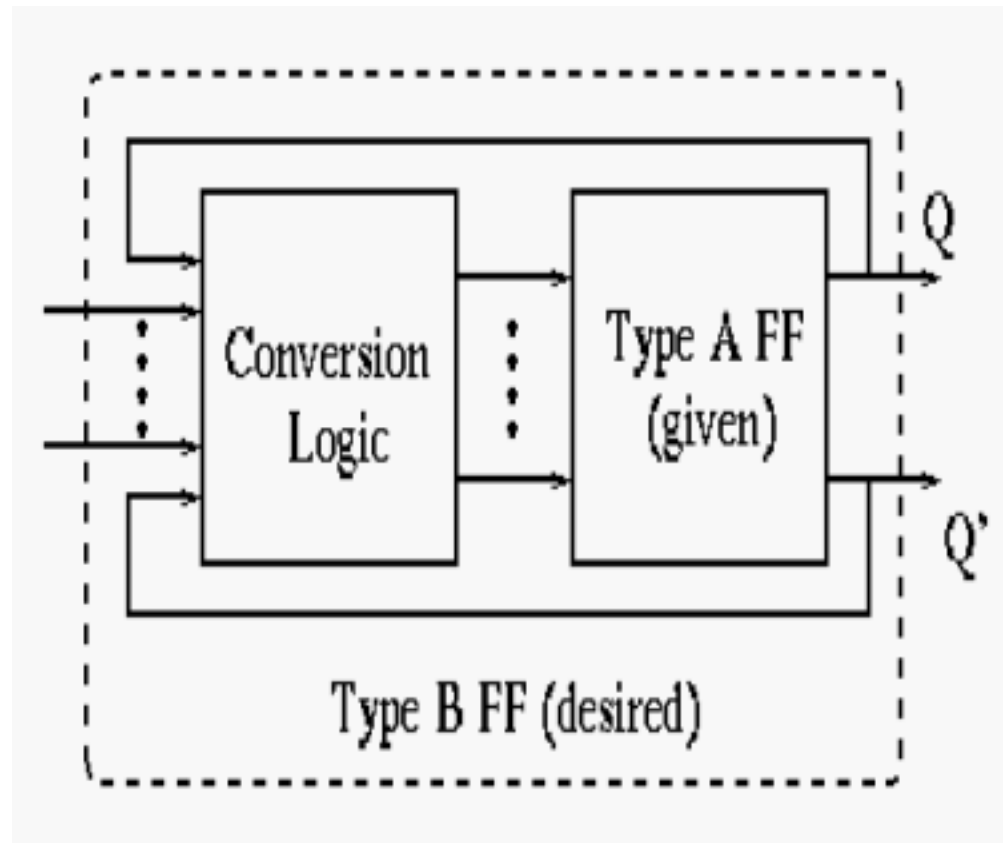


Flip flop Conversion

Flipflop Conversions

The purpose is to convert a given type A FF to a desired type B FF using some conversion logic.



Excitation Table

The key here is to use the excitation table, which shows the necessary


triggering signal (SR, JK, D and T) for a desired flip flop state transition $Q_t - Q_{t+1}$:

Q_t	Q_{t+1}	S	R	J	K	D	T
0	0	0	x	0	x	0	0
0	1	1	0	1	x	1	1
1	0	0	1	x	1	0	1
1	1	x	0	x	0	1	0

Excitation Table of Flip flops based on characteristics table

Convert a D-FF to a T-FF

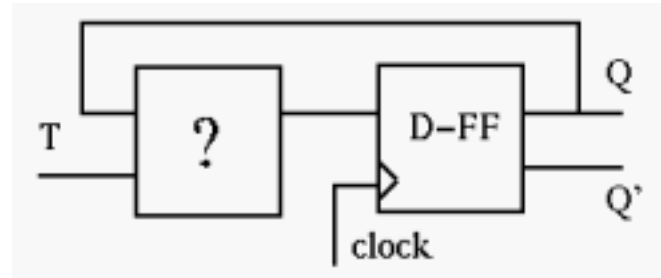The output of D flip flop should be as the output of T flip flop. We need to design the circuit to generate the triggering signal D as a function of T and Q: $D = f(T, Q)$



Consider the excitation table of T and D Flip flops.

Write Down Excitation Table of T, Q_n and Q_{n+1} , D. For the K-map, consider T and Q_n

T	Q_n	Q_{n+1}	D
0	0	0	0
1	0	1	1
1	1	0	0
0	1	1	1

As Input and D as output.


$D = TQ_n' + T'Q_n$ (Ex- OR gate)

Convert a D-FF to a T-FF


Treating as a function of and current FF state Q (Q_t), we

have:

$$D = T'Q + TQ' = T \oplus Q$$

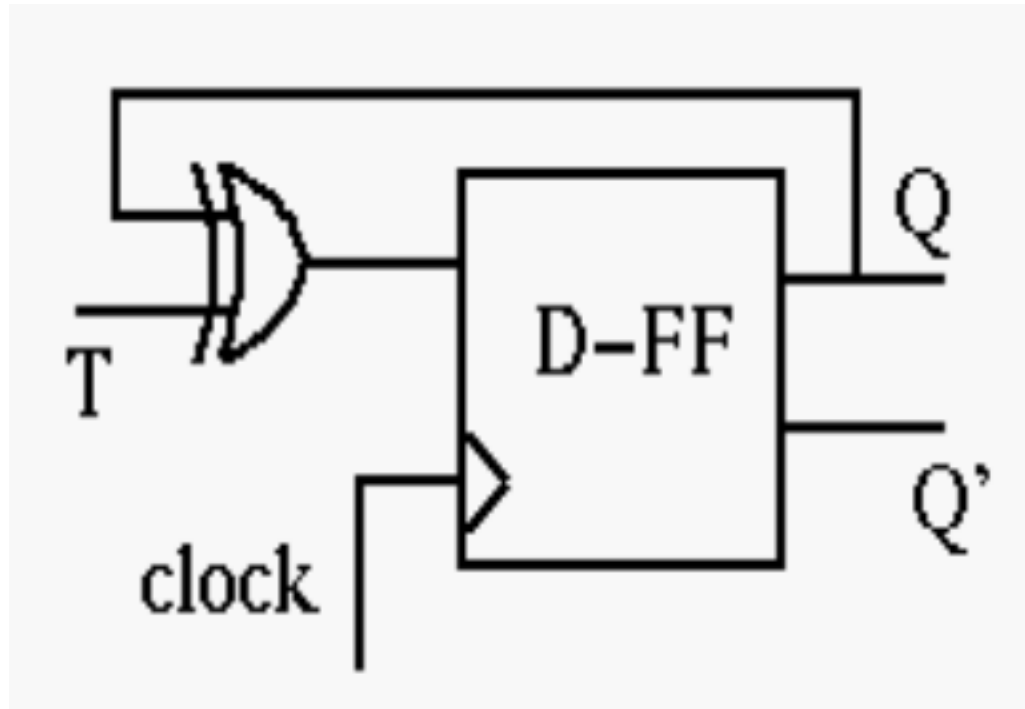

Convert a RS-FF to a D-FF

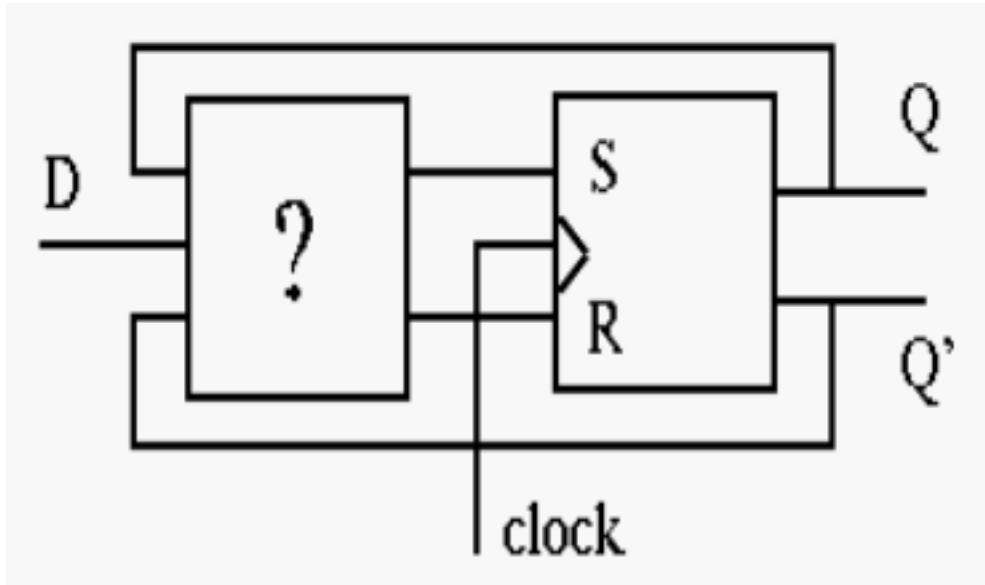

We need to design the circuit to generate the triggering signals S and R as functions of D and Q.

Consider the excitation table

D	Q_t	Q_{t+1}	S	R
0	0	0	0	x
1	0	1	1	0
0	1	0	0	1
1	1	1	x	0

The desired signal S and R can be obtained as functions of D and Q current FF state from the Karnaugh maps:


		Q	
		0	1
D	0	0	0
	1	1	X

$$S = D$$


		Q	
		0	1
D	0	X	1
	1	0	0

$$R = D'$$

Convert a D-FF to a T-FF

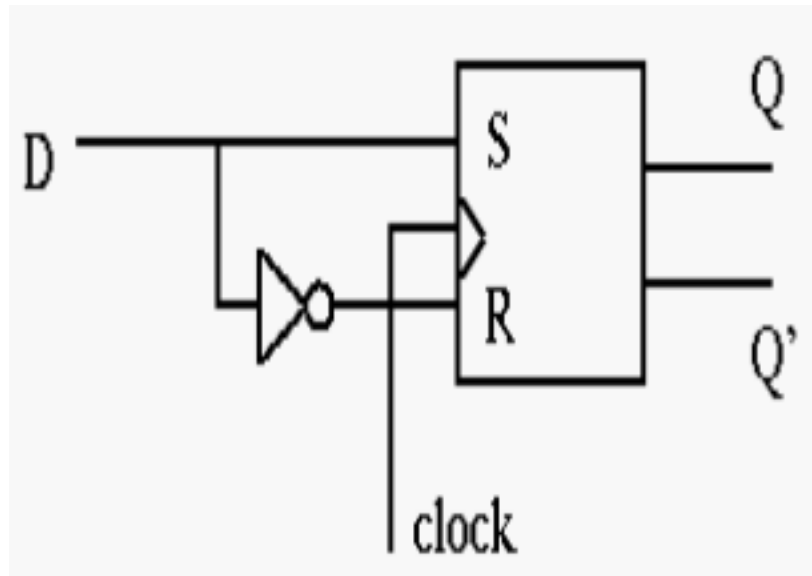

Convert a RS-FF to a JK-FF

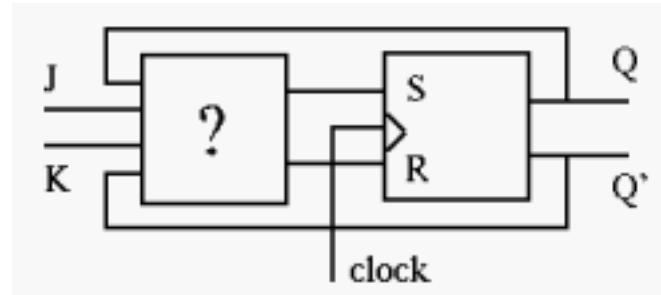

We need to design the circuit to generate the triggering signals S and R as functions of J, K and Q. Consider the excitation table:

J	K	Q_t	Q_{t+1}	S	R
0	x	0	0	0	x
1	x	0	1	1	0
x	1	1	0	0	1
x	0	1	1	x	0

Convert a RS-FF to a JK-FF

The desired signal S and R as functions of J, K and current FF state Q can be obtained from the Karnaugh maps:

		QJ			
		00	01	11	10
K	0	0	1	X	X
	1	0	1	0	0


$$S = Q'J$$

		QJ			
		00	01	11	10
K	0	X	0	0	0
	1	X	0	1	1

$$R = QK$$

Convert a RS-FF to a

JK-FF

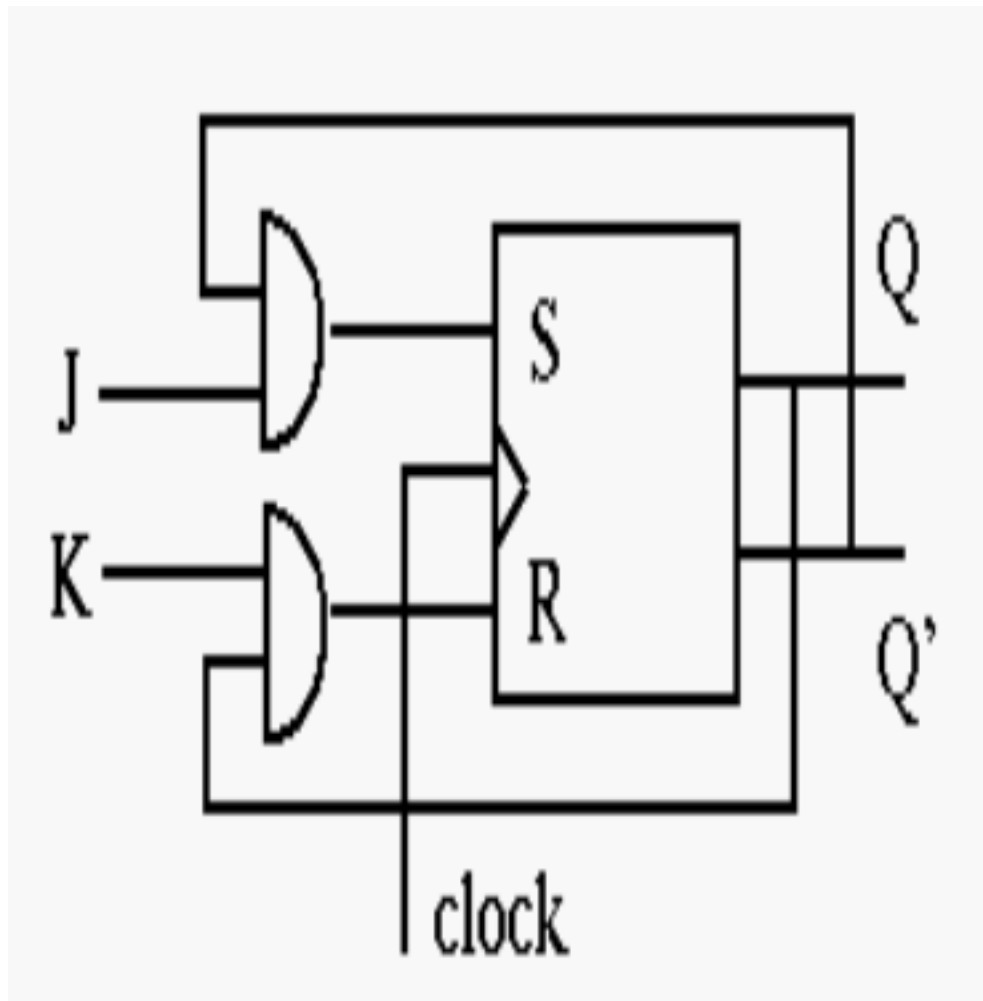

Assignment 23: Total Conversions

SR ---- JK
 D
 T
 D ----- T
 SR
 JK
 T -----D
 SR
 JK
 JK----- D
 T
 SR

Total Conversions – 12 (Practice for all)

Assignment - 23

How about this conversion?

