

# Basic Digital Circuits & Minimization using Boolean ALgebra


# NOT Gate

- A NOT gate accepts one input value and produces one output value

**Boolean Expression**

$$X = A'$$

**Logic Diagram Symbol**

 

**Truth Table**

A	X
0	1
1	0

# NOT Gate

- By definition, if the input value for a NOT gate is 0, the output value is 1, and if the input value is 1, the output is 0
- A NOT gate is sometimes referred to as an ***inverter*** because it inverts the input value


# AND Gate

- An AND gate accepts two input signals
- If the two input values for an AND gate are both 1, the output is 1; otherwise, the output is 0

## Boolean Expression

$$X = A \cdot B$$

## Logic Diagram Symbol

 

## Truth Table

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1


# OR Gate

- If the two input values are both 0, the output value is 0; otherwise, the output is 1

**Boolean Expression**

$$X = A + B$$

**Logic Diagram Symbol**

 

**Truth Table**

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1


# XOR Gate

## Boolean Expression

$$X = A \oplus B$$

$$X = A' \cdot B + A \cdot B'$$

## Logic Diagram Symbol

 

## Truth Table

A	B	X
0	0	0
0	1	1
1	0	1
1	1	0


- XOR, or *exclusive* OR, gate
  - An XOR gate produces 0 if its two inputs are the same, and a 1 otherwise

# XNOR Gate

Also called **Coincidence gate**.

The Output is High when both the inputs are same or Coincident.


$$Y = A \cdot B + A' \cdot B'$$

 


A	B	A'	B'	AB	A'B'	Y=AB+A'B'
0	0	1	1	0	1	1
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	1	0	0	1	0	1

# NAND and NOR Gates



- The NAND and NOR gates are essentially the opposite of the AND and OR gates, respectively

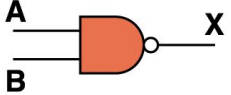Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = (A \cdot B)'$		<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0
A	B	X															
0	0	1															
0	1	1															
1	0	1															
1	1	0															

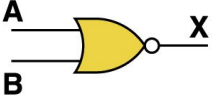Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = (A + B)'$		<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0
A	B	X															
0	0	1															
0	1	0															
1	0	0															
1	1	0															





# NOR Gate

  

$$Z = (X + Y)'$$

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0


# NAND Gate

  

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

# **Universal Property - NAND & NOR**


# NAND Gate as an Inverter Gate

 

X	Z
0	1
1	0

Equivalent to Inverter


# NAND Gate as an AND Gate

 

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

Equivalent to AND Gate

# NAND Gate as an OR Gate

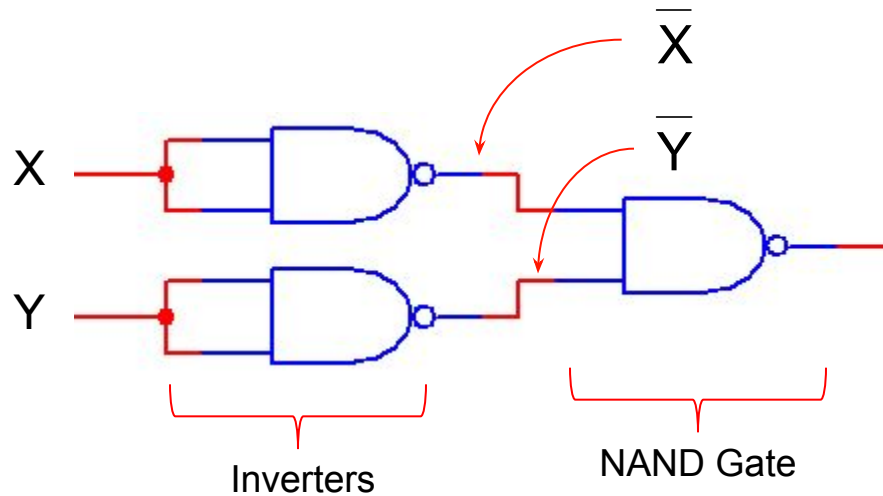

$$Z = \overline{\overline{X} \cdot \overline{Y}} = \overline{\overline{X}} + \overline{\overline{Y}} = X + Y$$



X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

Equivalent to OR Gate


# Universal Property - NAND & NOR
  
## NOR GATE AS A UNIVERSAL LOGIC ELEMENT

NOR gate is also a **universal gate** because it can be used to produce the **NOT**, **AND**, **OR** and **NAND** functions.




(a) One NOR gate used as an inverter

 

(b) Two NOR gates used as an OR gate

# Universal Property - NAND & NOR
 
## NOR GATE AS A UNIVERSAL LOGIC ELEMENT (Cont.)



(c) Three NOR gates used as an AND gate



# Introduction to Boolean Algebra

- Developed by English Mathematician *George Boole* in between 1815 - 1864.
- It is described as *an algebra of logic* or *an algebra of two values* i.e *True* or *False*.
- The term *logic* means a statement having binary decisions i.e *True/Yes* or *False/No*.

# Application of Boolean algebra

- It is used to perform the logical operations in digital computer.
- In digital computer **True** represent by '1' (high volt) and **False** represent by '0' (low volt)
- Logical operations are performed by logical operators.  
The fundamental logical operators are:
  1. **AND** (conjunction)
  2. **OR** (disjunction)
  3. **NOT** (negation/complement)

# Truth Table

- **Truth table** is a table that contains all possible values of logical variables/statements in a Boolean expression.

No. of possible combination =

$2^n$ , where  $n$ =number of variables used in a Boolean expression.

# Truth Table

- The truth table for  $XY + Z$  is as follows:

Dec	X	Y	Z	XY	XY+Z
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	0
3	0	1	1	0	1
4	1	0	0	0	0
5	1	0	1	0	1
6	1	1	0	1	1
7	1	1	1	1	1

# ***Boolean LAWS***

## ***(Existence of 1 and 0 element)***

$$(1) \quad x + 0 = x$$

$$(2) \quad x \cdot 0 = 0$$

$$(3) \quad x + 1 = 1$$

$$(4) \quad x \cdot 1 = x$$

## ***(Existence of complement)***

$$(5) \quad x + x = x$$

$$(6) \quad x \cdot x = x$$

$$(7) \quad x + x' = 1$$

$$(8) \quad x \cdot x' = 0$$

***(Commutativity):***

$$(9) \ x + y = y + x$$

$$(10) \ xy = yx$$

***(Associativity):***

$$(11) \ x + ( y + z ) = ( x + y ) + z$$

$$(12) \ x (yz) = (xy) z$$

***(Distributivity):***

$$(13) \ x ( y + z ) = xy + xz$$

$$(14) \ x + yz = ( x + y )( x + z )$$

***(DeMorgan's Theorem)***

$$(15) \ ( x + y )' = x' y'$$

$$(16) \ ( xy )' = x' + y'$$



## ***(Absorption Law)***

$$1) X + XY = X$$

$$\text{LHS: } X + XY$$

$$\Rightarrow X(1 + Y) \quad \text{Using } 1 + Y = 1$$

$$\Rightarrow X$$

$$2) X + X'Y = X + Y$$

$$\text{LHS: } X + X'Y$$

$$\Rightarrow X + XY + X'Y \quad \text{Using } X = X + XY \text{ i.e First Absorption Law}$$

$$\Rightarrow X + Y(X + X') \quad \text{Using } X + X' = 1$$

$$\Rightarrow X + Y$$

## ***(Involution)***

$$(17) \ (x')' = x$$

# Minimization of Boolean Expression

- Minimization of Boolean expression is needed to simplify the Boolean expression and thus reduce the circuitry complexity as it uses less number of gates to produce same output that can be taken by long expression.

## □ Algebraic Method

- The different Boolean rules and theorems are used to simplify the Boolean expression in this method.

# Minimization of Boolean Expression (Contd...)

## Solved Problem

Minimize the following Boolean Expression:

1.  $a'bc + ab'c' + ab'c + abc' + abc$

$$= a'bc + ab'(c' + c) + ab(c' + c)$$

Using  $X + X' = 1$

$$= a'bc + ab' + ab$$

$$= a'bc + a(b' + b)$$

$$= a'bc + a$$

2.  $AB'CD' + AB'CD + ABCD' + ABCD$

$$= AB'C(D' + D) + ABC(D' + D)$$

Using  $X + X' = 1$

$$= AC(B' + B)$$

$$= AC$$

A	B	C	D	MINTERM	DESIGNATION	MAXTERM	DESIGNATION
0	0	0	0	$A'B'C'D'$	$m_0$	$A+B+C+D$	$M_0$
0	0	0	1	$A'B'C'D$	$m_1$	$A+B+C+D'$	$M_1$
0	0	1	0	$A'B'CD'$	$m_2$	$A+B+C'+D$	$M_2$
0	0	1	1	$A'B'CD$	$m_3$	$A+B+C'+D'$	$M_3$
0	1	0	0	$A'BC'D'$			
0	1	0	1	$A'BC'D$			
0	1	1	0				
0	1	1	1				
1	0	0	0				
1	0	0	1				
1	0	1	0				
1	0	1	1				
1	1	0	0				
1	1	0	1				
1	1	1	0				
1	1	1	1				

1. Prove  $A' + AB = (A' + B)$

2.  $(A + B).(A' + C) = AC + A'B + BC$

3.  $AB + A'C + BC = (A + C).(A' + B)$