

Flip Flops

TRUTH TABLE FOR SR F/F

S	R	QN	QN+1	
0	0	0	0	NO CHANGE
0	0	1	1	
0	1	0	0	RESET
0	1	1	0	
1	0	0	1	SET
1	0	1	1	
1	1	0	X	PROHIBITED STATE
1	1	1	X	

TRUTH TABLE FOR JK F/F


J	K	QN	QN+1	
0	0	0	0	NO CHANGE
0	0	1	1	
0	1	0	0	J VALUE FORWARDED
0	1	1	0	
1	0	0	1	
1	0	1	1	
1	1	0	1	TOGGLE CASE
1	1	1	0	

TRUTH TABLE FOR T F/F

T	QN	QN+1	
0	0	0	NO CHANGE
0	1	0	
1	0	1	TOGGLE CASE
1	1	1	



TRUTH TABLE FOR D F/F

D	Q _N	Q _{N+1}
0	0	0
0	1	0
1	0	1
1	1	1





INPUT VALUE
FORWARDED
WITH SOME
DELAY

Other Flip Flops

  

Toggle Flip-Flop

  

Delay Flip-Flop (D-latch)

EXCITATION TABLE FOR F/F

PRESS ENT STATE	NEXT STATE	S	R	J	K	T	D
0	0	0	X	0	X	0	0
0	1	1	0	1	X	1	1
1	0	0	1	X	1	1	0
1	1	X	0	X	0	0	1

CONVERSION FROM ONE F/F TO ANOTHER


STEP1-Combine the excitation tables for both Flipflops, make a truth table.

The truth table has input values of target f/f as inputs of truth table and Inputs of Given or source f/f as outputs of the truth table.

STEP2-Draw the Kmap for each output & obtain the simplified expression.

STEP3-Implement using logic gates.

CONVERSION FROM ONE F/F TO ANOTHER

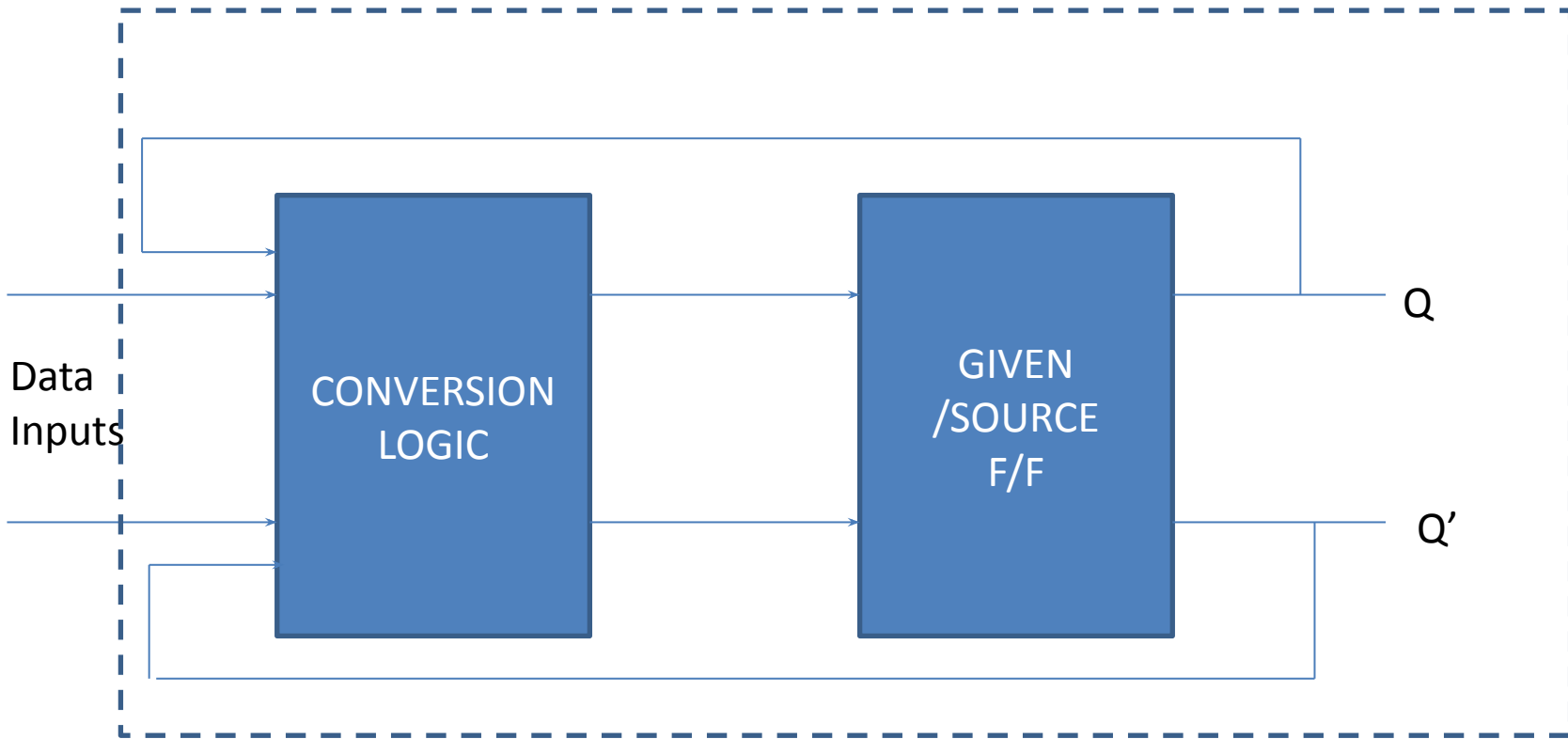

CONVERSION FROM SR F/F TO D F/F

- Truth table for SR to D Conversion

D	PRESENT STATE QN	NEXT STATE QN+1	S	R
0	0	0	0	X
1	0	1	1	0
0	1	0	0	1
1	1	1	X	0

Entries from Excitation
Table of D FF

Entries from Excitation
Table of SR FF


Kmaps for S&R

QN		0	1
D	0		
	1	1	X

$S=D$
Kmap for S

QN		0	1
D	0	X	1
	1		

$R=D'$
Kmap for R

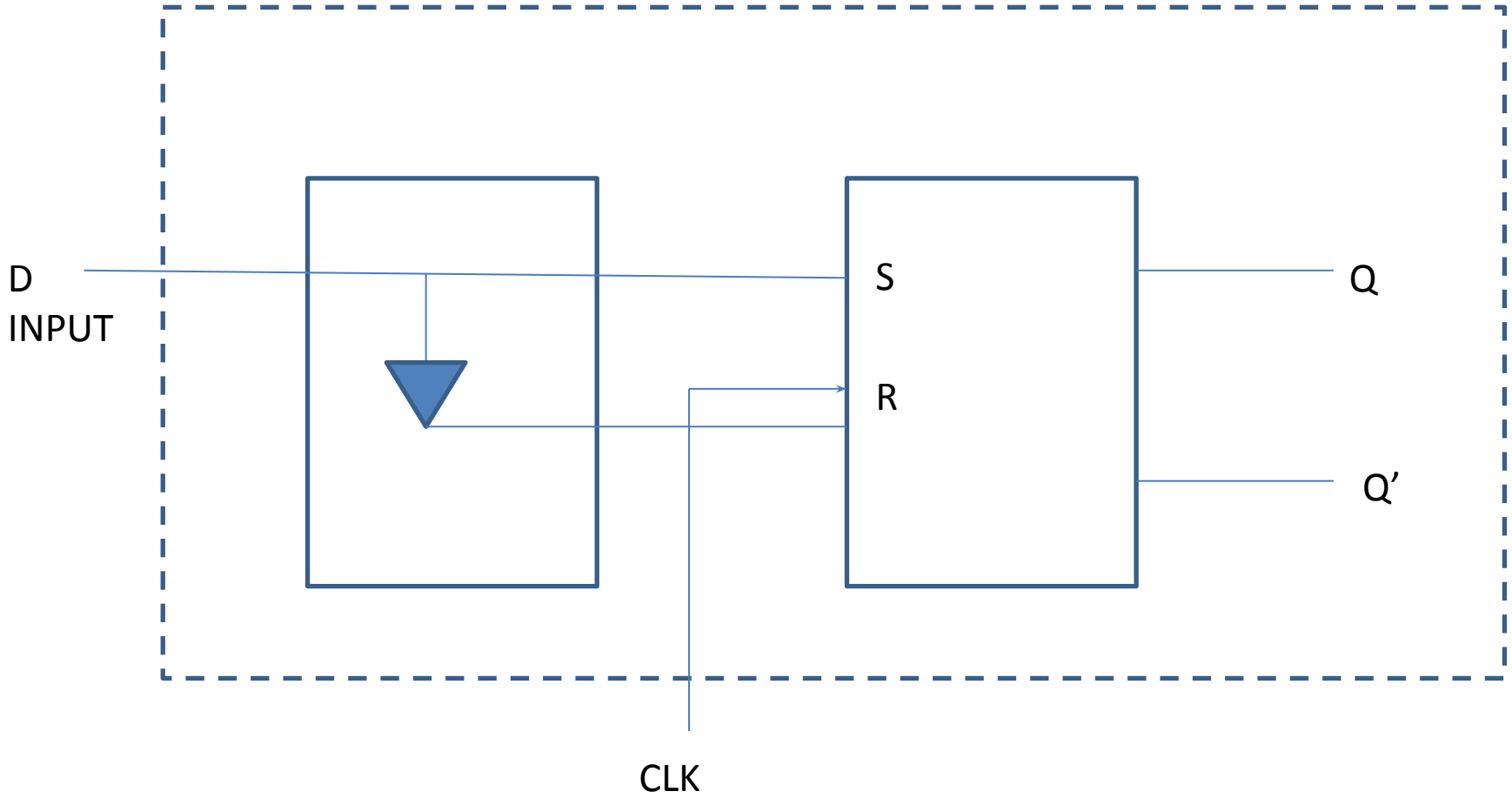

REGISTER

Register is composed of a group of flip flops to store data.

N f/f are used for storing N bit word.


1 f/f can store 1 bit of information

SHIFT REGISTERS


- Shift registers are a type of sequential logic circuit.
- They are a group of flip-flops connected in a chain so that the output from one flip-flop becomes the input of the next flip-flop.
- All flip-flop is driven by a common clock, and all are set or reset simultaneously.

- Shift registers are used for
 - Data Storage
 - Data movement
 - Arithmetic & Logic Operations


MODES OF OPERATION OF A SHIFT REGISTER

 


(a) Serial in/shift right/serial out

 


(b) Serial in/shift left/serial out

 

(c) Parallel in/serial out

 



(d) Serial in/parallel out

 


(e) Parallel in/parallel out

SISO(SHIFT RIGHT MODE)

 

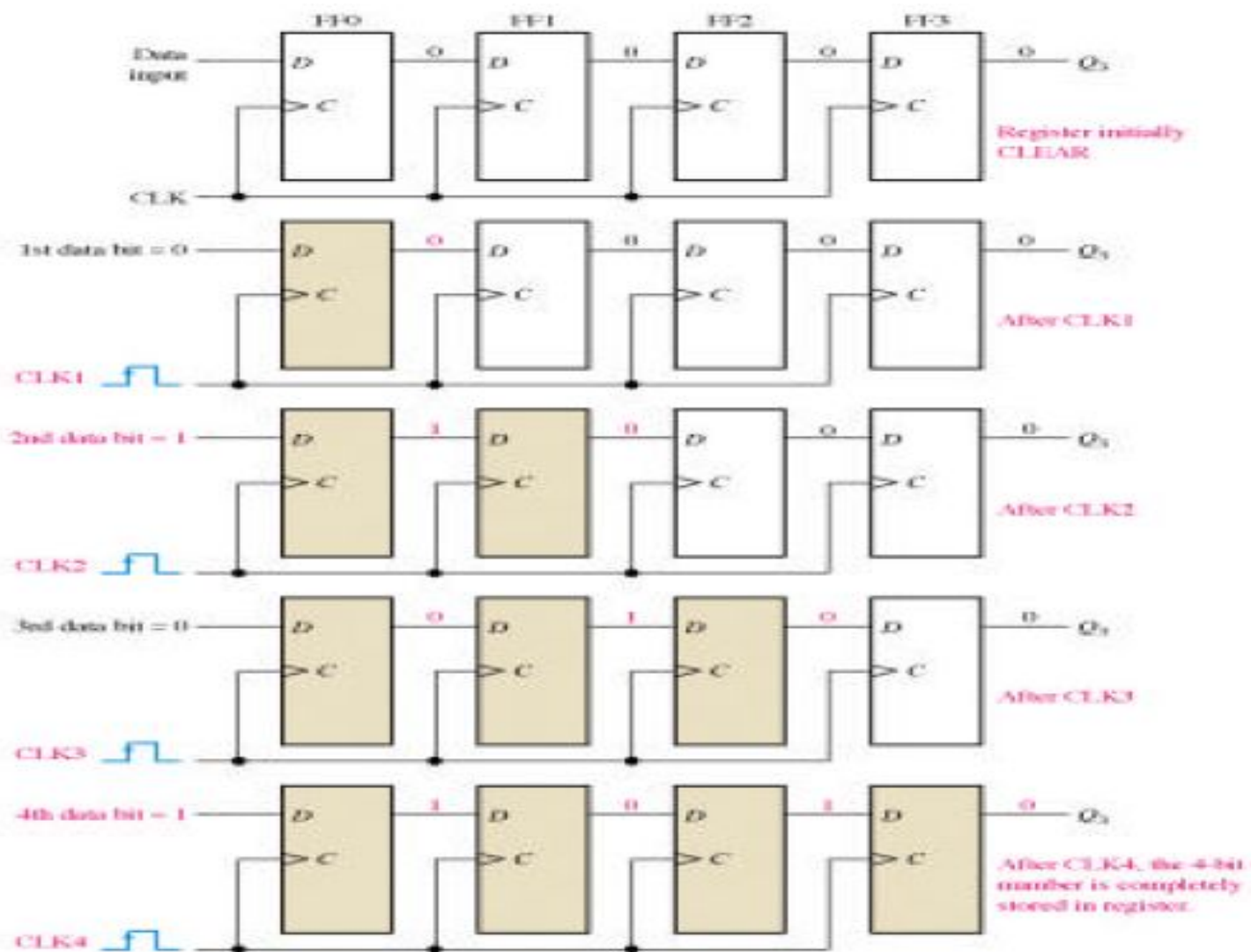


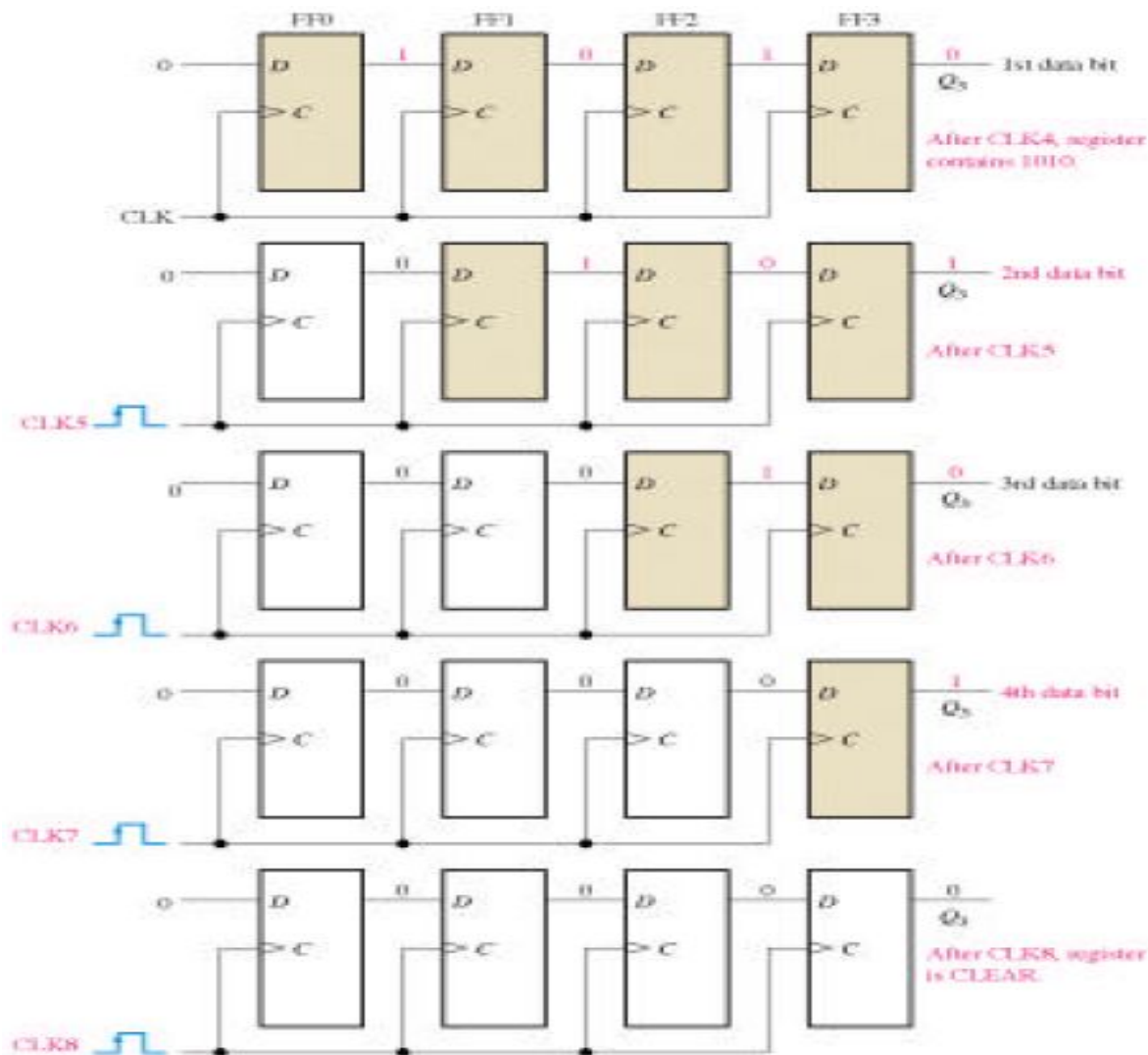Four bits (1010) being entered serially into the register.




Four bits (1010) being serially shifted out of the register and replaced by all zeros


SIPO (SERIAL INPUT PARALLEL OUTPUT)

 



PIPO(PARALLEL IN PARALLEL OUT)

 

PISO(PARALLEL IN SERIAL OUT)


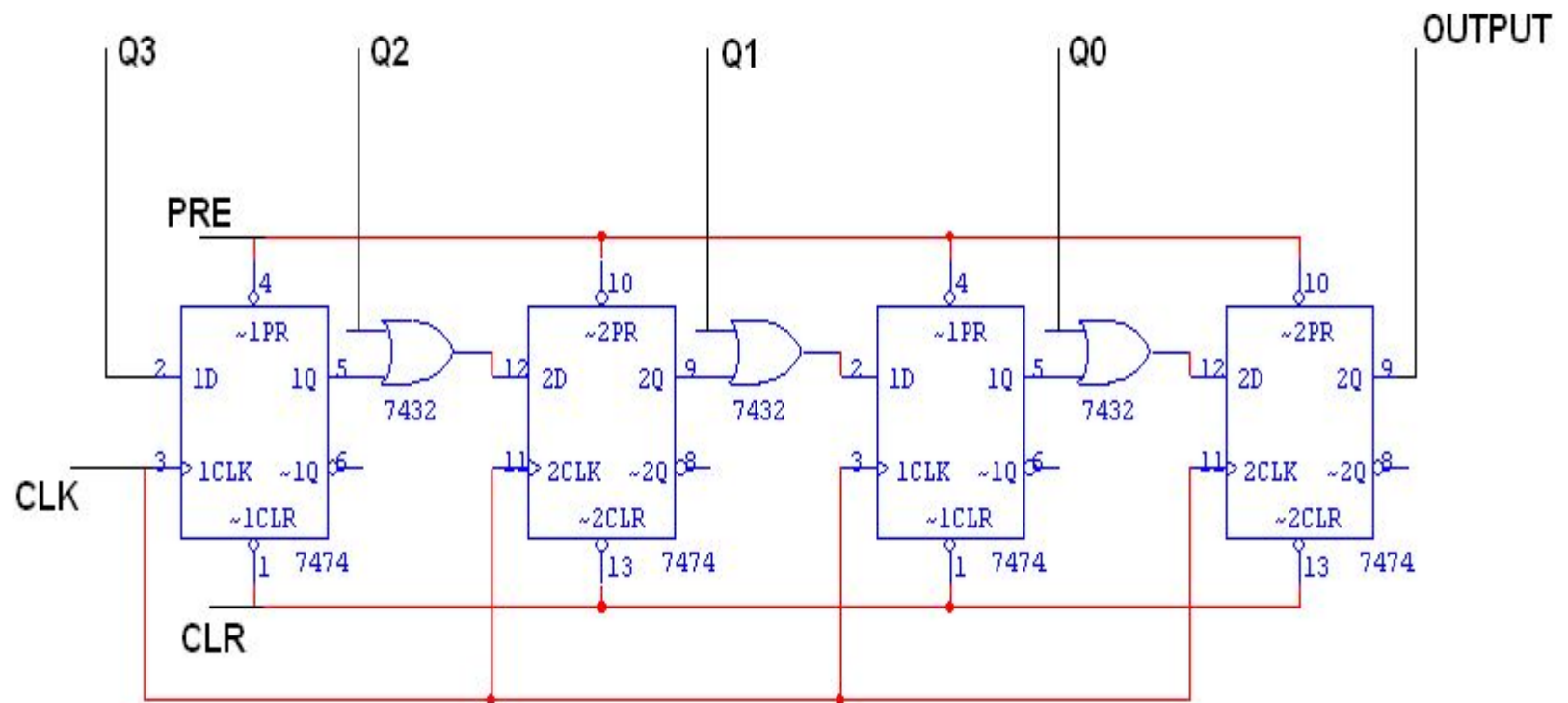


Race Problem

  

Signal can race around during $\phi = 1$

Master-Slave Flip Flop Implementation

  

Master transmits the signal to the output during the high clock phase and slave is waiting for the clock to change this prevents race conditions