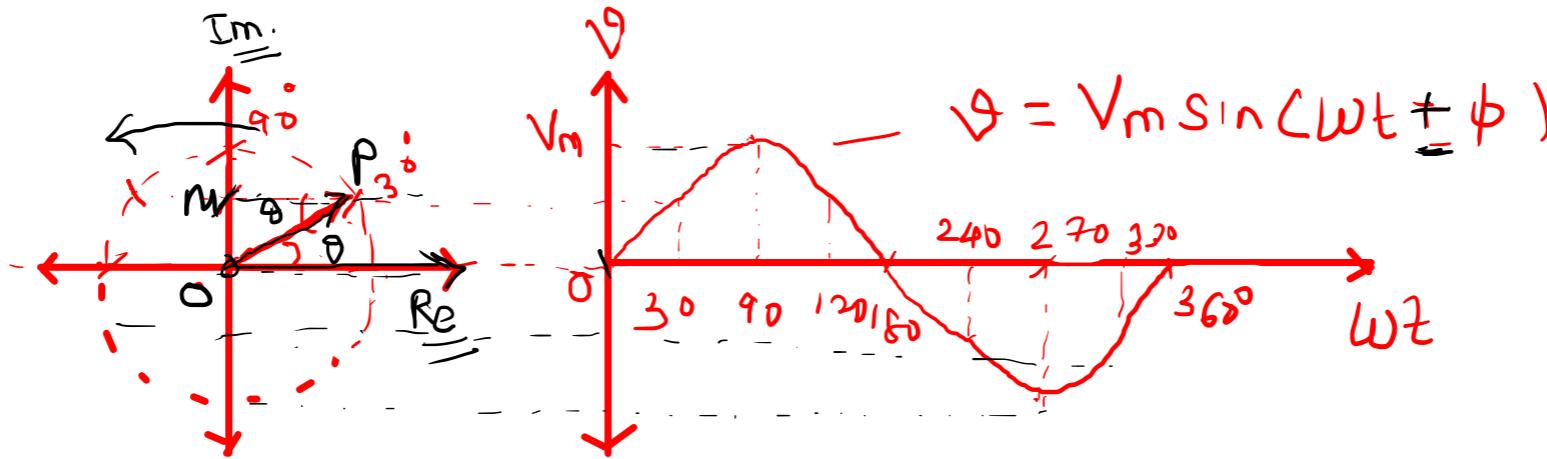


Phasor Representation of alternating quantities



$$\underline{\theta} = \underline{V_m} \sin \underline{\theta} = \underline{V_m} \sin \underline{\omega A}$$

$$\underline{\sin \theta} = \frac{\underline{OM}}{\underline{OP}}$$


$$\underline{OM} = \underline{OP} \sin \underline{\theta}$$

$$\theta = \sqrt{m} \sin(\omega t + \phi)$$

Lagging
Leading

$$\leftarrow \theta_2 = \sqrt{m} \sin(\omega t - 90^\circ)$$
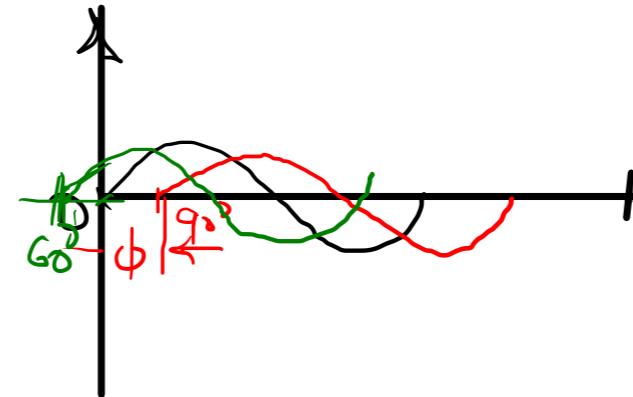
$$\theta_3 = \sqrt{m} \sin(\omega t + 60^\circ)$$



Mathematical representation of phasor

① Rectangular form

$$\bar{V} = \underline{x} + j\underline{y} \quad |V| = \sqrt{x^2 + y^2}$$

$$\text{Phase angle } \phi = \tan^{-1}\left(\frac{y}{x}\right)$$


② Triangular

$$V = V_m [\cos \phi + j \sin \phi]$$

③ Exponential $V = V e^{+j\phi}$

④ Polar form $\theta = |V| < \phi$


①

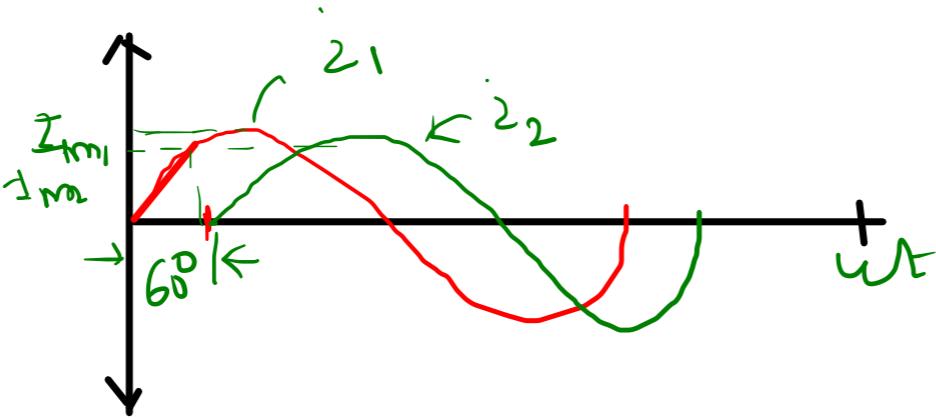

$$i_1 = I_{m1} \sin(\omega t) = |I_{m1}| \angle 0^\circ$$

$$i_2 = I_{m2} \sin(\omega t - 60^\circ) = |I_{m2}| \angle -60^\circ$$

$$i_3 = I_{m3} \sin(\omega t + 45^\circ) = |I_{m3}| \angle 45^\circ$$

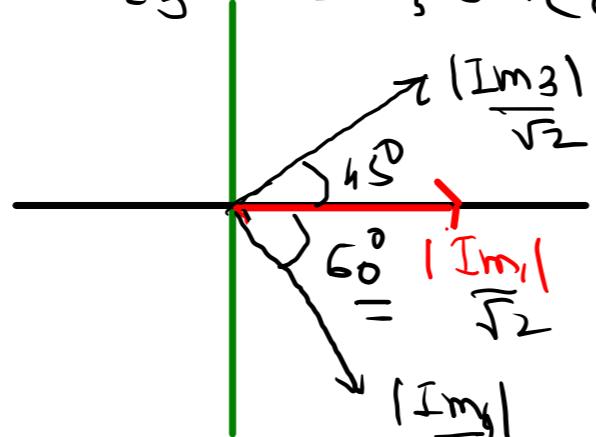

✓ I_{m2} is lagging I_{m1} by 60°

✓ I_{m1} is leading I_{m2} by 60°

$\sqrt{2}$ Rms value of alternating quantity
phasor

① Two sinusoidal currents are given as

$$i_1 = 10\sqrt{2} \sin \omega t \quad \& \quad i_2 = 20\sqrt{2} \sin(\omega t + 90^\circ)$$

Find sum of the currents

$$\Rightarrow \bar{i} = \bar{i}_1 + \bar{i}_2$$

$$= \left(\frac{10\sqrt{2}}{\sqrt{2}} \right) \angle 0^\circ + \frac{20\sqrt{2}}{\sqrt{2}} \angle 90^\circ$$

$$= 10 \angle 0^\circ + 20 \angle 90^\circ$$

$$= 10 [\cos 0 + j \sin 0] + 20 [\cos 90 + j \sin 90]$$

$$= 10 [1 + j 0] + 20 [0 + j \sin 90]$$

$$\bar{i} = \underline{(10 + j 20 \sin 90)}$$

① Two sinusoidal currents are given as

$$i_1 = 10\sqrt{2} \sin \omega t \quad \& \quad i_2 = 20\sqrt{2} \sin(\omega t + 90^\circ)$$

Find sum of the currents

$$\Rightarrow \bar{i} = \bar{i}_1 + \bar{i}_2$$

$$= \left(\frac{10\sqrt{2}}{\sqrt{2}} \right) \angle 0^\circ + \frac{20\sqrt{2}}{\sqrt{2}} \angle 90^\circ$$

$$= 10 \angle 0^\circ + 20 \angle 90^\circ$$

$$= 10 [\cos 0 + j \sin 0] + 20 [\cos 90 + j \sin 90]$$


$$= 10 [1 + j 0] + 20 [0 + j \sin 90]$$

$$\bar{i} = \underline{(10 + j 20 \sin 90)}$$


⇒ Resultant of phasors:

⇒ Law of triangle; If two vectors acting at a point are represented in magnitude and direction by two adjacent sides of the triangle taken in order then closing side of triangle taken in reverse order represents the resultant

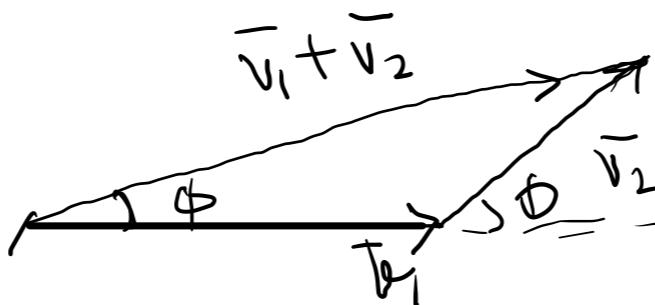
$$V_1 = V_m \sin \text{left} \quad \& \quad V_2 = V_m \sin (\text{left} + \theta)$$



⇒ Law of parallelogram

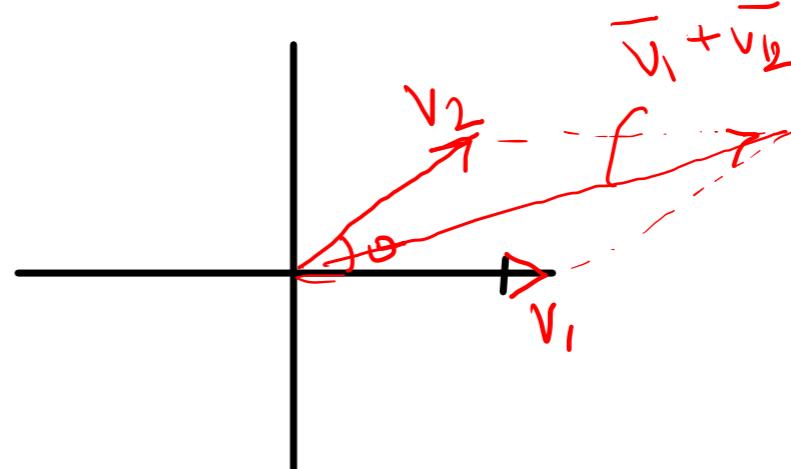


✓ Inphase

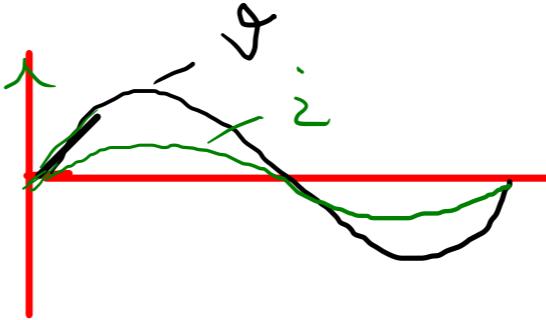


v & i are in phase

✓ Out of phase

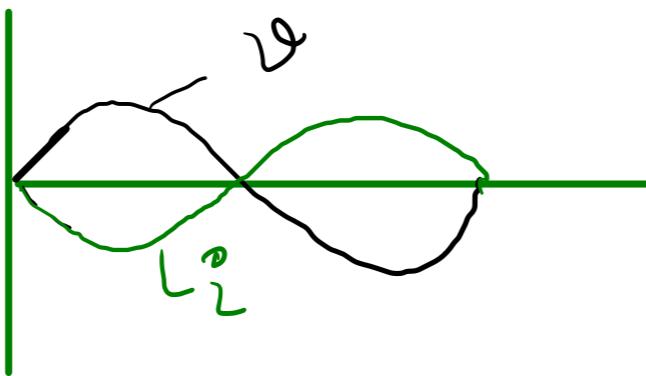


v & i are out of phase
phase diff of 180° .

Pure resistor with AC input

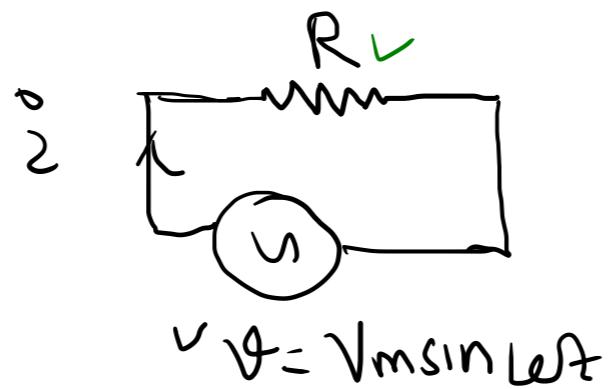

$$i = \frac{v}{R} = \frac{V_m \sin \omega t}{R} = \frac{V_m}{R} \sin \omega t = I_m \sin \omega t$$

Phasor Diagram

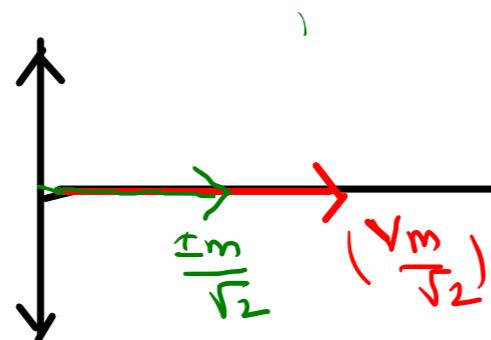

Voltage & Current are inphase

$$\underline{\text{Impedance}} = \frac{v}{i} = \frac{V_m \sin \omega t}{I_m \sin \omega t} = \frac{V_m}{I_m} = R$$

$$\text{Power factor} = \cos \phi = \cos(0) \leq 1$$


Instantaneous Power

$$\text{Instantaneous Power} = \underline{\underline{V}} \times \underline{\underline{I}}$$

$$= V_m \sin \omega t \cdot I_m \sin \omega t =$$

$$\begin{aligned} \text{Instantaneous Power} &= \underline{\underline{V_m I_m \sin^2 \omega t}} \\ &= \underline{\underline{V_m I_m \left[1 - \frac{\cos 2\omega t}{2} \right]}} \end{aligned}$$
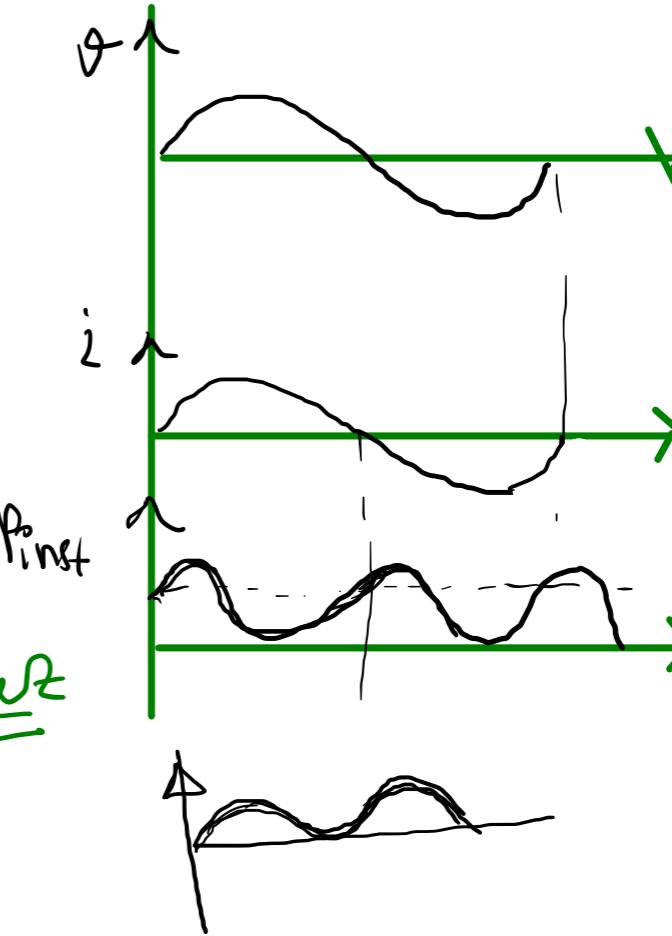
$$= \underline{\underline{\frac{V_m I_m}{2}}} - \underline{\underline{\frac{V_m I_m}{2} \cos 2\omega t}}$$



Instantaneous Power


$$\text{Instantaneous Power} = \underline{\underline{V}} \times \underline{\underline{I}}$$

$$= V_m \sin \omega t \cdot I_m \sin \omega t =$$

$$\begin{aligned} \text{Instantaneous Power} &= \underline{\underline{V_m I_m \sin^2 \omega t}} \\ &= \underline{\underline{V_m I_m \left[1 - \frac{\cos 2\omega t}{2} \right]}} \end{aligned}$$

$$= \underline{\underline{\frac{V_m I_m}{2}}} - \underline{\underline{\frac{V_m I_m}{2} \cos 2\omega t}}$$

Waveforms

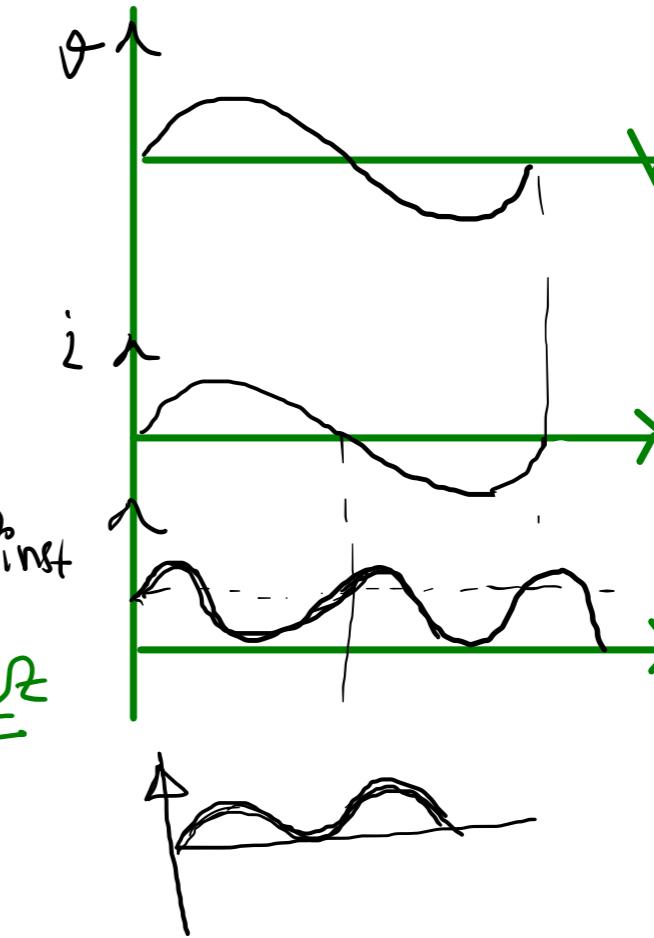

Average power consumed in resistor

$$\text{Average Power} = \frac{1}{2\pi} \int_0^{2\pi} P_{\text{inst}} dt$$

$$= \frac{1}{2\pi} \int_0^{2\pi} V_m I_m \sin^2 \omega t dt$$


$$= \frac{V_m I_m}{2\pi} \int_0^{2\pi} \frac{1 - \cos 2\omega t}{2} dt$$

$$= \frac{V_m I_m}{2\pi} \left[\frac{\omega t}{2} - \frac{\sin 2\omega t}{2} \right]_0^{2\pi}$$

$$= \frac{V_m I_m}{2\pi \cdot 2} [2\pi - 0 - 0] = 0$$

$$= \frac{V_m I_m}{2} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} = \underline{\underline{V_{\text{rms}} \cdot I_{\text{rms}}}}$$

Pure inductor with AC input

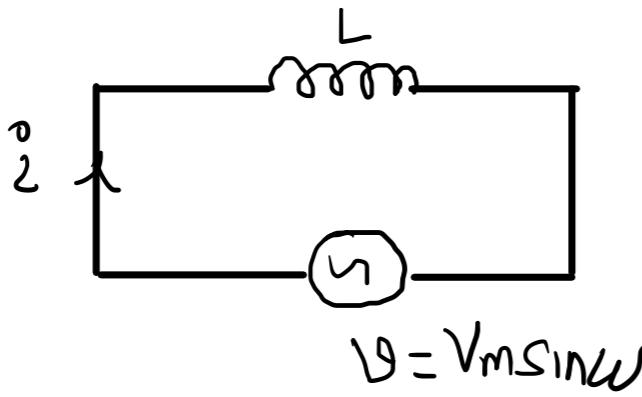


$$v = V_m \sin \omega t \quad \text{OR} \quad i = \frac{1}{L} \int v dt$$


$$\begin{aligned} i &= \frac{1}{L} \int V_m \sin \omega t dt \\ &= \frac{V_m}{L} \left[-\frac{\cos \omega t}{\omega} \right] \\ &= \frac{V_m}{\omega L} \left[\sin \left(\omega t - \frac{\pi}{2} \right) \right] \end{aligned}$$

$$i = I_m \sin \left(\omega t - \frac{\pi}{2} \right)$$
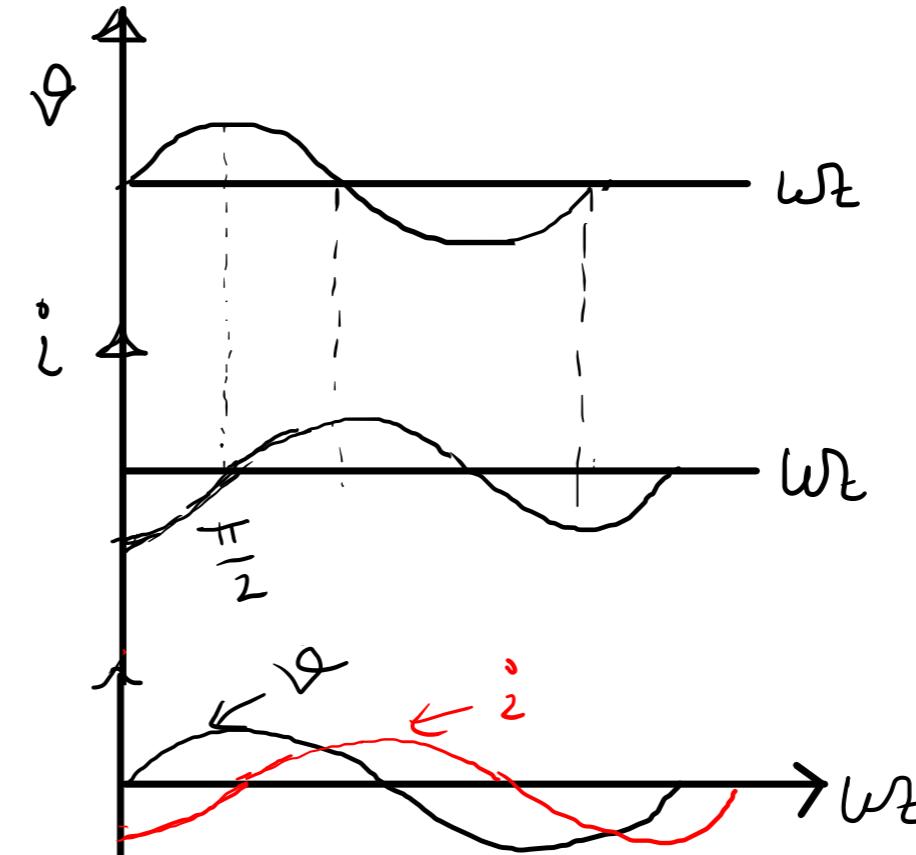
$$\text{where } I_m = \frac{V_m}{\omega L}$$



Pure inductor with AC input

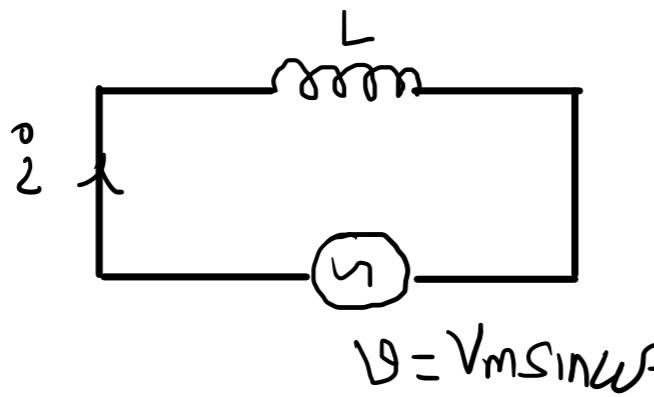


$$v = V_m \sin \omega t \quad \text{OR} \quad i = \frac{1}{L} \int v dt$$


$$\begin{aligned} i &= \frac{1}{L} \int V_m \sin \omega t dt \\ &= \frac{V_m}{L} \left[-\frac{\cos \omega t}{\omega} \right] \\ &= \frac{V_m}{\omega L} \left[\sin \left(\omega t - \frac{\pi}{2} \right) \right] \end{aligned}$$

$$i = I_m \sin \left(\omega t - \frac{\pi}{2} \right)$$
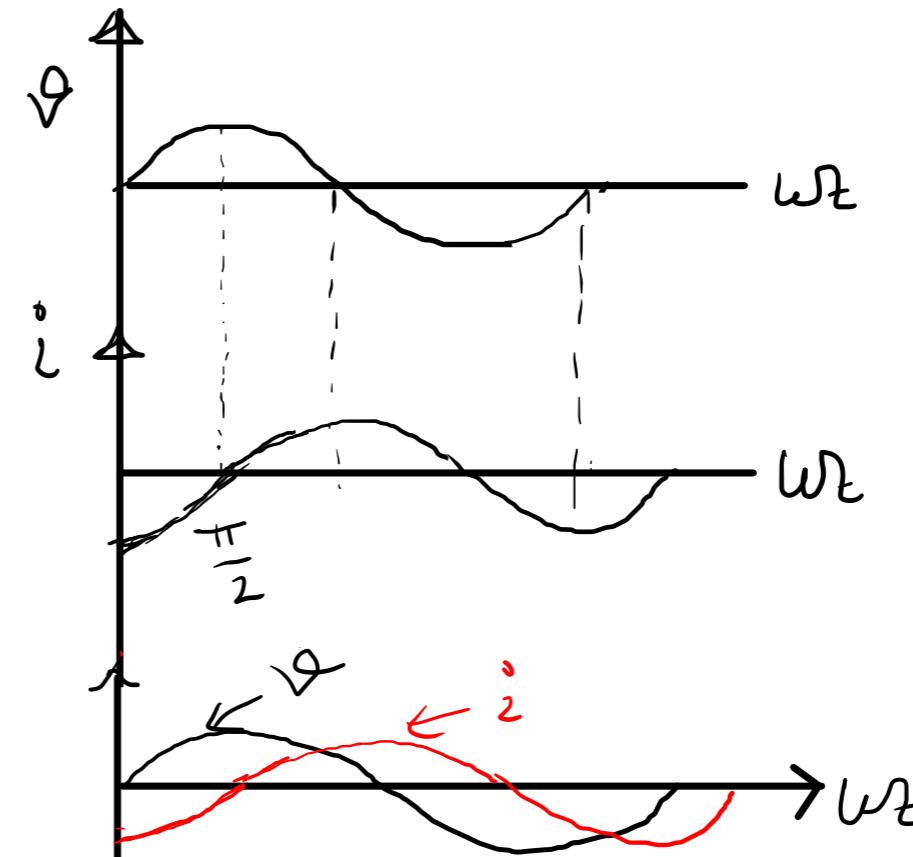
$$\text{where } I_m = \frac{V_m}{\omega L}$$



Phasor diagram

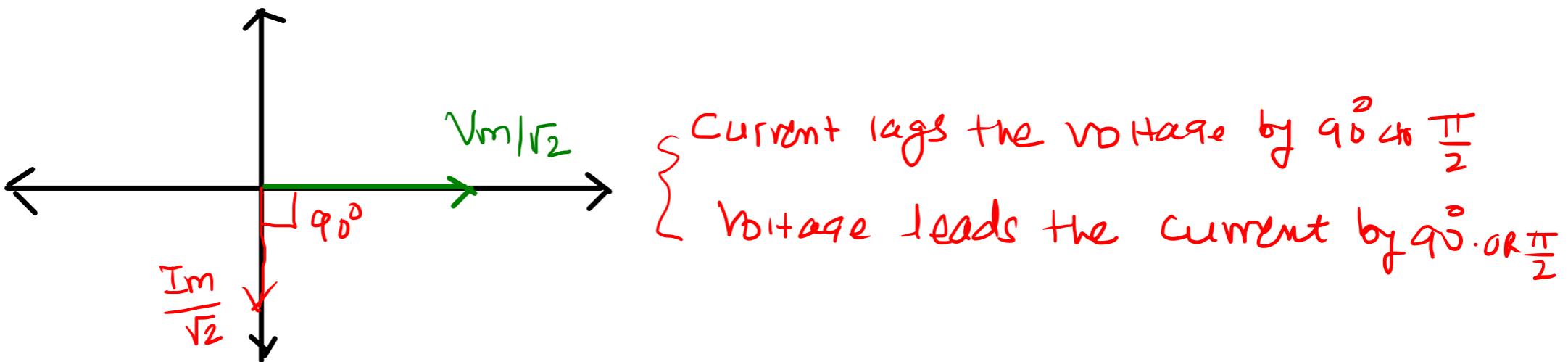

Impedance

$$Z = \frac{V}{I} = \frac{V_m}{I_m} = \frac{V_m}{V_m/\omega L} = \omega L$$

$$\omega L = X_L \Rightarrow \text{Inductive Reactance} = 2\pi f \cdot L$$

For DC input $f=0$ so $X_L = 2\pi f L = 0 \Omega$ so inductor acts as short circuit

Power factor: It is cosine of angle between the voltage and current phasors.

$$PF = \cos\phi = \cos(90^\circ) = 0$$

Instantaneous Power

$$P_{inst} = V \cdot i$$

$$= V_m \sin \omega t \times (-I_m \cos \omega t)$$

$$= -V_m I_m \sin \omega t \cdot \cos \omega t$$


$$\boxed{P_{inst} = -\frac{V_m I_m}{2} \sin 2\omega t}$$

Average power

$$\begin{aligned} P_{av} &= \frac{1}{2\pi} \int_0^{2\pi} P_{inst} dt = \frac{1}{2\pi} \left[\int_0^{2\pi} -\frac{V_m I_m}{2} \sin 2\omega t dt \right] \\ &= \frac{1}{2\pi} \left[-\frac{V_m I_m}{2} \left[-\frac{\cos 2\omega t}{2} \right] \right]_0^{2\pi} = \frac{V_m I_m}{8\pi} [\cos 4\pi - \cos 0] = 0 \end{aligned}$$

$P_{av} = 0$ Hence power consumed by pure inductor is zero.

Pure Capacitor with AC input

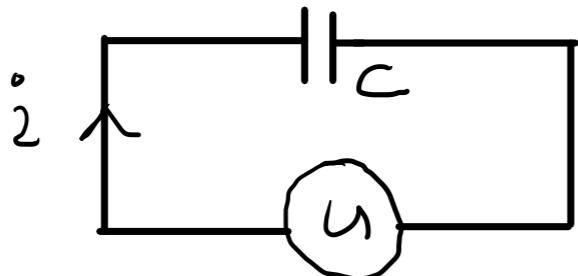

$$i = C \frac{dV}{dt}$$

$$V = V_m \sin \omega t$$

$$i = C \cdot \frac{d}{dt} [V_m \sin \omega t]$$

$$= V_m \cdot C [\cos \omega t \times \omega]$$

$$i = V_m \cdot \omega C [\cos \omega t]$$

$$i = I_m \cos \omega t$$

$$i = I_m \sin(\omega t + \frac{\pi}{2})$$

where $I_m = \frac{V_m}{\omega C}$

$$\text{So } \frac{V_m}{I_m} = \frac{1}{\omega C}$$

$$\text{Impedance } Z = \frac{V_m}{I_m} = \frac{1}{\omega C} = X_C$$


where $X_C = \frac{1}{\omega C}$ is Capacitive Reactance

$$X_C = \frac{1}{2\pi f C}$$


for DC Input $f = 0$ so $X_C = \frac{1}{0} = \infty$

so for DC input capacitor acts Open Circuit.

Waveforms:

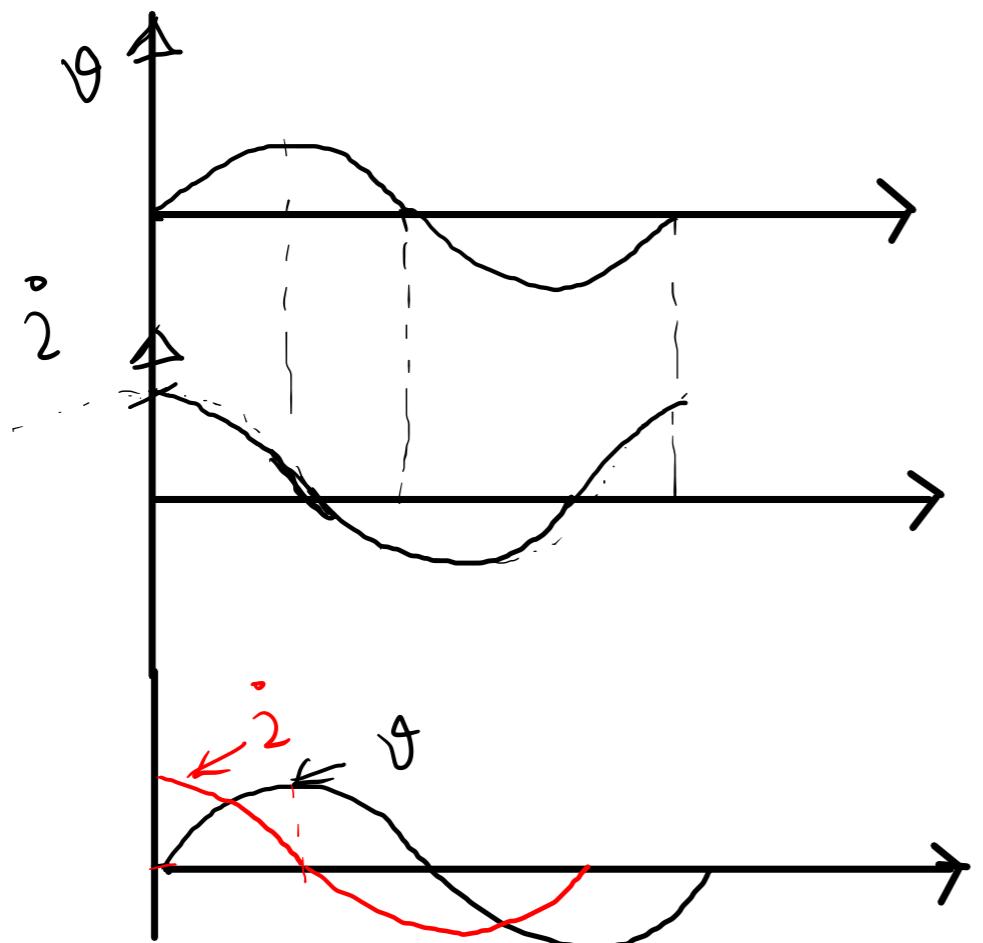

Phasor diagram

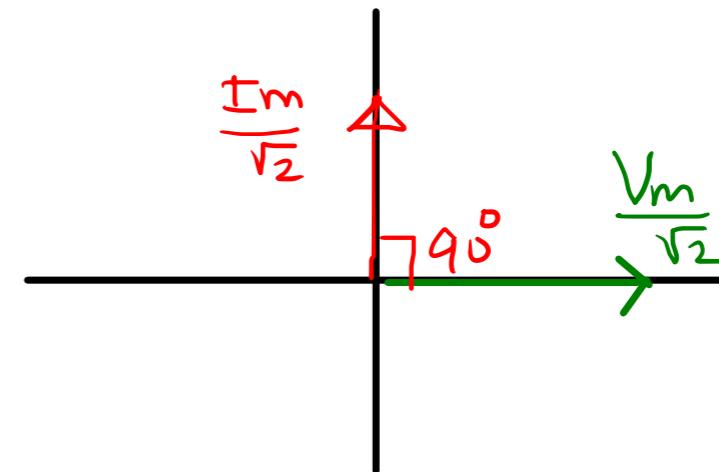

Power factor = $\cos \phi = \cos(90^\circ) = 0$

Instantaneous power


$$\begin{aligned} P_{\text{inst}} &= V \cdot i \\ &= V_m \sin \omega t \cdot I_m \cos \omega t \\ &= V_m I_m \sin \omega t \cdot \cos \omega t \end{aligned}$$

$$P_{\text{inst}} = \frac{V_m I_m}{2} \sin 2\omega t$$

$$\begin{aligned} \text{Average power} = P_{\text{av}} &= \frac{1}{2\pi} \int_0^{2\pi} P_{\text{inst.}} dt \\ &= \frac{1}{2\pi} \int_0^{2\pi} \frac{V_m I_m}{2} \sin 2\omega t dt \\ &= \frac{V_m I_m}{8\pi} \left[-\cos 2\omega t \right]_0^{2\pi} \\ &= \frac{V_m I_m}{8\pi} \left[-\cos 4\pi + \cos 0 \right] = 0 \end{aligned}$$


So power consumed by pure capacitor is zero.

Series R-L circuit with AC input

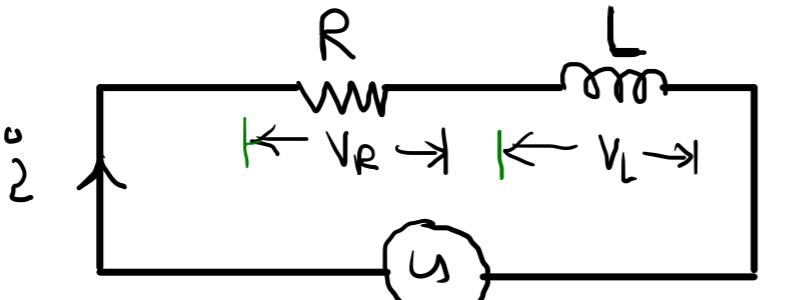


$$V = V_m \sin \omega t$$

Phasor diagram

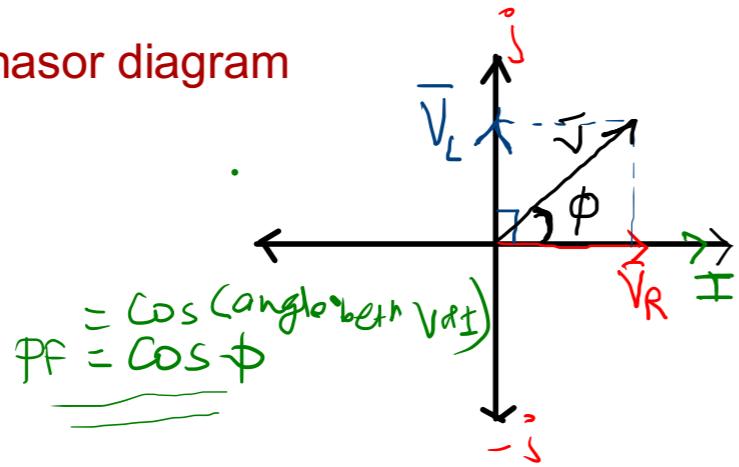


Impedance triangle

$$\begin{aligned} Z &= R + jX_L \\ |Z| &= \sqrt{R^2 + X_L^2} \\ \angle Z &= +\tan^{-1}\left(\frac{X_L}{R}\right) \\ \boxed{\phi = \angle Z = +\tan^{-1}\left(\frac{X_L}{R}\right)} \end{aligned}$$

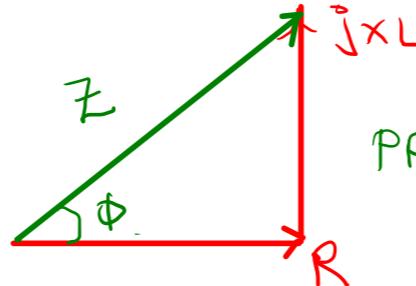

Voltage triangle

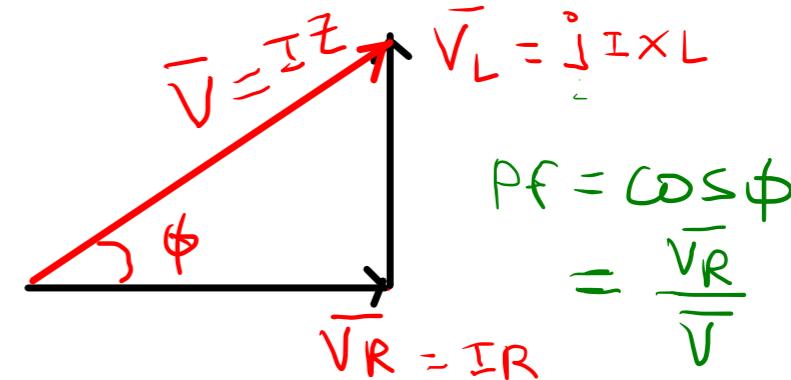


$$PF = \cos \phi = \frac{R}{Z} \text{ (lagging PF)}$$

Waveforms

$$v = V_m \sin \omega t$$

$$i = I_m \sin(\omega t - \phi)$$

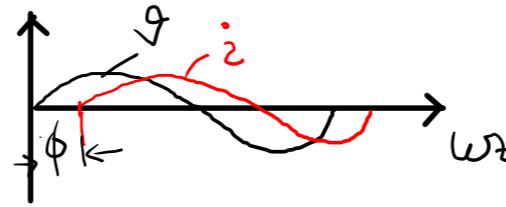

Instantaneous Power

$$P_{inst} = \underline{v} \times \dot{\underline{i}} = \underline{V_m \sin \omega t} \times \underline{I_m \sin (\omega t - \phi)} =$$

$$P_{inst} = \frac{V_m I_m}{2} [\cos(\omega t - \omega t + \phi) - \cos(\omega t + \omega t - \phi)]$$

$$P_{inst} = \frac{V_m I_m}{2} [\cos \phi - \cos(2\omega t - \phi)]$$

Average power

$$P_{av} = \frac{1}{2\pi} \int_0^{2\pi} \left[\frac{V_m I_m}{2} \cos \phi - \frac{V_m I_m}{2} \cos(2\omega t - \phi) \right] d\omega t$$

$$P_{av} = \frac{1}{2\pi} \left[\frac{V_m I_m}{2} \cos \phi [wt]_0^{2\pi} - \frac{V_m I_m}{2} \left[\frac{\sin(2\omega t - \phi)}{2} \right]_0^{2\pi} \right]$$

$$P_{av} = \frac{1}{2\pi} \left[\frac{V_m I_m}{2} \cos \phi (2\pi - 0) - \frac{V_m I_m}{4} [\sin(4\pi - \phi) - \sin(0 - \phi)] \right]$$

$$P_{av} = \frac{1}{2\pi} \left[\frac{V_m I_m}{2} \cos \phi \times 2\pi - \frac{V_m I_m}{4} (-\sin \phi + \sin \phi) \right]$$


$$P_{av} = \frac{V_m I_m}{2} \cos \phi \quad \text{So } \Rightarrow P_{av} = \frac{V_m}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}} \cos \phi = V_{rms} \cdot I_{rms} \cos \phi$$

Active power:

$$P_{av} = P_{active} = V I \cos \phi \text{ & unit is Watts}$$

Reactive power: Circulating power
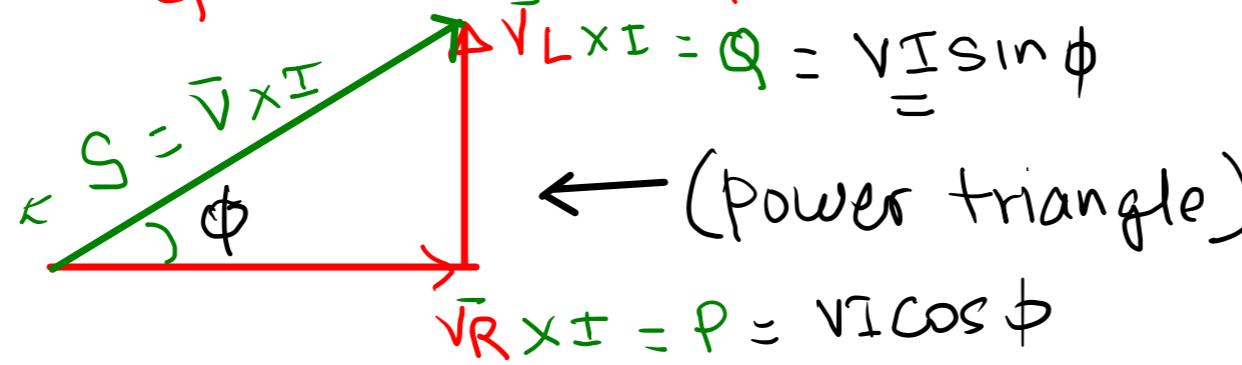
$$Q = V I \sin \phi \text{ & unit VAR (Volt-Ampere Reactive)}$$




Apparent Power (S)

$$S^2 = P^2 + Q^2$$


$$S = V \times I \text{ & unit is VA (Volt - Ampere)}$$

Series RC circuit with AC input

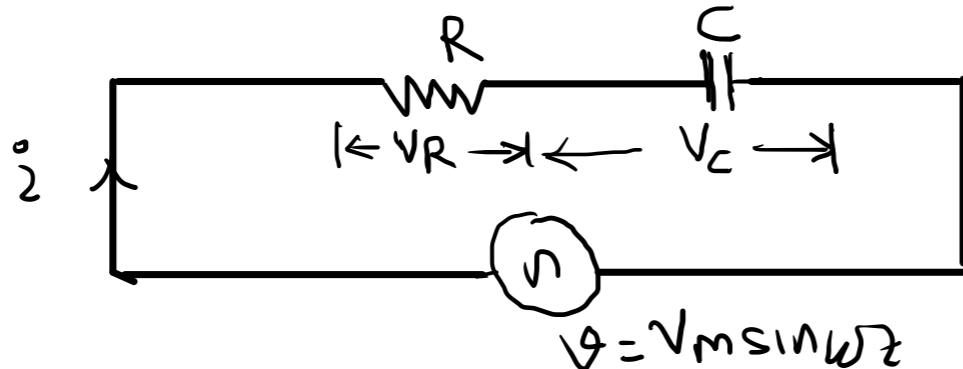


$$\bar{V} = \bar{V}_R + \bar{V}_C$$

⇒ phasor Diagram

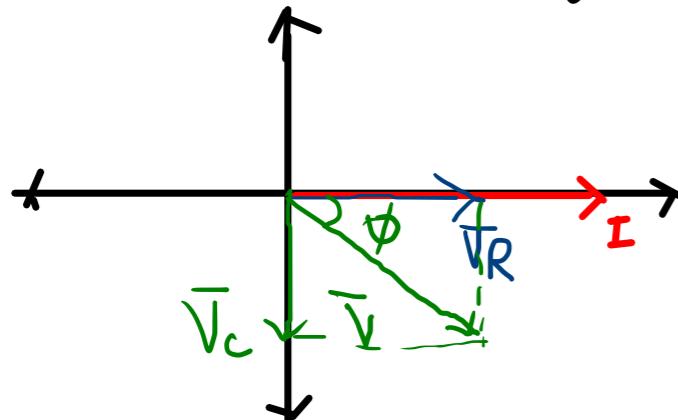


Leading PF because current leads the voltage.

⇒ Voltage triangle

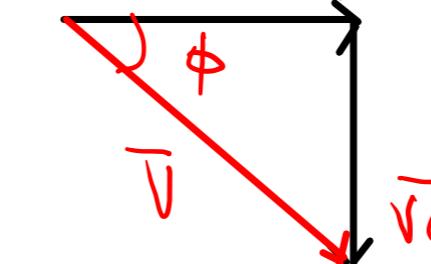

⇒ Impedance triangle

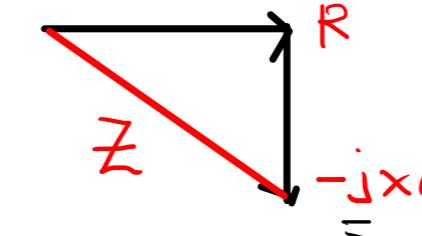

$$\begin{aligned}\bar{V} &= \bar{V}_R + \bar{V}_C \\ &= \bar{I} \cdot R - j \bar{I} \cdot X_c\end{aligned}$$

$$\frac{\bar{V}}{\bar{I}} = R - j X_c = Z$$

Instantaneous Power ; $P_{inst} = V \times I$

$$= V_m \sin \omega t \times I_m \sin(\omega t + \phi)$$

$$P_{inst} = V_m I_m \sin \omega t \cdot \sin(\omega t + \phi)$$

$$P_{inst} = \frac{V_m I_m}{2} [\cos \phi - \cos(2\omega t + \phi)]$$


Average Power

$$P_{av} = \frac{1}{2\pi} \int_0^{2\pi} P_{inst} d\omega t = \frac{V_m I_m}{2} \cos \phi = V_{rms} I_{rms} \cos \phi$$


$$P_{av} = P_{active} = V I \cos \phi \text{ (watts)}$$

Reactive power $\Rightarrow Q = V I \sin \phi \text{ (VAR)}$

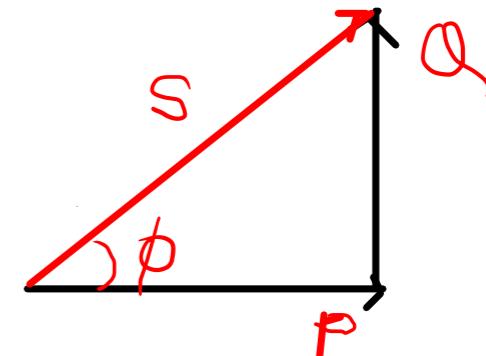Apparent power $\Rightarrow S = V I = \sqrt{P^2 + Q^2} \text{ (VA)}$



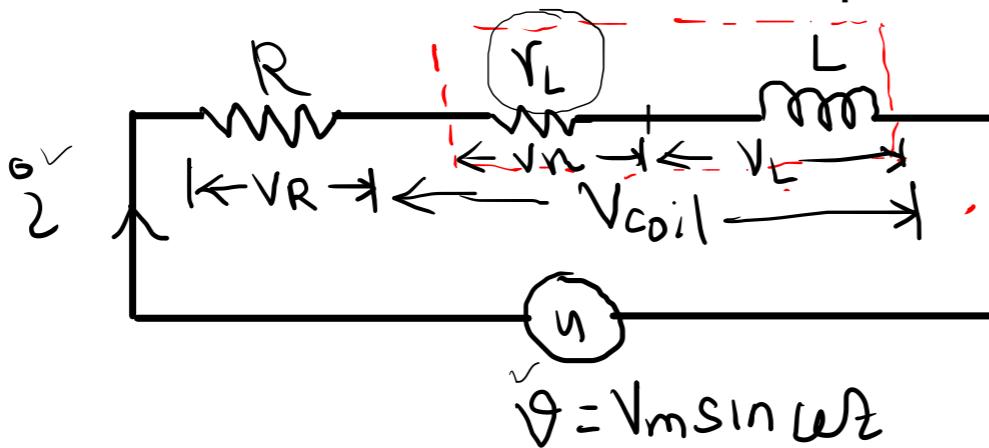
R-L series circuit with AC input where inductor is Impure




$$\bar{V} = \bar{V}_R + \bar{V}_{\text{Coil}} - \dots \quad (1)$$

$$\bar{V}_{\text{Coil}} = \bar{V}_{rL} + \bar{V}_L$$

⇒ phasor diagram.

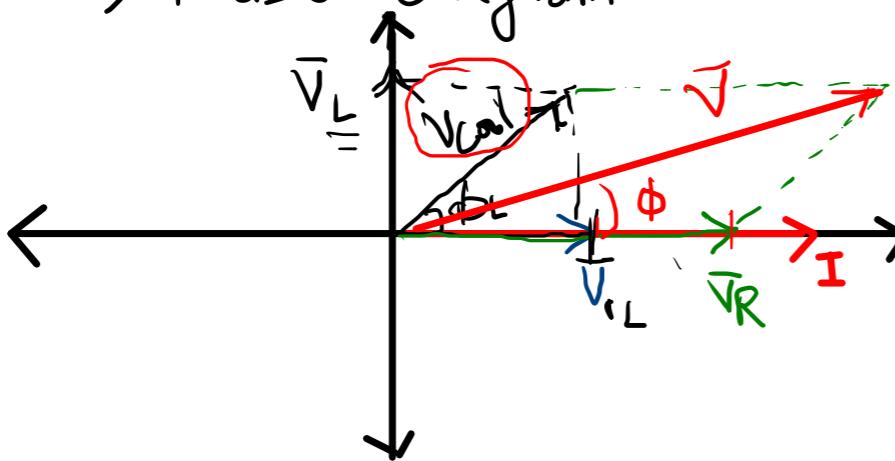


⇒ Voltage triangle

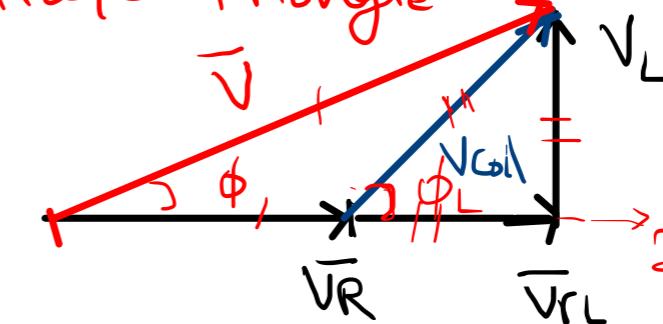

⇒ Impedance triangle

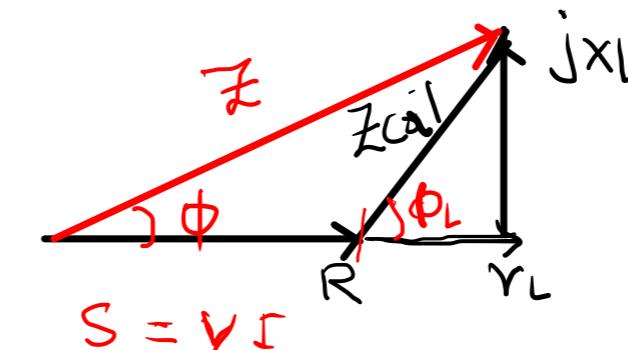
$$P = VI \cos \phi \quad Q = VI \sin \phi$$



$$Z = R + Z_{\text{Coil}}$$

$$Z = (R + r_L) + j X_L$$

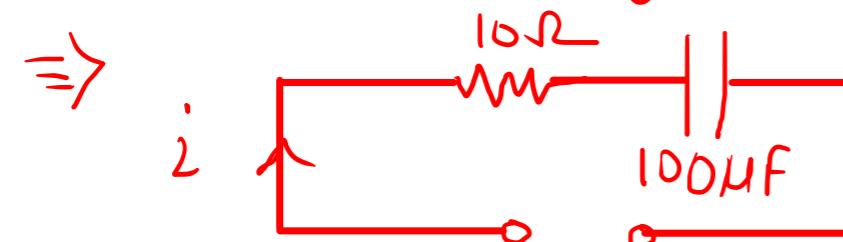Example ① \Rightarrow A capacitor which has an internal resistance of 10Ω & capacitance value of $100\mu F$ is connected to ac voltage $V(t) = 100\sin(314t)$. Calculate current flowing through the circuit & construct voltage triangle.




$$Z = R - jX_C$$

$$Z = 10 - jX_C$$

$$Z = (10 - j31.8)$$

$$\boxed{Z = 33.38 \angle -72.5^\circ}$$
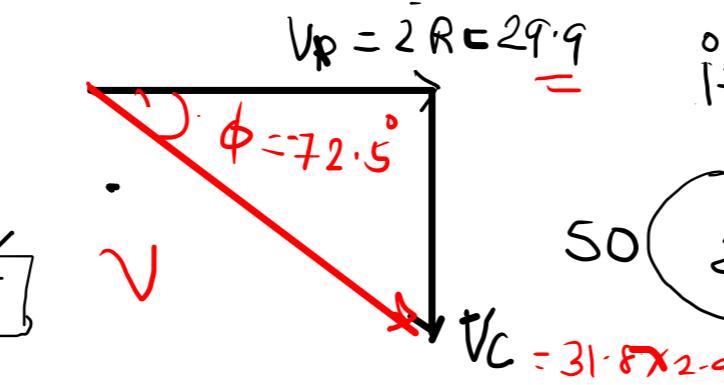
$$PF = \cos \phi = \cos 72.5^\circ = 0.299 \text{ (Leading)}$$



$$X_C = \frac{1}{2\pi f C} = \frac{1}{\omega C}$$

$$\omega = 314 \quad \therefore X_C = \frac{1}{314 \times 100 \times 10^{-6}}$$

$$X_C = 31.8 \Omega$$

$$i = \frac{V}{Z} = \frac{100}{(10 - j31.8)} = \frac{100}{33.38 \angle -72.5^\circ}$$


$$\text{So } i = 2.99 \angle 72.5^\circ \quad [0.899 + j2.81]$$

$$|i| = \sqrt{(0.899)^2 + (2.81)^2}$$

$$\angle i = \tan^{-1}\left(\frac{2.81}{0.899}\right)$$

$$|V| = |VR + VC| = \sqrt{(29.9)^2 + (95.4)^2} \leq 100V$$

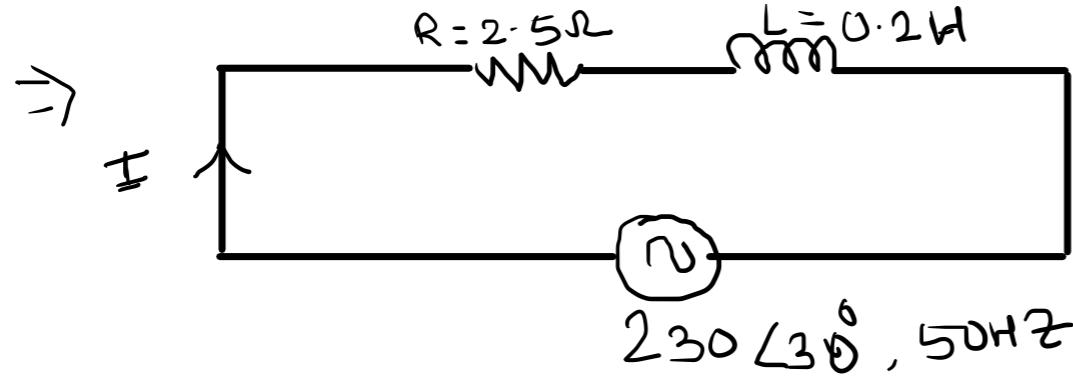3). A R-L series circuit is connected across $230\angle 30^\circ$, 50Hz supply. The value of R is 2.5 ohms and inductor $L=0.2$ H. Find current flowing through the circuit and power factor of the circuit.



$$I = \frac{V}{Z} = \frac{230\angle 30^\circ}{Z}$$

$$Z = R + jX_L$$

$$\text{Here } X_L = \omega L = 2\pi f L$$

$$X_L = 2\pi \times 50 \times 0.2$$

$$X_L = 62.8\Omega$$


$$Z = (2.5 + j62.8)$$

$$Z = 62.87 \angle 87.72^\circ$$

$$I = \frac{230\angle 30^\circ}{62.87 \angle 87.72^\circ} \quad \phi = 87.72^\circ$$

$$I = 3.65 \angle -57.72^\circ$$
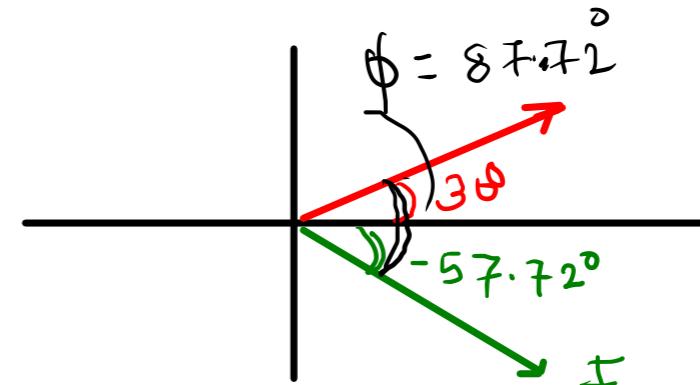
$$\text{PF} = \cos \phi = \cos 87.72^\circ = 0.039 \text{ (lagging)}$$



Example ② In a series circuit containing a pure resistance and a pure inductor. The current & voltage are given as

$$i(t) = 5 \sin(314t + \frac{2\pi}{3}) \text{ & } V(t) = 15 \sin(314t + \frac{5\pi}{6})$$

Find ① Impedance of the circuit ② Value of resistance

③ Value of inductor ④ Active power ⑤ Power factor.


\Rightarrow



$V(t)$


$$\bar{I} = \frac{5}{\sqrt{2}} \angle \frac{2\pi}{3} = \frac{5}{\sqrt{2}} \angle 120^\circ$$
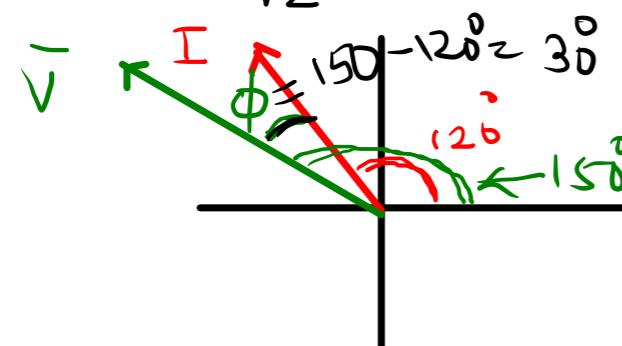
$$\bar{V} = \frac{15}{\sqrt{2}} \angle \frac{5\pi}{6} = \frac{15}{\sqrt{2}} \angle 150^\circ$$



$$\text{So } \phi = 150^\circ - 120^\circ = 30^\circ$$
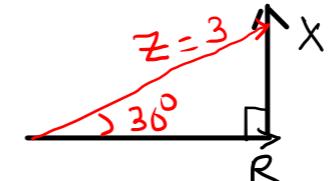
$$\textcircled{1} \quad Z = \frac{V}{I} = \frac{15\sqrt{2} \angle 150^\circ}{5\sqrt{2} \angle 120^\circ} = 3 \angle 30^\circ$$



$$\textcircled{2} \quad R = Z \cos \phi \quad \begin{cases} X_L = Z \sin \phi \\ R = 3 \cos 30^\circ \\ X_L = 3 \sin 30^\circ \\ R = 2.6 \Omega \\ X_L = 1.5 \Omega \end{cases}$$


$$X_L = \omega L \quad \therefore L = \frac{X_L}{\omega} = \frac{1.5}{314} = 4.78 \text{ mH}$$

$$\textcircled{3} \quad \text{Power factor} = \cos \phi = \cos 30^\circ = 0.866 \text{ (lagging)}$$

$$\textcircled{4} \quad \text{ACTIVE POWER} = V I \cos \phi = \frac{15}{\sqrt{2}} \times \frac{5}{\sqrt{2}} \cos 30^\circ$$

$$P = I^2 R = 32.5 \text{ W}$$

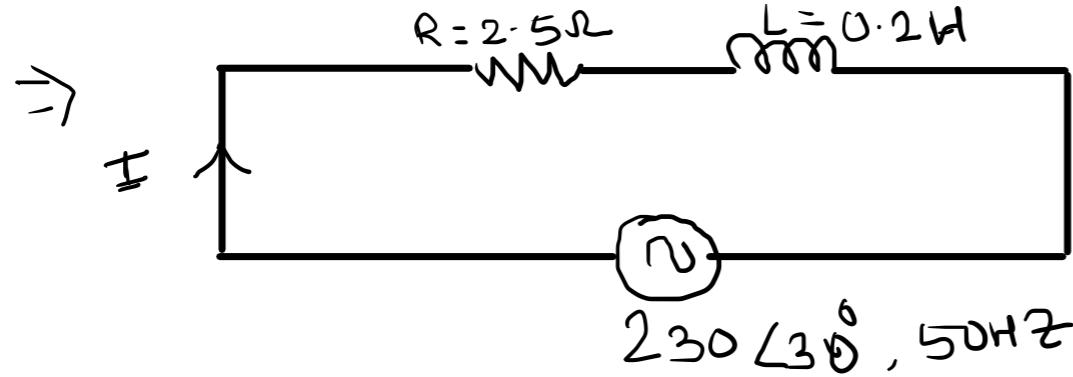3). A R-L series circuit is connected across $230 \angle 30^\circ$, 50Hz supply. The value of R is 2.5 ohms and inductor $L=0.2$ H. Find current flowing through the circuit and power factor of the circuit.



$$I = \frac{V}{Z} = \frac{230 \angle 30^\circ}{Z}$$

$$Z = R + jX_L$$

$$\text{Here } X_L = \omega L = 2\pi f L$$

$$X_L = 2\pi \times 50 \times 0.2$$

$$X_L = 62.8\Omega$$


$$Z = (2.5 + j62.8)$$

$$Z = 62.87 \angle 87.72^\circ$$

$$I = \frac{230 \angle 30^\circ}{62.87 \angle 87.72^\circ} \quad \phi = 87.72^\circ$$

$$I = 3.65 \angle -57.72^\circ$$
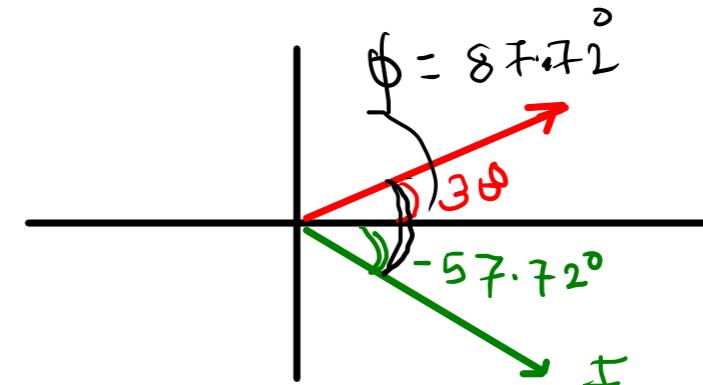
$$\text{PF} = \cos \phi = \cos 87.72^\circ = 0.039 \text{ (lagging)}$$



4). Two elements series circuit is connected across ac source $e = 200\sqrt{2} \sin(341t + 20^\circ)$. The current flowing in the circuit is found to be $10\sqrt{2} \cos(314t - 25^\circ)$. Determine the parameters of the circuit.


$$\Rightarrow E = \frac{200\sqrt{2}}{\sqrt{2}} \angle 20^\circ \quad i = 10\sqrt{2} \cos(314t - 25^\circ) = 10\sqrt{2} \sin(314t - 25 + 90^\circ) \\ = 10\sqrt{2} \sin(314t + 65^\circ)$$

$$I = \frac{10\sqrt{2}}{\sqrt{2}} \angle 65^\circ$$

$$Z = \frac{E}{I} = \frac{200 \angle 20^\circ}{10 \angle 65^\circ}$$

$$Z = 20 \angle -45^\circ \quad \phi = -45^\circ$$

$$PF = \cos \phi = \cos 45^\circ =$$

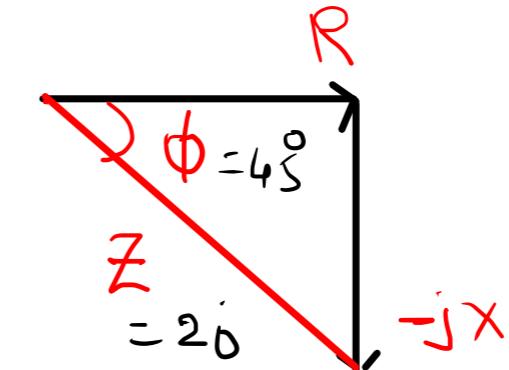

$$\cos \phi = \frac{R}{Z}$$

$$\sin \phi = \frac{X_c}{Z}$$


$$R = Z \cos \phi = 20 \cos 45^\circ = 14.14 \Omega$$

$$X_c = Z \sin \phi = 20 \sin 45^\circ = 14.14 \Omega$$

$$X_c = \frac{1}{\omega C} \quad C = \frac{1}{\omega X_c} = \frac{1}{314 \times 14.14}$$

$$C = 225.4 \mu F$$

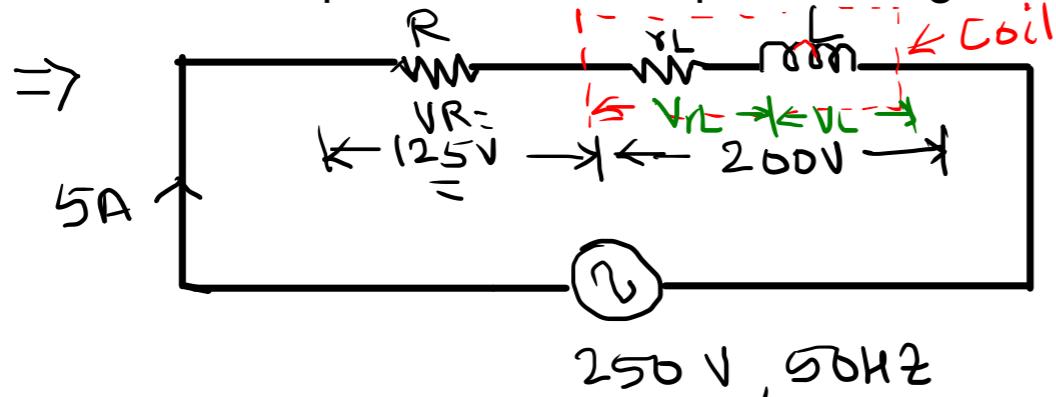5). A current of 5A flows through a non-inductive resistance in series with a choking coil when supplied at 250 V, 50Hz. If the voltage across the non-inductive resistance is 125 V and that of the coil 200 V. Calculate the impedance, reactance and resistance of the coil, power absorbed by the coil and total power. Draw the phasor diagram.



$$\Rightarrow Z_{\text{coil}} = \frac{200}{5} = 40 \Omega$$

$$\Rightarrow \text{Voltage triangle } \bar{V}_{\text{coil}} = \bar{V}_L + \bar{V}_R, \bar{V} = \bar{V}_R + \bar{V}_{\text{coil}}$$

Voltage triangle diagram showing $V = 250V$, $VR = 125V$, $VL = 200V$, and the angle ϕ between VR and V .

$$\begin{aligned} \bar{V}_L^2 + \bar{V}_R^2 &= (200)^2 \quad \dots \textcircled{1} \\ (125 + \bar{V}_L)^2 + \bar{V}_L^2 &= (250)^2 \quad \dots \textcircled{2} \\ 125^2 + 2 \times 125 \times \bar{V}_L + \bar{V}_L^2 + \bar{V}_L^2 &= (250)^2 \end{aligned}$$

$$(125^2 + 250 \bar{V}_L + 200^2) = (250)^2$$

$$R = 125 / 5 = 25 \Omega$$

$$Y_L = ? \quad X_L = ?, \quad Z_{\text{coil}} = ?$$

$$P_{\text{coil}} = ? \quad P_{\text{total}} = ?$$

$$250 \bar{V}_L = (250)^2 - (200)^2 - (125)^2$$

$$\bar{V}_L = 27.5V \quad \therefore Y_L = \frac{\bar{V}_L}{5} = \frac{27.5}{5} = 5.5 \Omega$$

$$Y_L = 5.5 \Omega$$

$$(V_{\text{coil}})^2 = V_R^2 + V_L^2$$


$$V_L^2 = (200)^2 - (27.5)^2$$

$$V_L = 198.1V$$

$$X_L = \frac{V_L}{I} = \frac{198.1}{5} = 39.6 \Omega$$

$$\begin{aligned} P_{\text{coil}} &= V_{\text{coil}} \times I \cos \phi_L = I \times Z_{\text{coil}} \times I \times \frac{Y_L}{Z_{\text{coil}}} \\ &= I^2 Y_L = 5^2 \times 5.5 = 137.5W \\ P_T &= I^2 (R + Y_L) = 25 \times (25 + 5.5) = 762.5W \end{aligned}$$

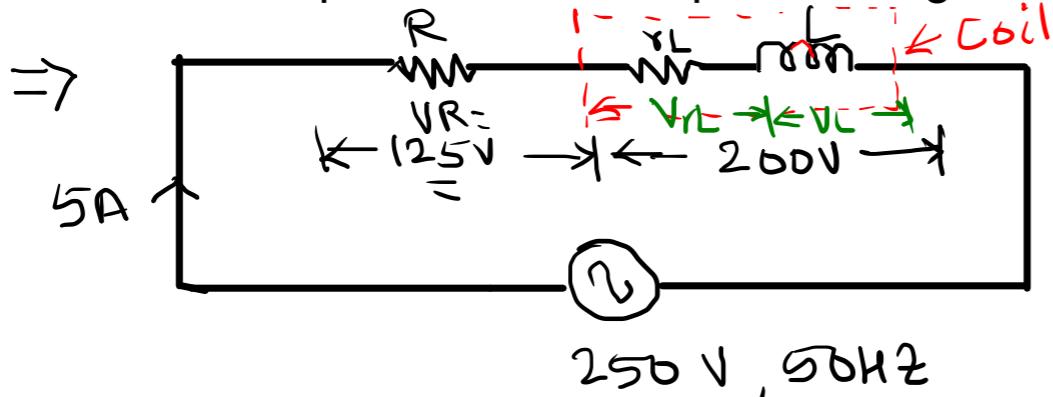5). A current of 5A flows through a non-inductive resistance in series with a choking coil when supplied at 250 V, 50Hz. If the voltage across the non-inductive resistance is 125 V and that of the coil 200 V. Calculate the impedance, reactance and resistance of the coil, power absorbed by the coil and total power. Draw the phasor diagram.



$$\Rightarrow Z_{\text{coil}} = \frac{200}{5} = 40 \Omega$$

$$\Rightarrow \text{Voltage triangle } \bar{V}_{\text{coil}} = \sqrt{\bar{V}_L + \bar{V}_R}, \bar{V} = \sqrt{\bar{V}_R + \bar{V}_{\text{coil}}}$$

Voltage triangle diagram showing $V = 250V$, $VR = 125V$, $VL = 200V$, and the angle ϕ between VR and V .

$$\sqrt{V_L^2 + V_R^2} = (200)^2 \quad \dots \textcircled{1}$$

$$(125 + V_L)^2 + V_L^2 = (250)^2 \quad \dots \textcircled{2}$$

$$125^2 + 2 \times 125 \times V_L + V_L^2 + V_L^2 = (250)^2$$

$$(125^2 + 250V_L + 200^2) = (250)^2$$

$$R = 125/5 = 25 \Omega$$

$$V_L = ? \quad X_L = ?, \quad Z_{\text{coil}} = ?$$

$$P_{\text{coil}} = ? \quad P_{\text{total}} = ?$$

$$250^2 = (250)^2 - (200)^2 - (125)^2$$

$$V_L = 27.5V \quad \therefore R_L = \frac{V_L}{I} = \frac{27.5}{5} = 5.5 \Omega$$

$$R_L = 5.5 \Omega$$

$$(V_{\text{coil}})^2 = V_L^2 + V_R^2$$

$$V_L^2 = (200)^2 - (27.5)^2$$


$$V_L = 198.1V$$

$$X_L = \frac{V_L}{I} = \frac{198.1}{5} = 39.6 \Omega$$

$$P_{\text{coil}} = V_{\text{coil}} \times I \cos \phi_L = I \times Z_{\text{coil}} \times I \times \frac{V_L}{Z_{\text{coil}}} = I^2 V_L = 5^2 \times 5.5 = 137.5W$$

$$P_T = I^2 (R + X_L) = 25 \times (25 + 5.5) = 762.5W$$

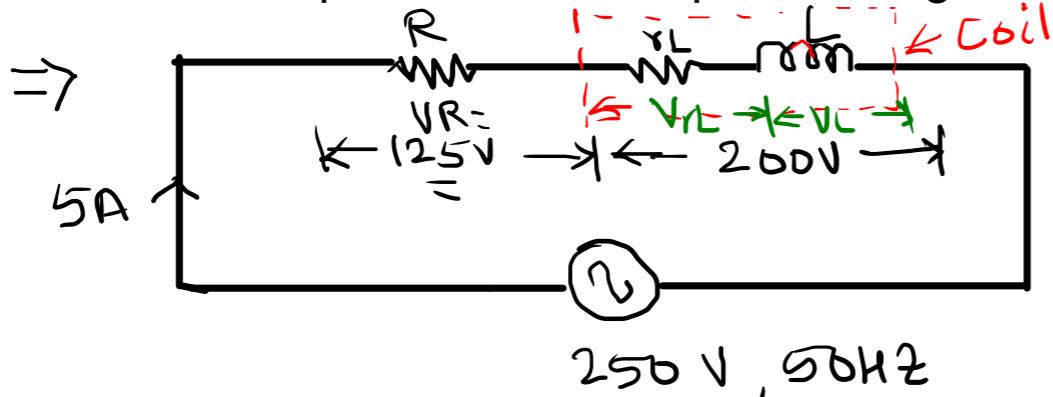5). A current of 5A flows through a non-inductive resistance in series with a choking coil when supplied at 250 V, 50Hz. If the voltage across the non-inductive resistance is 125 V and that of the coil 200 V. Calculate the impedance, reactance and resistance of the coil, power absorbed by the coil and total power. Draw the phasor diagram.



$$\Rightarrow Z_{\text{coil}} = \frac{200}{5} = 40 \Omega$$

$$\Rightarrow \text{Voltage triangle } \bar{V}_{\text{coil}} = \bar{V}_L + \bar{V}_R, \bar{V} = \bar{V}_R + \bar{V}_{\text{coil}}$$

Voltage triangle diagram showing $V = 250V$, $VR = 125V$, $VL = 200V$, and the angle ϕ between VR and V .

$$\bar{V}_L^2 + \bar{V}_R^2 = (200)^2 \quad \dots \textcircled{1}$$

$$(125 + \bar{V}_L)^2 + \bar{V}_L^2 = (250)^2 \quad \dots \textcircled{2}$$

$$125^2 + 2 \times 125 \times \bar{V}_L + \bar{V}_L^2 + \bar{V}_L^2 = (250)^2$$

$$(125^2 + 250\bar{V}_L + 200^2) = (250)^2$$

$$R = 125 / 5 = 25 \Omega$$

$$Y_L = ? \quad X_L = ?, \quad Z_{\text{coil}} = ?$$

$$P_{\text{coil}} = ? \quad P_{\text{total}} = ?$$

$$250^2 = (250)^2 - (200)^2 - (125)^2$$

$$V_R = 27.5V \quad \therefore Y_L = \frac{V_R}{5} = \frac{27.5}{5} = 5.5 \Omega$$

$$Y_L = 5.5 \Omega$$

$$(V_{\text{coil}})^2 = V_R^2 + V_L^2$$

$$V_L^2 = (200)^2 - (27.5)^2$$


$$V_L = 198.1V$$

$$X_L = \frac{V_L}{I} = \frac{198.1}{5} = 39.6 \Omega$$

$$P_{\text{coil}} = V_{\text{coil}} \times I \cos \phi_L = I \times Z_{\text{coil}} \times I \frac{Y_L}{Z_{\text{coil}}} = I^2 Y_L = 5^2 \times 5.5 = 137.5W$$

$$P_T = I^2 (R + Y_L) = 25 \times (25 + 5.5) = 762.5W$$

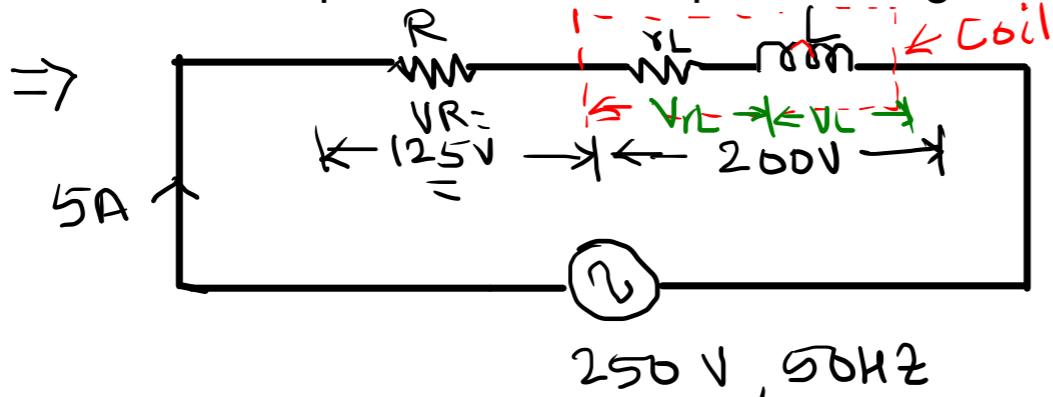5). A current of 5A flows through a non-inductive resistance in series with a choking coil when supplied at 250 V, 50Hz. If the voltage across the non-inductive resistance is 125 V and that of the coil 200 V. Calculate the impedance, reactance and resistance of the coil, power absorbed by the coil and total power. Draw the phasor diagram.



$$\Rightarrow Z_{\text{coil}} = \frac{200}{5} = 40 \Omega$$

$$\Rightarrow \text{Voltage triangle } \bar{V}_{\text{coil}} = \bar{V}_L + \bar{V}_R, \bar{V} = \bar{V}_R + \bar{V}_{\text{coil}}$$

Voltage triangle diagram showing $V = 250V$, $VR = 125V$, $VL = 200V$, and the angle ϕ between VR and V .

$$\bar{V}_L^2 + \bar{V}_R^2 = (200)^2 \quad \dots \textcircled{1}$$

$$(125 + \bar{V}_L)^2 + \bar{V}_L^2 = (250)^2 \quad \dots \textcircled{2}$$

$$125^2 + 2 \times 125 \times \bar{V}_L + \bar{V}_L^2 + \bar{V}_L^2 = (250)^2$$

$$(125^2 + 250\bar{V}_L + 200^2) = (250)^2$$

$$R = 125 / 5 = 25 \Omega$$

$$Y_L = ? \quad X_L = ?, \quad Z_{\text{coil}} = ?$$

$$P_{\text{coil}} = ? \quad P_{\text{total}} = ?$$

$$250^2 = (250)^2 - (200)^2 - (125)^2$$

$$V_R = 27.5V \quad \therefore Y_L = \frac{V_R}{5} = \frac{27.5}{5} = 5.5 \Omega$$

$$Y_L = 5.5 \Omega$$

$$(V_{\text{coil}})^2 = V_R^2 + V_L^2$$

$$V_L^2 = (200)^2 - (27.5)^2$$


$$V_L = 198.1V$$

$$X_L = \frac{V_L}{I} = \frac{198.1}{5} = 39.6 \Omega$$

$$P_{\text{coil}} = V_{\text{coil}} \times I \cos \phi_L = I \times Z_{\text{coil}} \times I \frac{Y_L}{Z_{\text{coil}}} = I^2 Y_L = 5^2 \times 5.5 = 137.5W$$

$$P_T = I^2 (R + Y_L) = 25 \times (25 + 5.5) = 762.5W$$

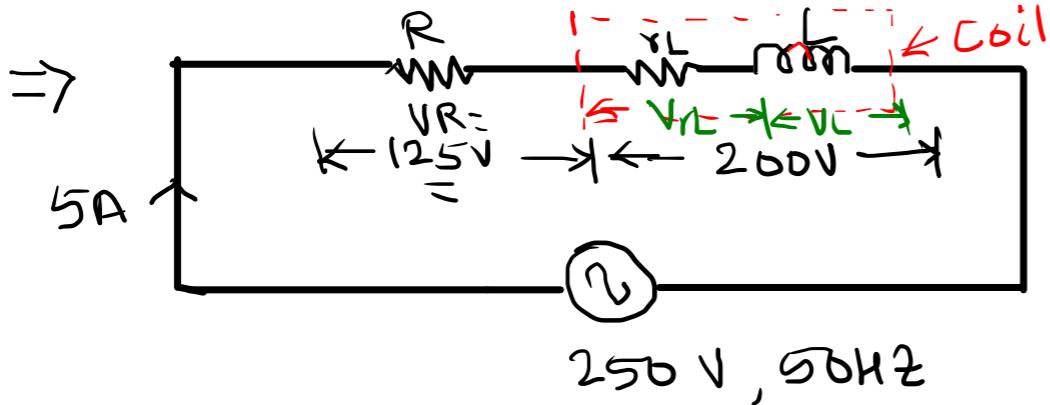5). A current of 5A flows through a non-inductive resistance in series with a choking coil when supplied at 250 V, 50Hz. If the voltage across the non-inductive resistance is 125 V and that of the coil 200 V. Calculate the impedance, reactance and resistance of the coil, power absorbed by the coil and total power. Draw the phasor diagram.



$$\Rightarrow Z_{\text{coil}} = \frac{200}{5} = 40 \Omega$$

$$\Rightarrow \text{Voltage triangle } \underline{V}_{\text{coil}} = \underline{V}_n + \underline{V}_L, \underline{V} = \underline{V}_R + \underline{V}_{\text{coil}}$$

Voltage triangle diagram showing $V = 250V$, $V_R = 125V$, $V_L = 200V$, and phase angle ϕ .

$$\begin{aligned} \underline{V}^2 &= \underline{V}_R^2 + \underline{V}_L^2 = (200)^2 \quad \dots \textcircled{1} \\ (125 + V_n)^2 + V_L^2 &= (250)^2 \quad \dots \textcircled{2} \\ 125^2 + 2 \times 125 \times V_n + V_n^2 + V_L^2 &= (250)^2 \\ (125^2 + 250V_n + 200^2) &= (250)^2 \end{aligned}$$

$$R = 125 / 5 = 25 \Omega$$

$$V_L = ? \quad X_L = ?, \quad Z_{\text{coil}} = ?$$

$$P_{\text{coil}} = ? \quad P_{\text{total}} = ?$$

$$250 V_L = (250)^2 - (200)^2 - (125)^2$$

$$V_n = 27.5V \quad \therefore V_L = \frac{V_n}{5} = \frac{27.5}{5} = 5.5 \Omega$$

$$\boxed{V_L = 5.5 \Omega}$$

$$(V_{\text{coil}})^2 = V_n^2 + V_L^2$$

$$V_L^2 = (200)^2 - (27.5)^2$$


$$V_L = 198.1V$$

$$X_L = \frac{V_L}{I} = \frac{198.1}{5} = 39.62 \Omega$$


$$\begin{aligned} P_{\text{coil}} &= V_{\text{coil}} \times I \cos \phi_L = I \times Z_{\text{coil}} \times I \frac{V_L}{Z_{\text{coil}}} \\ &= I^2 V_L = 5^2 \times 5.5 = 137.5W \end{aligned}$$

$$P_t = I^2 (R + V_L) = 25 \times (25 + 5.5) = 762.5W$$

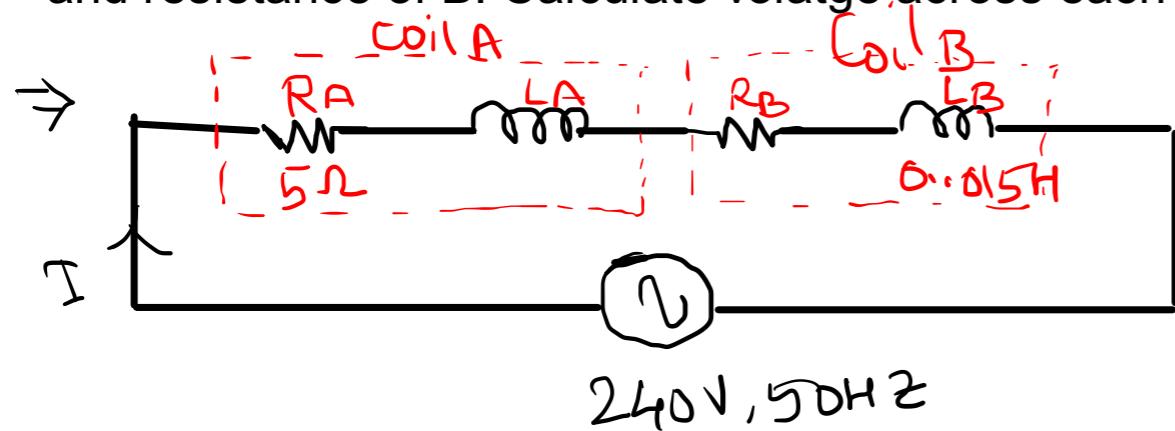6. Two coils A and B are connected in series across a 240 V, 50 Hz supply. The resistance of A is 5Ω and inductance of B is 0.015 H. If the input from the supply is 3kWatts and 2kVAr. Find inductance of A and resistance of B. Calculate voltage across each coil.



⇒ Power triangle

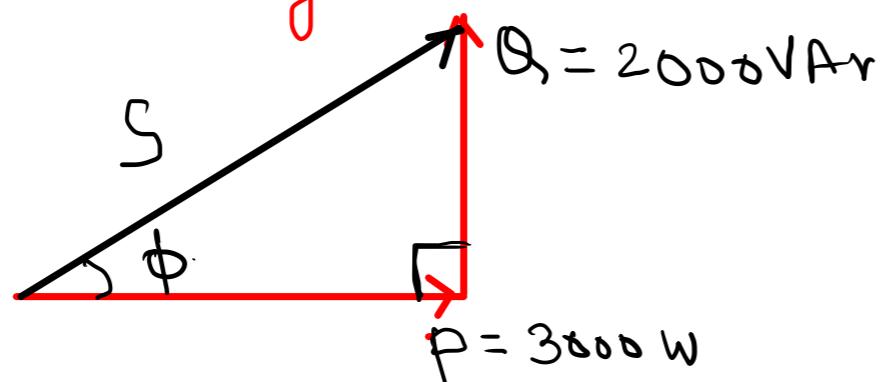

$$\cos\phi = \frac{P}{S}$$

$$S^2 = P^2 + Q^2 = (3000)^2 + (2000)^2$$

$$P = \text{Active power} = 3 \text{ kW}$$

$$Q = \text{Reactive power} = 2 \text{ kVAr}$$

$$S = 3605.5 \text{ VA} \quad \left| \cos\phi = \frac{3000}{3605.5} = 0.83 \text{ (say)} \right.$$

$$\phi = 33.7^\circ$$

$$S = V \times I \quad I = \frac{S}{V} = \frac{3605.5}{240}$$


$$I = 15.02 \text{ A}$$

$$|Z| = \frac{V}{I} = \frac{240}{15.02} = 15.98 \Omega$$


$$Z = 15.98 \angle 33.7^\circ$$

$$Z = Z_A + Z_B = R_A + jX_A + R_B + jX_B$$

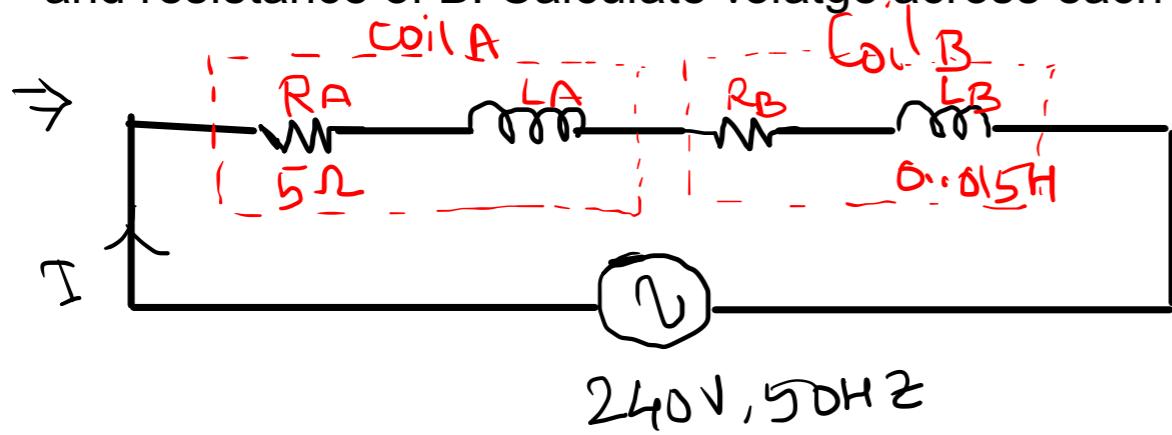6. Two coils A and B are connected in series across a 240 V, 50 Hz supply. The resistance of A is 5Ω and inductance of B is 0.015 H. If the input from the supply is 3kWatts and 2kVAr. Find inductance of A and resistance of B. Calculate voltage across each coil.



\Rightarrow Power triangle

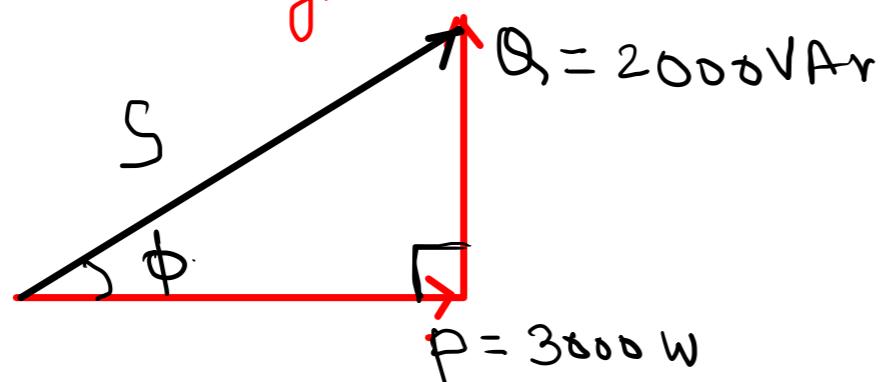

$$\cos \phi = \frac{P}{S}$$

$$S^2 = P^2 + Q^2 = (3000)^2 + (2000)^2$$

$$P = \text{Active power} = 3 \text{ kW}$$

$$Q = \text{Reactive power} = 2 \text{ kVAr}$$

$$S = 3605.5 \text{ VA} \quad \left| \cos \phi = \frac{3000}{3605.5} = 0.83 \text{ (say)} \right.$$

$$\phi = 33.7^\circ$$

$$S = V \times I \quad I = \frac{S}{V} = \frac{3605.5}{240}$$


$$I = 15.02 \text{ A}$$

$$|Z| = \frac{V}{I} = \frac{240}{15.02} = 15.98 \Omega$$

$$Z = 15.98 \angle 33.7^\circ$$

$$Z = Z_A + Z_B = R_A + jX_A + R_B + jX_B$$

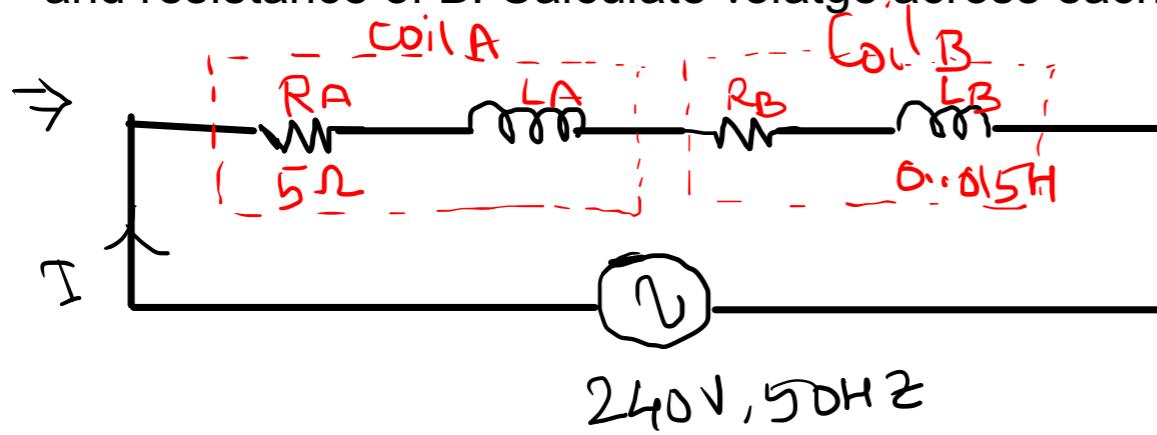6. Two coils A and B are connected in series across a 240 V, 50 Hz supply. The resistance of A is 5Ω and inductance of B is 0.015 H. If the input from the supply is 3kWatts and 2kVAr. Find inductance of A and resistance of B. Calculate voltage across each coil.



$$Z = (R_A + R_B) + j(X_A + X_B)$$

$$Z = 15.98 \angle 33.7^\circ$$

$$P = 3000 \text{ Watts}$$

$$P = I^2 R = I^2 (R_A + R_B)$$

$$R_A + R_B = \frac{P}{I^2} = \frac{3000}{(15.02)^2}$$

$$R_A + R_B = 13.29 \Omega$$

$$R_B = 13.29 - R_A = 13.29 - 5 = 8.3 \Omega$$

$$X_B = 2\pi f L_B = 2\pi \times 50 \times 0.015 = 4.7 \Omega$$

$$Z^2 = (R_A + R_B)^2 + (X_A + X_B)^2$$

$$(X_A + X_B) = Z \sin \phi$$

$$(15.98)^2 = (13.29)^2 + (X_A + X_B)^2$$

$$(X_A + X_B)^2 = (15.98)^2 - (13.29)^2 =$$

$$X_A + X_B = 8.86 \quad \therefore X_A = 4.16 \Omega$$

$$X_A = 2\pi f L_A \quad \therefore L_A = \frac{X_A}{2\pi f} = \frac{4.16}{2\pi \times 50}$$

$$L_A = 0.613 \text{ H}$$


$$V_A = I \times Z_A = 15.02(R_A + jX_A) = 15.02(5 + j4.16)$$

$$V_A = (97.6 \angle 33.7^\circ) \quad \leftarrow = 75.1 + j62.33$$

$$V_B = I \times Z_B = 15.02(R_B + jX_B) = 15.02(8.3 + j4.7)$$

$$V_B = 143.17 \angle 29.45^\circ$$

R-L-C series Circuit

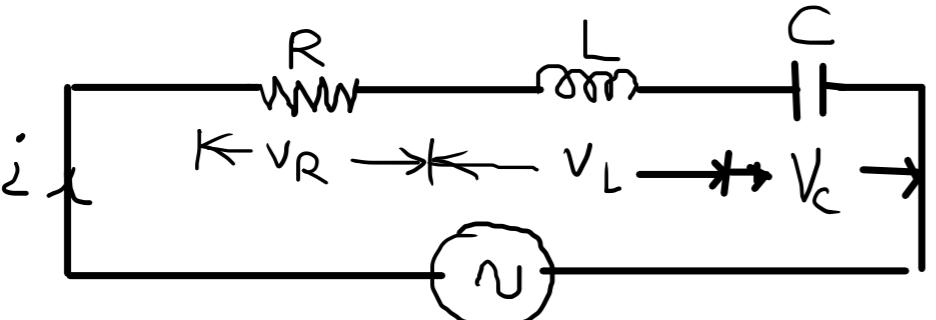


$$\theta = V_m \sin \omega t$$


\Rightarrow Case I $X_L > X_C$

$$V_L > V_C$$

\rightarrow Phasor diagram

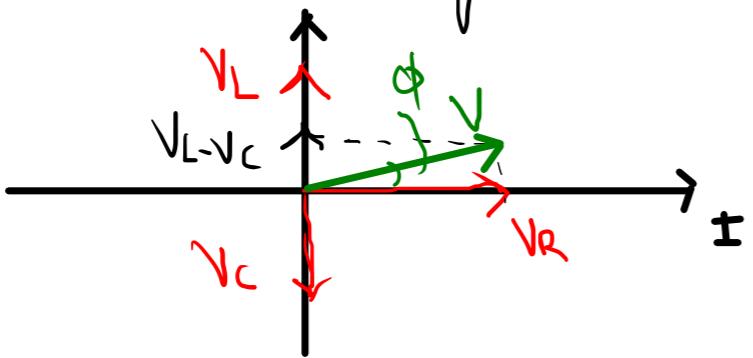

\rightarrow Impedance triangle

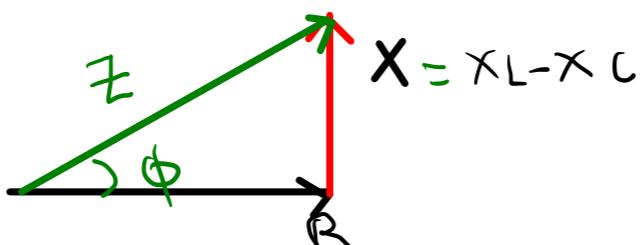


$$\bar{V} = \bar{V}_R + \bar{V}_L + \bar{V}_C$$


$$V_R = IR, V_L = X_L I, V_C = X_C I$$

$$Z = R + j(X_L - X_C) = R + jX$$


\rightarrow In wave forms.

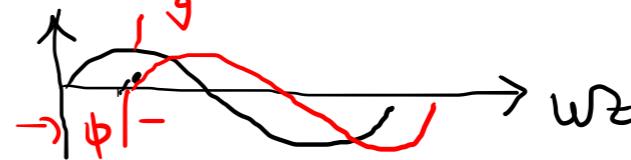

\rightarrow Voltage triangle

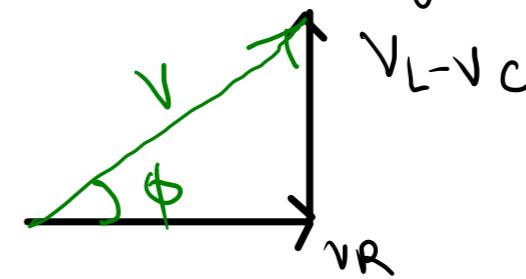


\rightarrow Power triangle

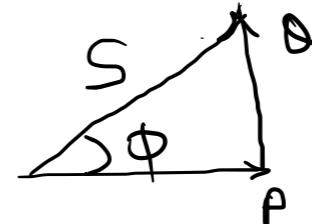

$$\text{Power factor} = \cos \phi = \frac{V_R}{V} = \frac{R}{Z} = \frac{P}{S}$$


R-L-C series Circuit

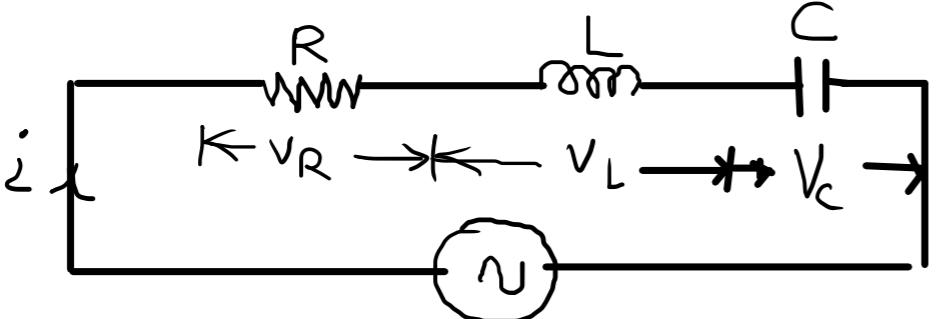


$$\theta = V_m \sin \omega t$$

\Rightarrow Case I $x_c > x_L$

\rightarrow Phasor diagram

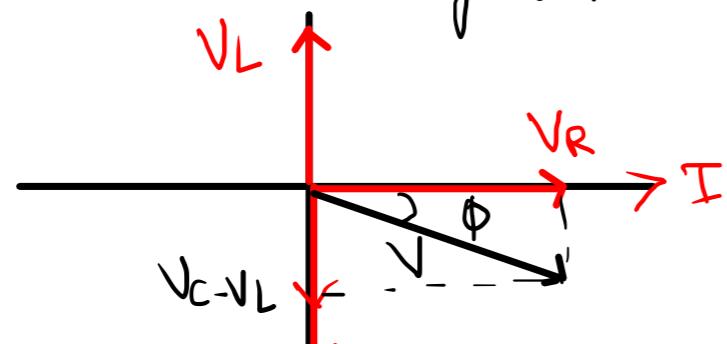


\rightarrow Impedance triangle

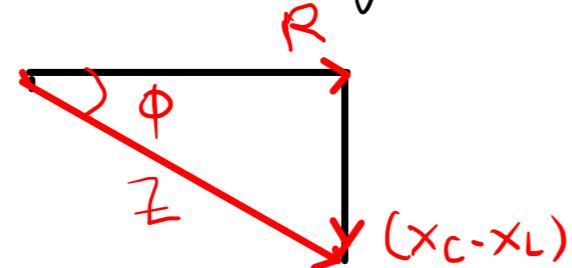


$$\bar{V} = \bar{V}_R + \bar{V}_L + \bar{V}_C$$

$$V_R = IR, \quad V_L = X_L \cdot I, \quad V_C = X_C \cdot I$$


\rightarrow In waveforms

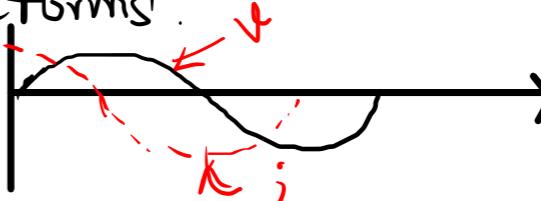

\rightarrow Voltage triangle

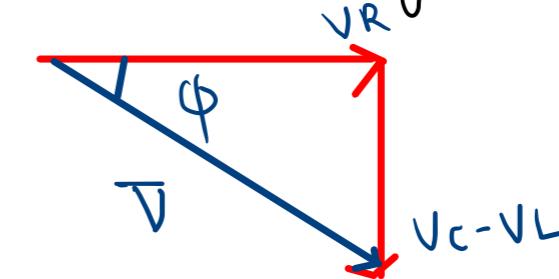


\rightarrow Power triangle

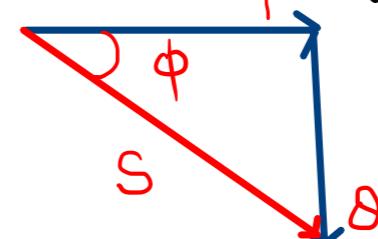

$$\text{Power factor} = \cos \phi = \frac{V_R}{V} = \frac{R}{Z} = \frac{P}{S}$$

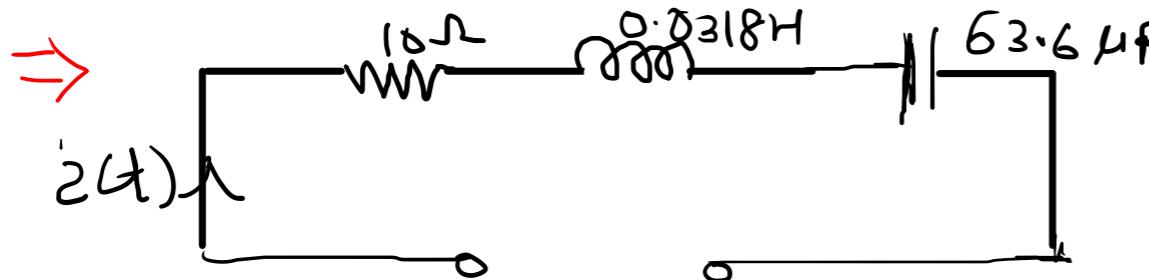7) A voltage $e(t) = 100\sin(314t)$ is applied to a series circuit consisting of 10 ohm resistance, a 0.0318 H inductor and 63.6 μ F capacitor. Calculate (i) expression for current (ii) Power factor (iii) Active power.



$$e(t) = 100\sin(314t)$$

$$I = \frac{E}{Z}$$

$$Z = R + j(X_L - X_C)$$

$$X_L = \omega L = 314 \times 0.0318 = 9.98 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{314 \times 63.6 \times 10^{-6}} = 50.07 \Omega$$

$$Z = 10 + j(9.98 - 50.07)$$

$$Z = 10 - j40.09$$

$$E = \frac{100}{\sqrt{2}} \angle 0^\circ$$

$$Z = 41.31 \angle -76^\circ$$

$$I = \frac{V}{Z} = \frac{(100/\sqrt{2}) \angle 0^\circ}{41.31 \angle -76^\circ}$$

$$I = 1.71 \angle 76^\circ$$

$$i(t) = I \times \sqrt{2} \sin(314t + 76^\circ)$$

$$= 1.71 \times \sqrt{2} \sin(314t + 76^\circ)$$


$$i(t) = 2.42 \sin(314t + 76^\circ)$$

$$\text{PF} = \cos \phi = \cos 76^\circ = 0.24 \text{ (leading)}$$

$$P = VI \cos \phi$$

$$= \frac{100}{\sqrt{2}} \times 1.71 \times 0.24 = 29.25 \text{ Watts}$$

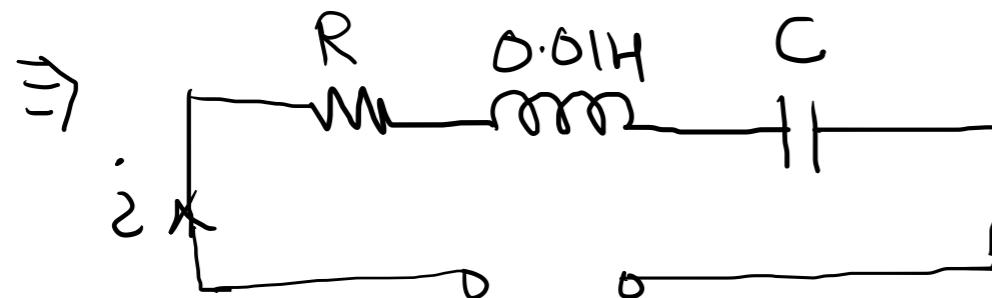8). A resistance R , an inductor $L = 0.01 \text{ H}$ and a capacitance C are connected in series when voltage $v = 400 \cos(3000t - 10^\circ)$ is applied to a series combination. If the current is $i = 10\sqrt{2} \cos(3000t - 55^\circ)$. Find R and C .



$$v = 400 \cos(3000t - 10^\circ)$$

$$i = 10\sqrt{2} \cos(3000t - 55^\circ)$$

$$v = 400 \sin(3000t - 10^\circ + 90^\circ)$$

$$v = 400 \sin(3000t + 80^\circ)$$

$$V = \frac{400}{\sqrt{2}} \angle 80^\circ$$

$$i = 10\sqrt{2} \sin(3000t - 55 + 90^\circ)$$

$$i = 10\sqrt{2} \sin(3000t + 35^\circ)$$


$$I = \frac{10\sqrt{2}}{\sqrt{2}} \angle 35^\circ$$

I lags V by $(\underline{\underline{E}}_0 - \underline{\underline{I}}_0) = 45^\circ$

$$\phi = 45^\circ$$

$$\text{PF} = \cos \phi = \cos 45^\circ = 0.707 \text{ (lagging)}$$
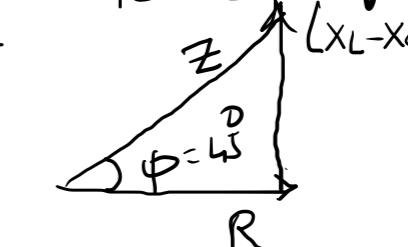
$$Z = \frac{V}{I} = \frac{\frac{400}{\sqrt{2}} \angle 80^\circ}{10 \angle 35^\circ} \quad \text{Impedance triangle}$$



$$Z = 28.28 \angle 45^\circ$$

$$R = Z \cos \phi = 28.28 \cos 45^\circ$$

$$R = 19.99 \Omega$$

$$(X_L - X_C) = Z \sin \phi = 28.28 \sin 45^\circ = 19.99 \Omega$$

$$X_L = \omega L = 3000 \times 0.01 = 30 \Omega$$

$$X_L - X_C = 19.99$$

$$-X_C = 19.99 - 30 = -10.01$$

$$C = 33.3 \mu F$$

$$\begin{cases} X_C = \frac{1}{\omega C} \\ C = \frac{1}{\omega \times X_C} \\ C = \frac{1}{3000 \times 10.01} \end{cases}$$

Concept Admittance (\bar{Y})

Admittance is Reciprocal of Impedance.

$$\bar{Y} = \frac{1}{Z} = \frac{1}{R \pm jX}$$

$$\bar{Y} = \frac{1}{R \pm jX} \times \frac{R \mp jX}{R \mp jX}$$

$$Y = \frac{R \mp jX}{R^2 + X^2}$$

$$Y = \frac{R}{R^2 + X^2} \mp j \frac{X}{R^2 + X^2}$$

$$Y = G \mp jB$$

↓ Conductance ↓ Susceptance
 (Ω) (Ω)
 (mho) (mho)
 Siemens Siemens Siemens

Admittance =
 $(\Omega^{-1})(\text{mho})$

For R-L circuit

$$Z = R \pm jX_L \quad Y = G - jB$$

for R-C circuit

$$Z = R - jX_C \quad Y = G + jB$$

Concept Admittance (\bar{Y})

Admittance is Reciprocal of Impedance.

$$\bar{Y} = \frac{1}{Z} = \frac{1}{R \pm jX}$$

$$\bar{Y} = \frac{1}{R \pm jX} \times \frac{R \mp jX}{R \mp jX}$$

$$Y = \frac{R \mp jX}{R^2 + X^2}$$

$$Y = \frac{R}{R^2 + X^2} \mp j \frac{X}{R^2 + X^2}$$

$$Y = G \mp jB$$

↓ Conductance ↓ Susceptance
 (S) (S)
 (mho) (mho)
 Siemens Siemens Siemens

Admittance =
 (S) (mho)

For R-L circuit

$$Z = R \pm jX_L \quad Y = G - jB$$

for R-C circuit

$$Z = R - jX_C \quad Y = G + jB$$

Concept Admittance (\bar{Y})

Admittance is Reciprocal of Impedance.

$$\bar{Y} = \frac{1}{Z} = \frac{1}{R \pm jX}$$

$$\bar{Y} = \frac{1}{R \pm jX} \times \frac{R \mp jX}{R \mp jX}$$

$$Y = \frac{R \mp jX}{R^2 + X^2}$$

$$Y = \frac{R}{R^2 + X^2} \mp j \frac{X}{R^2 + X^2}$$

$$Y = G \mp jB$$

↓ Conductance ↓ Susceptance
 (S) (S)
 (mho) (mho)
 Siemens Siemens Siemens

Admittance =
 (S) (mho)


For R-L circuit

$$Z = R \pm jX_L \quad Y = G - jB$$

for R-C circuit

$$Z = R - jX_C \quad Y = G + jB$$

R-L Parallel Circuit

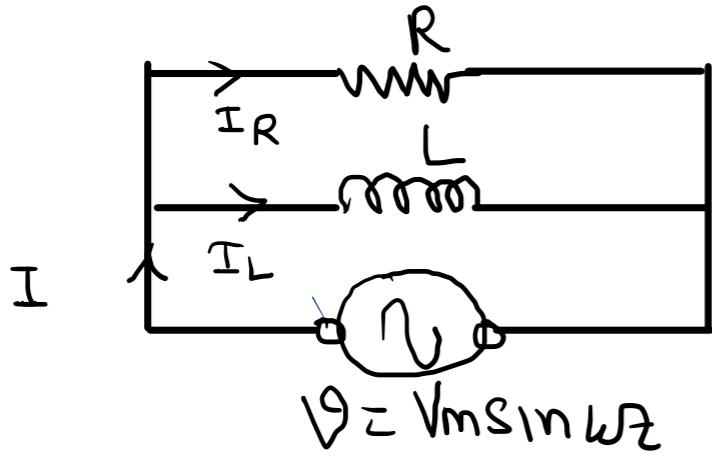

$$\bar{I} = \bar{I}_R + \bar{I}_L$$

$$\frac{1}{Z} = \frac{1}{R} + \frac{1}{jX_L}$$

$$Y_R = \frac{1}{R}$$

$$Y_L = \frac{1}{jX_L}$$


$$Y = Y_R - jY_L$$

$$Y = \frac{1}{R} - j\frac{1}{X_L}$$


⇒ phasor diagram

since voltage across R & L is same so take V as reference.

PF = $\cos \phi$ (lagging)

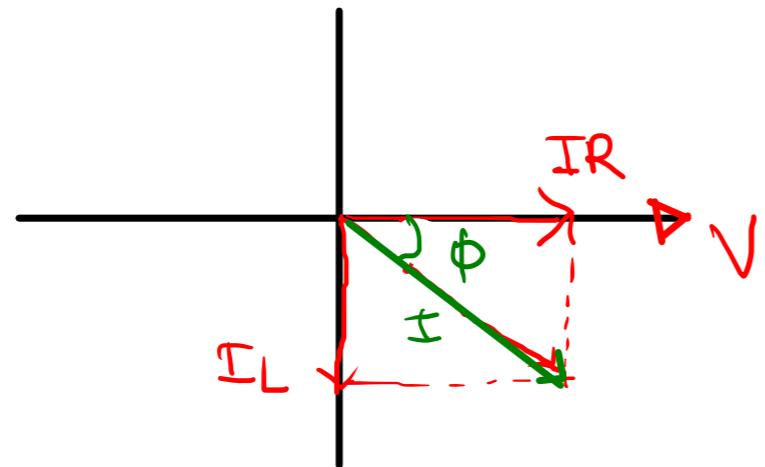

R-C Parallel Circuit

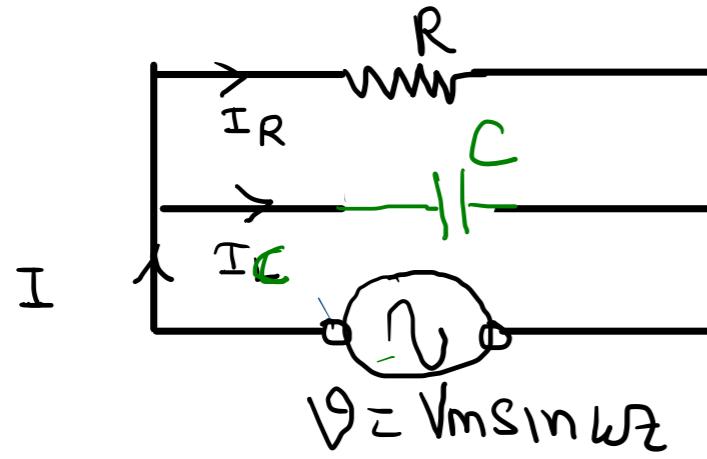

$$\bar{I} = \bar{I}_R + \bar{I}_C$$


$$Y_R = \frac{1}{R}$$

$$Y_C = \frac{1}{-j\omega C} = j\omega C$$


$$Y = Y_R + Y_C = \frac{1}{R} + j\omega C$$

$$PF = \cos \phi \text{ (leading)}$$

⇒ phasor diagram


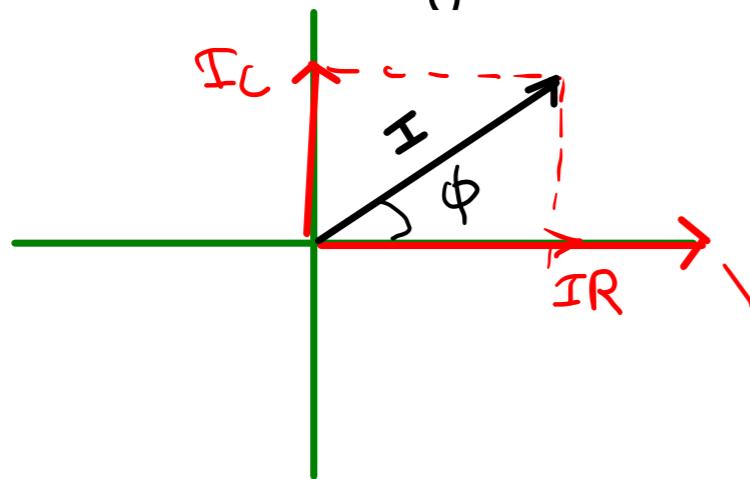


R-L-C Parallel Circuit

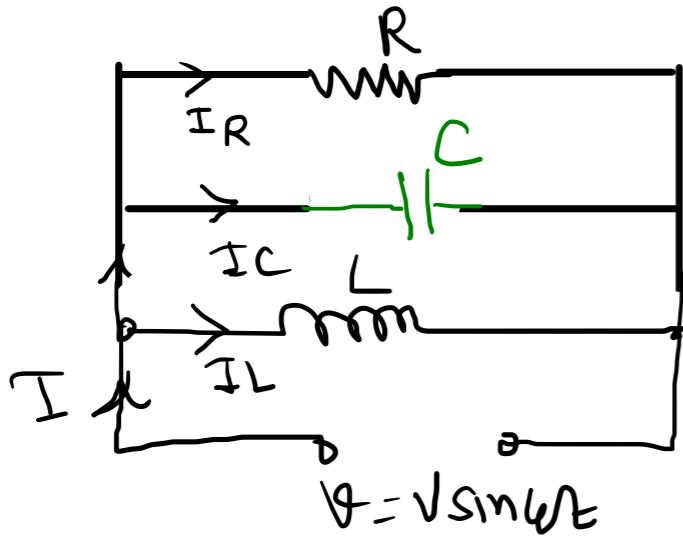


\Rightarrow phasor diagram ($I_C > I_L$)

\Rightarrow phasor diagram ($I_L > I_C$)

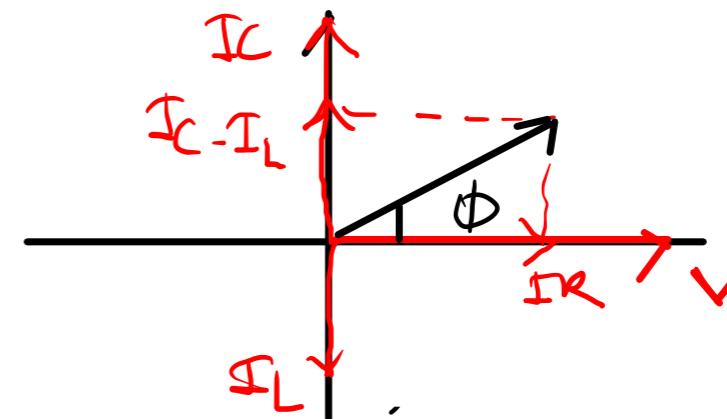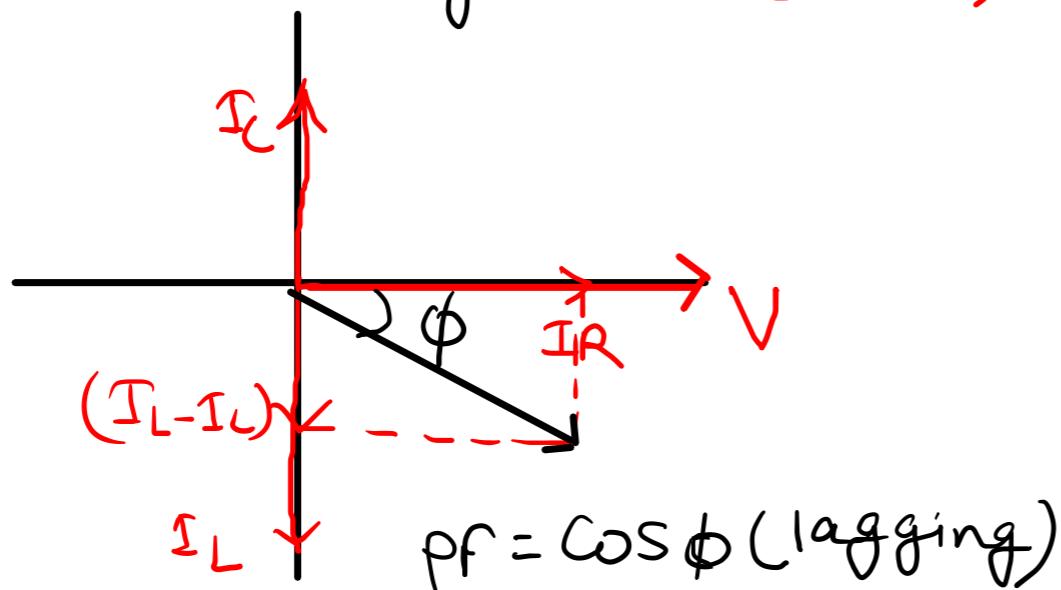

$$\text{PF} = \cos \phi$$
 (leading)

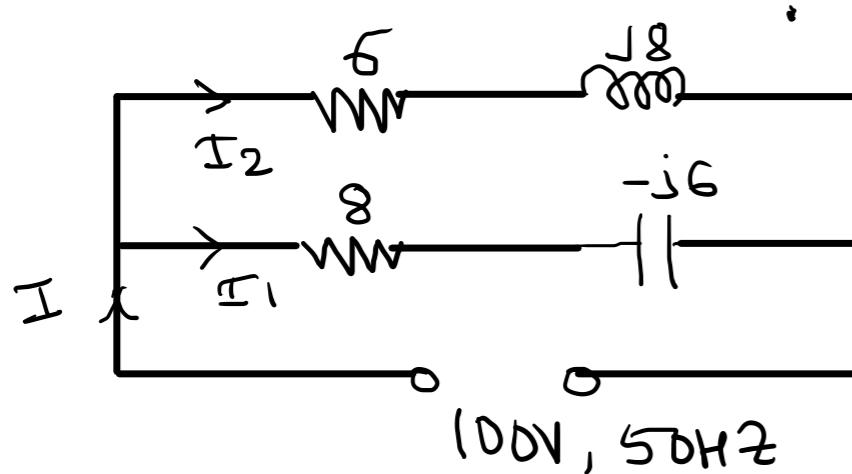1. Find current I_1 and I_2 in the following circuit. Find overall power factor of the circuit, Active power. Draw phasor diagram of the circuit.



$$\Rightarrow V = 100\angle 0^\circ$$

$$Z_1 = 8 - j6 = 10 \angle -36.86^\circ$$

$$Z_2 = 6 + j8 = 10 \angle 53.13^\circ$$

$$I_1 = \frac{V}{Z_1} = \frac{100\angle 0^\circ}{10 \angle -36.86^\circ} = 10 \angle 36.86^\circ$$

$$I_2 = \frac{V}{Z_2} = \frac{100\angle 0^\circ}{10 \angle 53.13^\circ} = 10 \angle -53.13^\circ$$

$$\underline{I} = \underline{I}_1 + \underline{I}_2$$


$$\underline{I} = 10 \angle 36.86^\circ + 10 \angle -53.13^\circ$$

$$\underline{I} = 14.14 \angle -j2 \approx 14 - j2$$

$$\boxed{\underline{I} = 14.14 \angle -8.13^\circ} \quad V = 100\angle 0^\circ$$


$$\text{PF} = \cos \phi = \cos (-8.13^\circ)$$
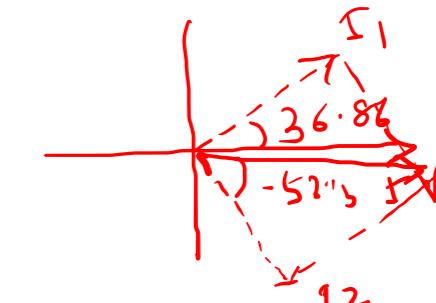
$$\boxed{\text{PF} = 0.989 \text{ (lagging)}}$$




$$P = VI \cos \phi = 100 \times 14.14 \times 0.989$$

$$P = 1398.44 \text{ Watts}$$

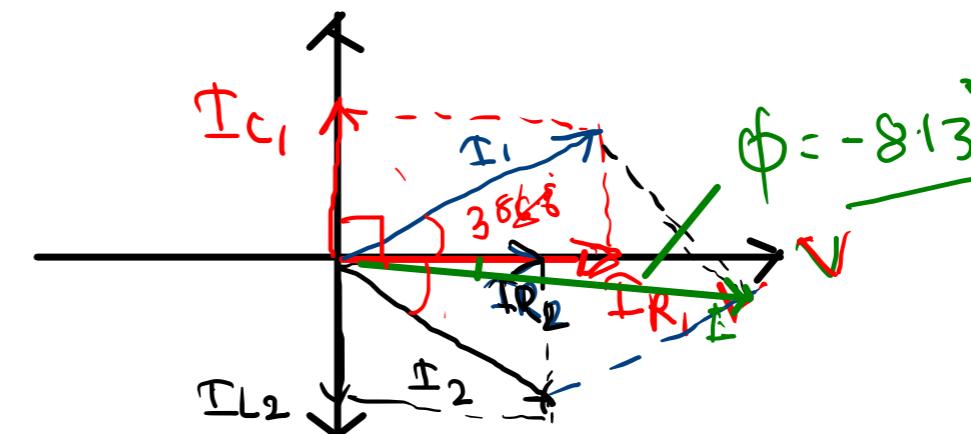

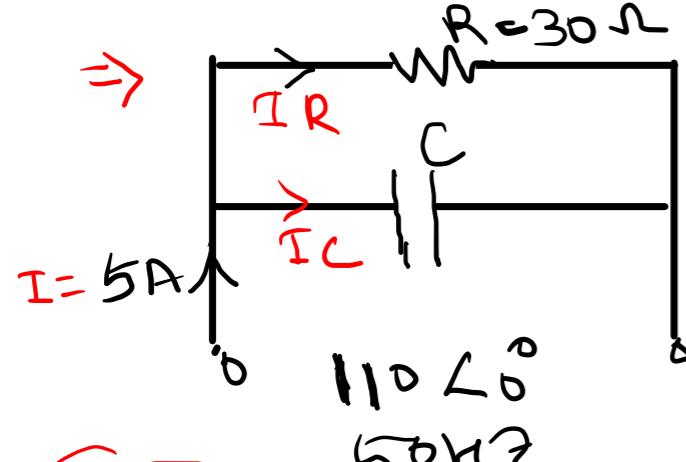2. A resistor of 30 ohm and a capacitor of unknown value are connected in parallel across a 110 V, 50Hz supply. The combination draws a current of 5A from the supply. Find the value of unknown capacitance. The combination is connected across a 110 V supply of unknown frequency, it is observed that total current drawn from the mains falls to 4 A , determine frequency of the supply.



(PQ#1)

$$\bar{I} = \bar{I}_R + \bar{I}_C$$

$$I^2 = I_R^2 + I_C^2$$

$$I = 5, \quad I_R = \frac{110}{30} = 3.67 \text{ A}$$

$$I_C^2 = I^2 - I_R^2$$

$$I_C^2 = (5)^2 - (3.67)^2$$

$$I_C = 3.39 \text{ A}$$

$$X_C = \frac{V}{I_C} = \frac{110}{3.39}$$

$$X_C = 32.45 \Omega$$

$$X_C = \frac{1}{\omega C}$$

$$C = \frac{1}{\omega X_C}$$

$$C = \frac{1}{314 \times 32.45}$$

$$C = 98.15 \mu\text{F}$$

(PQ#2) $I = 4 \text{ A}$

$$I_C^2 = (4)^2 - (3.67)^2$$

$$I_C = 1.59 \text{ A}$$


$$X_C = \frac{110}{1.59} = 69.18 \Omega$$

$$X_C = \frac{1}{\omega C}$$

$$\omega = \frac{1}{C \times X_C} = \frac{1}{98.15 \times 10^{-6} \times 69.18} = 147.27 \text{ rad}$$

$$f = \frac{\omega}{2\pi} = \frac{147.27}{2\pi} = 23.47 \text{ Hz}$$

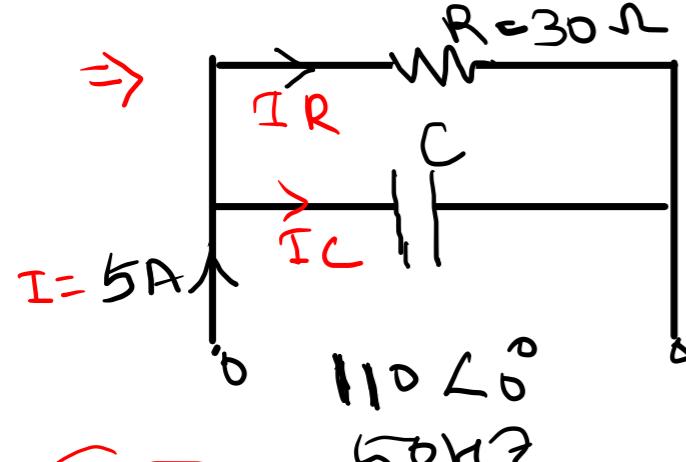2. A resistor of 30 ohm and a capacitor of unknown value are connected in parallel across a 110 V, 50Hz supply. The combination draws a current of 5A from the supply. Find the value of unknown capacitance. The combination is connected across a 110 V supply of unknown frequency, it is observed that total current drawn from the mains falls to 4 A , determine frequency of the supply.



(PQ#1)

$$\bar{I} = \bar{I}_R + \bar{I}_C$$

$$I^2 = I_R^2 + I_C^2$$

$$I = 5, \quad I_R = \frac{110}{30} = 3.67 \text{ A}$$

$$I_C^2 = I^2 - I_R^2$$

$$I_C^2 = (5)^2 - (3.67)^2$$

$$I_C = 3.39 \text{ A}$$

$$X_C = \frac{V}{I_C} = \frac{110}{3.39}$$

$$X_C = 32.45 \Omega$$

$$X_C = \frac{1}{\omega C}$$

$$C = \frac{1}{\omega X_C}$$

$$C = \frac{1}{314 \times 32.45}$$

$$C = 98.15 \mu\text{F}$$

(PQ#2) $I = 4 \text{ A}$

$$I_C^2 = (4)^2 - (3.67)^2$$

$$I_C = 1.59 \text{ A}$$


$$X_C = \frac{110}{1.59} = 69.18 \Omega$$

$$X_C = \frac{1}{\omega C}$$

$$\omega = \frac{1}{C X_C} = \frac{1}{98.15 \times 10^{-6} \times 69.18} = 147.27 \text{ rad}$$

$$f = \frac{\omega}{2\pi} = \frac{147.27}{2\pi} = 23.47 \text{ Hz}$$

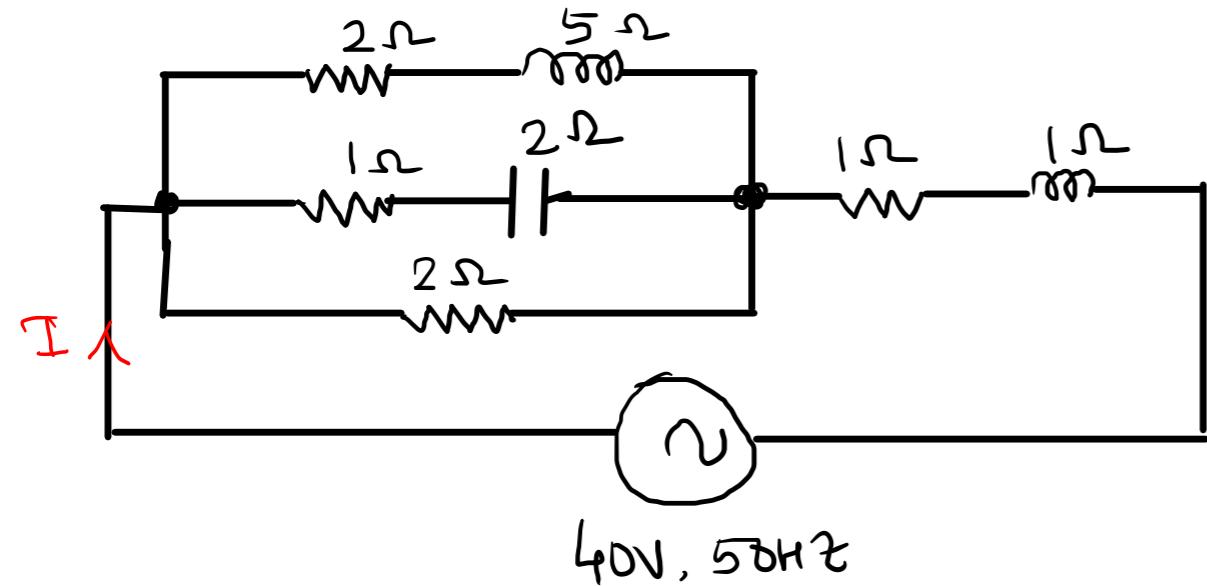3. In the following circuit, calculate i) total impedance (ii) total current (iii) power factor (iv) Active and reactive power.



$$Y_2 = \frac{1}{Z_2} = \frac{1}{1-j2} = 0.2 + j0.4$$

$$Y_3 = \frac{1}{Z_3} = \frac{1}{2} = 0.5$$

$$Y_p = Y_1 + Y_2 + Y_3 = 0.768 + j0.228$$

$$Z_p = \frac{1}{Y_p} = \frac{1}{0.768 + j0.228}$$

$$Z_p = 1.196 - j0.355$$

$$Z_T = Z_p + Z_4 = 2.196 + j0.645$$

$$Z_T = 2.28 \angle 16.36^\circ$$

$$I = \frac{V}{Z_T} = \frac{40 \angle 0}{2.28 \angle 16.36} = 17.54 \angle -16.36^\circ$$

$$PF = \cos \phi = \cos(16.36) = 0.95 \text{ (lagging)}$$

$$P = VI \cos \phi$$

$$Q = VI \sin \phi$$

$$P = 40 \times 17.54 \times 0.95 \\ P = 666.62 \text{ Watts}$$

$$Q = 40 \times 17.54 \sin(16.36^\circ) \\ Q = 197.62 \text{ VAR}$$

$$\Rightarrow Z_1 = 2 + j5$$


$$\underline{Z_4 = 1 + j1}$$

$$Z_2 = 1 - j2$$

$$Z_3 = 2 \Omega$$

$$Y_1 = \frac{1}{Z_1} = \frac{1}{(2 + j5)} = 0.1068 - j0.172$$

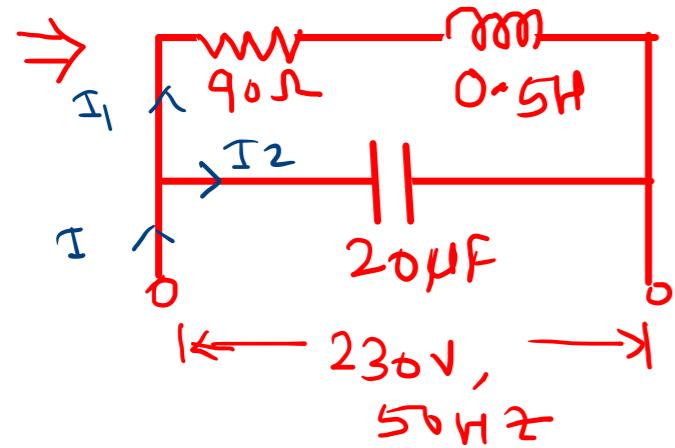4) A series combination of 0.5 H inductor and 90 ohm resistor are connected in parallel across 20 μ F. Find
 (i) the total current (ii) power factor of the circuit (iii) total power taken from the source. Draw phasor
 diagram. A voltage of 230 V, 50 Hz is maintained across the circuit.



$$Z_1 = 90 + j 314 \times 0.5$$

$$Z_1 = 90 + j 157 = 180.9 \angle 60.17^\circ$$

$$Z_2 = -j \frac{1}{314 \times 20 \times 10^{-6}}$$

$$Z_2 = -j 159.15 = 159.15 \angle -90^\circ$$

$$I_1 = \frac{V}{Z_1} = \frac{230 \angle 0^\circ}{180.9 \angle 60.17^\circ} = 1.27 \angle -60.17^\circ$$

$$I_2 = \frac{V}{Z_2} = \frac{230 \angle 0^\circ}{159.15 \angle -90^\circ} = 1.44 \angle 90^\circ$$

$$\bar{I} = \bar{I}_1 + \bar{I}_2 = 1.27 \angle -60.17^\circ + 1.44 \angle 90^\circ$$


$$\boxed{\bar{I} = 0.716 \angle 28.16^\circ}$$

$$PF = \cos \phi = \cos(28.16^\circ) = 0.88 \text{ (leading)}$$

$$\text{Power } P = V I \cos \phi = 230 \times 0.716 \times 0.88$$

$$P = 144.91 \text{ Watts.}$$


\Rightarrow Phasor diagram

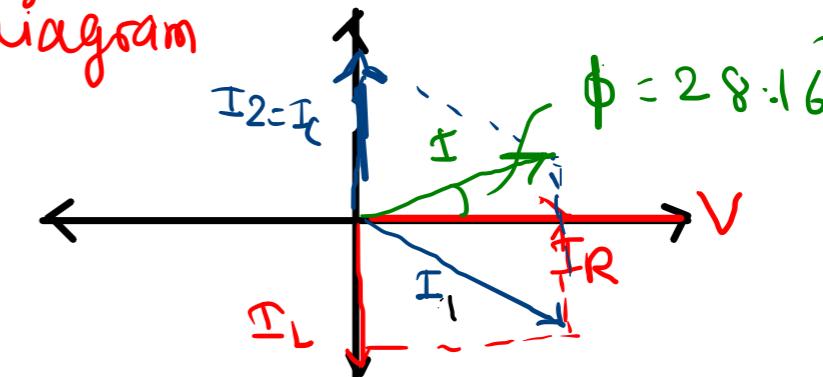

Resonance

Resonance is said to occur when the current is either maximum or minimum for a particular frequency of the AC input. At resonance circuit impedance becomes minimum or maximum. The power factor of the circuit becomes unity.

Series Resonance

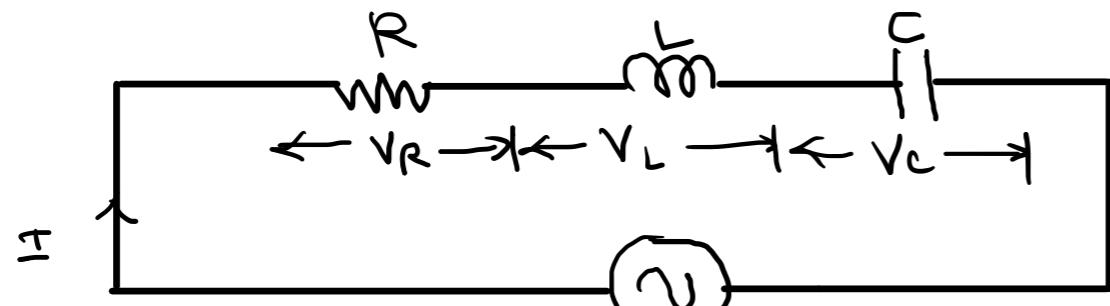

$$V = V_m \sin \omega t \quad | \quad \omega \uparrow$$

$$Z = R + j(X_L - X_C)$$

$$X_L = \omega L = 2\pi f L \quad f \uparrow X_L \uparrow$$

at $f = 0, X_L = 0$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} \quad f \uparrow X_C \downarrow$$

at $f = 0, X_C = \infty$

At resonance ($\text{PF} = 1$)

$$X_L = X_C$$

$$Z = R + j(X_L - X_C)$$

$$Z_r = R + j0 = R \quad (\text{minimum})$$

$$I_r = \frac{V}{Z} = \frac{V}{R} \quad (\text{maximum})$$

[Acceptor Circuit]

$$\rightarrow X_L = X_C \text{ at } \omega = \omega_r$$

$$\omega_r = \frac{1}{\omega_r C}$$


$$\omega_r^2 = \frac{1}{L C} \quad \text{So} \quad \boxed{\omega_r = \frac{1}{\sqrt{L C}} \text{ rad/sec}}$$

$$2\pi f_r = \frac{1}{\sqrt{L C}} \quad \text{So} \quad f_r = \frac{1}{2\pi\sqrt{L C}} \text{ Hz}$$

$f_r \rightarrow$ Resonance frequency,

⇒ Series Resonance

→ phasor diagram.

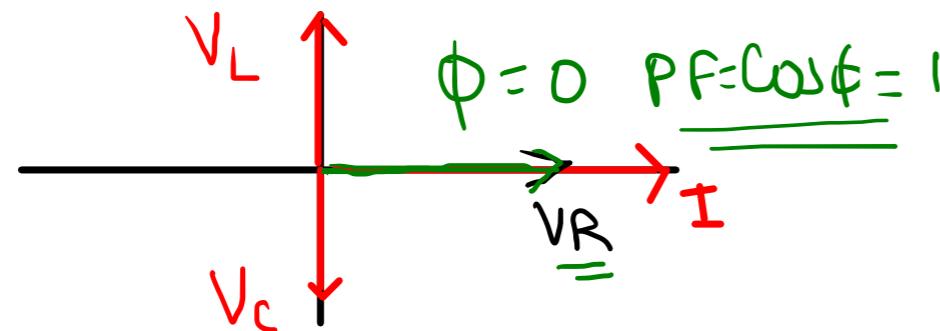

$$X_L = X_C$$

$$I_r \cdot X_L = I_r \cdot X_C$$


$$(V_L = V_C) > V$$

$$\underline{V_R = I_r \cdot R}$$

$$(V_L = V_C) > V \text{ So}$$

→ Voltage magnification circuit

⇒ Variation of R , X_L & X_C and Z

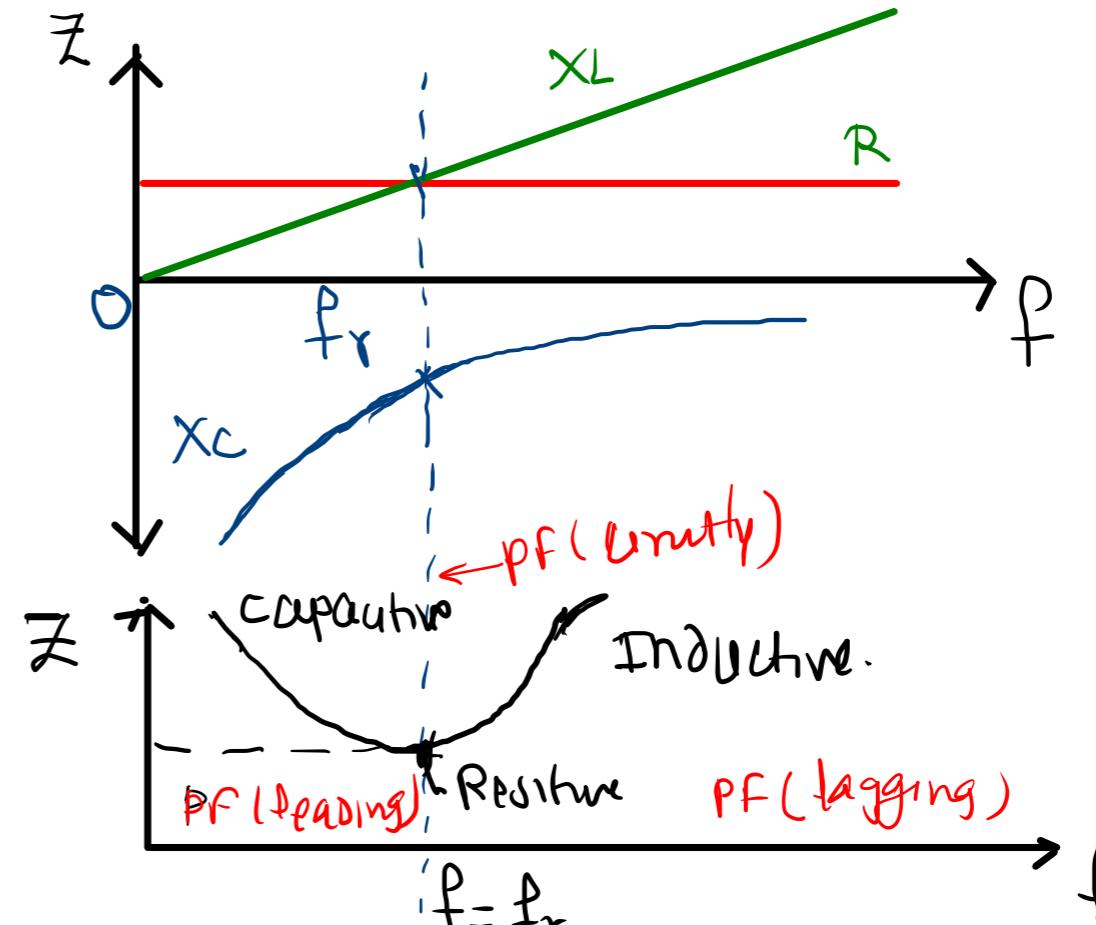


- $f < f_r \rightarrow$ impedance capacitive, pf leading
- $f = f_r \rightarrow$ impedance resistive, pf + unity
- $f > f_r \rightarrow$ impedance inductive, pf lagging

⇒ Bandwidth

$$P = I^2 R$$

At resonance $I = I_r$ (max)

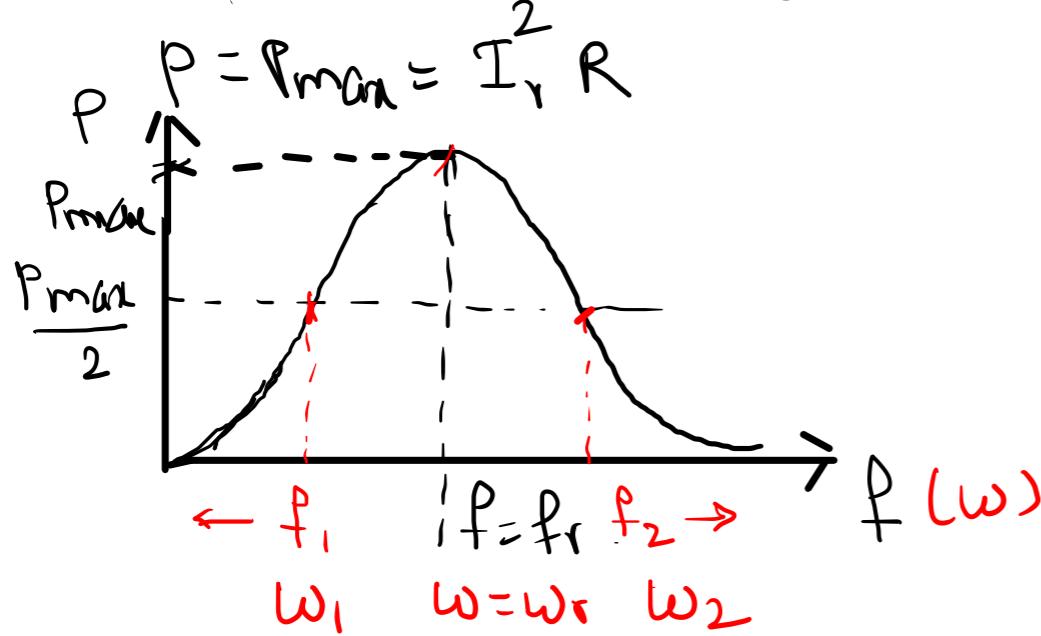

→ Half power frequencies
 (ω_1, ω_2) or (f_1, f_2)

$$\text{Bandwidth} = (f_2 - f_1) \text{ or } (\omega_2 - \omega_1)$$


$$P_{\text{max}} = I_r^2 R$$

$$P_{\text{Half}} = \frac{P_{\text{max}}}{2} = \frac{I_r^2 R}{2}$$

Let at $P = P_{\text{Half}}$, $I = I_H$

$$I_H^2 R = \frac{I_r^2 R}{2}$$
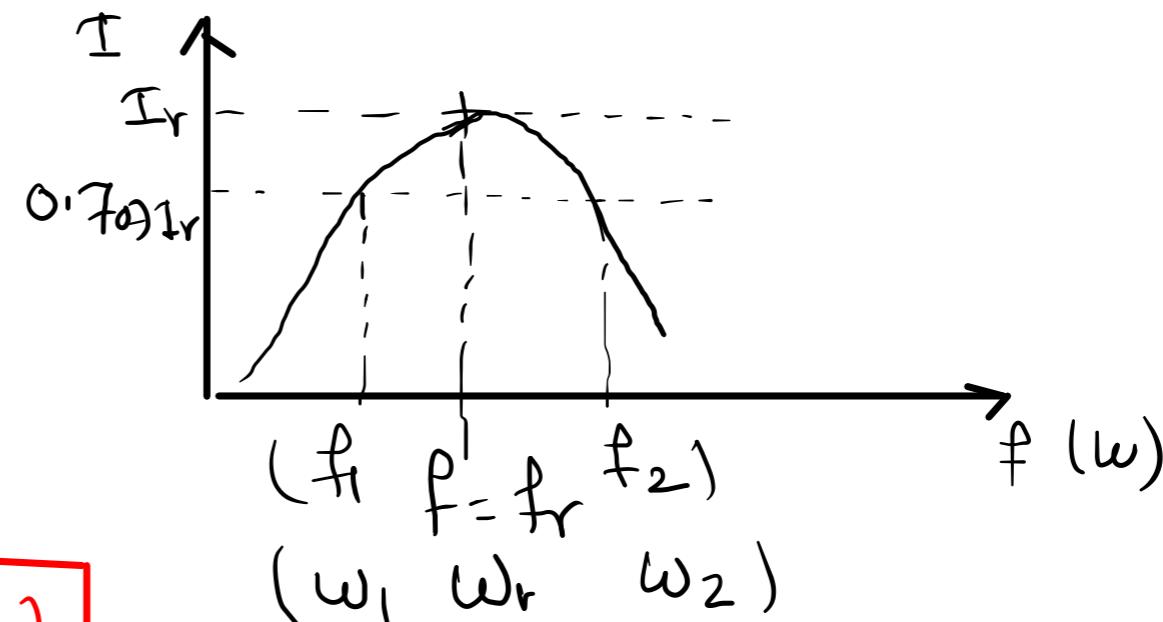
$$I_H = \frac{I_r}{\sqrt{2}} = 0.707 I_r$$



\Rightarrow Bandwidth

At any freqn $I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}} \quad \text{--- } ①$

$$= \frac{V}{\sqrt{R^2 + (\omega_L - \frac{1}{\omega_C})^2}}$$

At half power $I = \frac{I_r}{\sqrt{2}} = \frac{V}{R\sqrt{2}} = \frac{V}{\sqrt{2} \cdot R} \quad \text{--- } ②$

put ② in eqn ①

$$\frac{\sqrt{V}}{\sqrt{2}R} = \frac{\sqrt{V}}{\sqrt{R^2 + (\omega_L - \frac{1}{\omega_C})^2}}$$

$$\sqrt{2}R = \sqrt{R^2 + (\omega_L - \frac{1}{\omega_C})^2}$$

Squaring both sides

$$2R^2 = R^2 + (\omega_L - \frac{1}{\omega_C})^2$$

$$(\omega_L - \frac{1}{\omega_C})^2 = R^2$$

$$(\omega_L - \frac{1}{\omega_C}) = \pm R$$

$$\frac{(\omega^2 L C - 1)}{\omega_C} = R$$

$$\omega^2 L C - 1 = \pm \omega_C R$$

$$\omega^2 L C - 1 \pm \omega_C R = 0$$

$$LC \left[\omega^2 \pm \frac{R}{L} \omega - \frac{1}{LC} \right] = 0$$

$$\omega^2 \pm \frac{R}{L} \omega - \frac{1}{LC} = 0$$

Solving

$$ax^2 + bx + c \text{ roots } \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

Finding roots.

$$\omega = \frac{-\frac{R}{L} \pm \sqrt{\frac{R^2}{L^2} + \frac{4}{LC}}}{2} = \pm \frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$

→ Bandwidth

$$\omega = \pm \frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$

For low values of R

$$\frac{R^2}{4L^2} \ll \frac{1}{LC}$$

$$\omega = \pm \frac{R}{2L} \pm \sqrt{\frac{1}{LC}}$$

$$\omega = \pm \frac{R}{2L} \pm \frac{1}{\sqrt{LC}}$$

$$\omega = \pm \frac{R}{2L} \pm \omega_r$$

Considering ω_r as positive

$$\boxed{\omega_1 = \omega_r - \frac{R}{2L}} \text{ or } f_1 = f_r - \frac{R}{4\pi L}$$

$$\boxed{\omega_2 = \omega_r + \frac{R}{2L}}$$

$$f_2 = f_r + \frac{(R)}{4\pi L}$$

$$BW = \omega_2 - \omega_1$$

$$= \omega_r + \frac{R}{2L} - \omega_r + \frac{R}{2L}$$

$$BW = \frac{2R}{2L} = \frac{R}{L} \text{ rad/sec}$$

Bandwidth in Hz

$$\begin{aligned} BW &= f_2 - f_1 = \frac{\omega_2}{2\pi} - \frac{\omega_1}{2\pi} \\ &= \frac{1}{2\pi} (\omega_2 - \omega_1) \end{aligned}$$

$$\boxed{BW = \frac{R}{2\pi L} \text{ Hz}}$$

\Rightarrow Quality Factor (Q)

$$Q = \frac{\text{potential drop across } L \text{ at resonance}}{\text{potential drop across } R \text{ at resonance}}$$

$$Q = \frac{x_L \times I_r}{R \times I_r} = \frac{\omega_r L}{R} = \frac{1}{\sqrt{LC}} \times \frac{L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

OR

$$Q = \frac{\text{potential drop across } C \text{ at resonance}}{\text{potential drop across } R \text{ at resonance}}$$

$$Q = \frac{x_C \cdot I_r}{R \cdot I_r} = \frac{1}{\omega_r C \cdot R} = \frac{\sqrt{LC}}{RC} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$Q = \frac{\omega_r \cdot L}{R} \quad \text{--- (1)}$$

$$BW = \frac{R}{L} \quad \text{--- (2)}$$


$$BW = \frac{R}{L} \text{ rad/sec}$$

Comparing (1) & (2)

$$Q = \frac{\omega_r}{BW(\text{rad/sec})} = \frac{2\pi f_r}{2\pi BW \text{ Hz}}$$

$$Q = \frac{f_r}{BW(\text{Hz})}$$
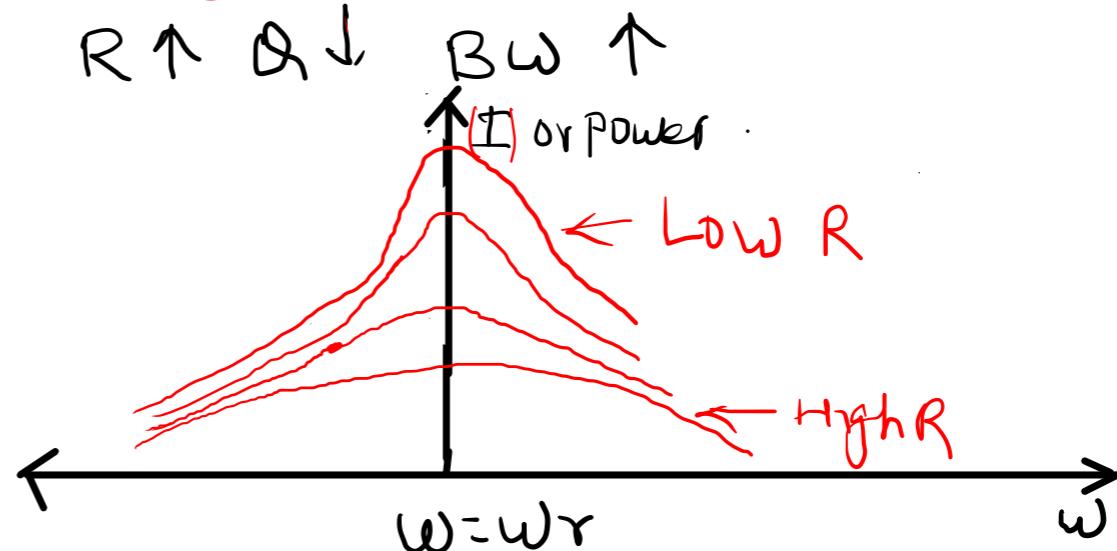
$$BW = \frac{f_r}{Q} \quad \text{--- (3)}$$



→ Frequency at which V_L & V_C are maximum :-

$$V_C = I \times C \quad \text{or} \quad V_L = I \times X_L \quad Z = R + j(X_L - X_C)$$

$$V_C = I \times C = \frac{V}{Z} \times C = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}} \times X_C = \frac{V}{\sqrt{R^2 + (\omega_L - \frac{1}{\omega_C})^2}} \times \frac{1}{\omega_C}$$

Squaring both sides

$$V_C^2 = \frac{V^2}{R^2 + (\omega_L - \frac{1}{\omega_C})^2 (\omega_C)^2} = \frac{V^2}{\omega_C^2 R^2 + [\omega_{LC-1}^2]^2 \cdot \frac{1}{\omega_C^2}}$$

$$\left| \begin{array}{l} V_C^2 = \frac{V^2}{\omega_C^2 R^2 + (\omega_{LC-1}^2)^2} \\ \frac{dV_C^2}{d\omega} = 0 \\ 0 = \frac{(\omega_C^2 R^2 + (\omega_{LC-1}^2)^2) \times 0 - V^2 (2 \omega_C^2 R^2 \omega + 2 (\omega_{LC-1}^2)^2 \omega)}{[(\omega_C^2 R^2 + (\omega_{LC-1}^2)^2)]^2} \\ 2 \omega_C^2 R^2 + 2 (\omega_{LC-1}^2) 2 \omega_C \omega = 0 \\ C \neq 0, \omega \neq 0 \end{array} \right.$$

$$\frac{dV_C^2}{d\omega} = 0$$

$$2\omega C(CR^2 + 2\omega^2 L^2 - \omega^2) = 0$$

$$2L^2 C \omega^2 = 2L - CR^2$$

$$\omega^2 = \frac{2L}{2L^2 C} - \frac{CR^2}{2L^2 C}$$

$$\omega^2 = \frac{1}{LC} - \frac{R^2}{2L^2}$$

$$\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}}$$

$$\frac{1}{LC} \gg \frac{R^2}{2L^2}$$

$$\boxed{\omega = \frac{1}{\sqrt{LC}}}$$

$$2\omega C(CR^2 + 2\omega^2 L^2 - \omega^2) = 0$$

$$2L^2 C \omega^2 = 2L - CR^2$$

$$\omega^2 = \frac{2L}{2L^2 C} - \frac{CR^2}{2L^2 C}$$

$$\omega^2 = \frac{1}{LC} - \frac{R^2}{2L^2}$$

$$\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}}$$

$$\frac{1}{LC} \gg \frac{R^2}{2L^2}$$

$$\boxed{\omega = \frac{1}{\sqrt{LC}}}$$

$$2\omega C(CR^2 + 2\omega^2 L^2 - \omega^2) = 0$$

$$2L^2 C \omega^2 = 2L - CR^2$$

$$\omega^2 = \frac{2L}{2L^2 C} - \frac{CR^2}{2L^2 C}$$

$$\omega^2 = \frac{1}{LC} - \frac{R^2}{2L^2}$$

$$\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}}$$

$$\frac{1}{LC} \gg \frac{R^2}{2L^2}$$

$$\boxed{\omega = \frac{1}{\sqrt{LC}}}$$

$$2\omega C(CR^2 + 2\omega^2 L^2 - \omega^2) = 0$$

$$2L^2 C \omega^2 = 2L - CR^2$$

$$\omega^2 = \frac{2L}{2L^2 C} - \frac{CR^2}{2L^2 C}$$


$$\omega^2 = \frac{1}{LC} - \frac{R^2}{2L^2}$$

$$\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}}$$

$$\frac{1}{LC} \gg \frac{R^2}{2L^2}$$

$$\boxed{\omega = \frac{1}{\sqrt{LC}}}$$

→ Parallel Resonance

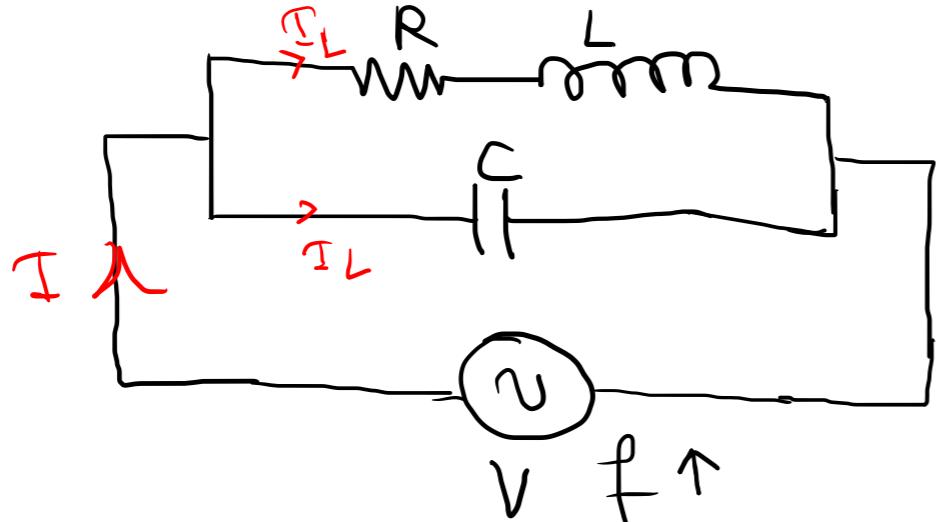

$$Z_1 = R + jX_L$$

$$Z_2 = -jX_C$$

$$Y_1 = \frac{1}{Z_1} = \frac{1}{R + jX_C} \times \frac{R - jX_L}{R - jX_L}$$

$$Y_1 = \frac{R - jX_L}{R^2 + X_L^2}$$

$$Y_2 = Z_2 = \frac{1}{-jX_C} = j \frac{1}{X_C}$$

$$Y = Y_1 + Y_2 = \frac{R - jX_L}{R^2 + X_L^2} + j \frac{1}{X_C}$$

$$Y = \frac{R}{R^2 + X_L^2} - j \left[\frac{X_L}{R^2 + X_L^2} - \frac{1}{X_C} \right] \quad \text{--- (A)}$$

At resonance the circuit is purely resistive
so the reactive term must be zero.

$$\frac{X_L}{R^2 + X_L^2} - \frac{1}{X_C} = 0$$

$$\frac{X_L}{R^2 + X_L^2} = \frac{1}{X_C}$$

$$X_L X_C = R^2 + X_L^2 \quad \text{--- (1)}$$

$$\omega_r \cdot \frac{1}{\omega_r} = R^2 + \omega_r^2 L^2$$

$$\frac{L}{C} = R^2 + \omega_r^2 L^2$$

$$\omega_r^2 L^2 = \frac{L}{C} - R^2$$


$$\omega_r^2 = \frac{L}{C \cdot L^2} - \frac{R^2}{L^2}$$

$$\omega_r^2 = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$\omega_r = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$\frac{1}{L_C} > \frac{R^2}{L^2} \quad \text{so } L_C = \frac{1}{\sqrt{L_C}}$$

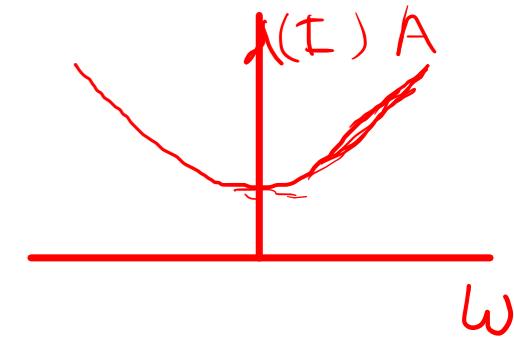If Y is minimum so $Z = \frac{1}{Y}$ will be maximum
if Z is maximum so current I will be minimum.



Impedance at Resonance for parallel Resonance circuit

⇒ At Resonance the real part of admittance (from eqn A)

$$\frac{R}{\underline{R^2 + X_L^2}}$$

So impedance $Z_r = \frac{R^2 + X_L^2}{R} = \frac{1}{Y_{real}}$
At resonance

↑ from eqn ① $Z_r = \frac{X_L X_C}{R}$

$$Z_r = \frac{\cancel{\omega_r} L \times \frac{1}{\cancel{\omega_r} C}}{R}$$

$Z_r = \frac{L}{CR}$ dynamic impedance

→ Comparison of series and parallel R-L-C Resonant Circuits

parameter	series RLC circuit	parallel RLC circuit
Current	$I = \frac{V}{R}$ (maximum)	$I = \frac{V}{Z_0}$ (minimum)
Impedance	$Z = R$	$Z = L/C R$
Power factor	Unity (1)	Unity (1)
Resonant frequency	$f_r = \frac{1}{2\pi\sqrt{LC}}$	$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{Z_L^2}}$
Quality factor	$Q = \frac{\omega_r L}{R} = \frac{2\pi f_r L}{R}$	$Q = \frac{2\pi f_r L}{R}$
Magnification	Voltage (V_L, V_C)	Current (I_L, I_C)

Acceptor circuit

Rejector circuit

Example:1 : A 5 uF capacitor is connected in series with the coil having an inductance of 50 mH. Calculate the frequency of resonance and resistance of the coil if a 60V source operating at resonance causes current of 1.5 A . What is power factor of the coil.



Resonant Frequency

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$f_r = \frac{1}{2\pi\sqrt{50 \times 10^{-3} \times 5 \times 10^{-6}}}$$

$$f_r = 318.3 \text{ Hz}$$

$$f_r \approx 318 \text{ Hz}$$

Impedance at resonance

$$Z = \frac{60}{1.5} = 40 \Omega$$

$$Z^2 = R^2 + (X_L - X_C)^2$$

But at resonance

$$Z = R = 40 \Omega$$


$$\text{So } R = 40 \Omega$$

$$\text{Quality factor } Q = \frac{X_L}{R} = \frac{2\pi f_r L}{R}$$

$$Q = \frac{2\pi \times 318 \times 50 \times 10^{-3}}{40}$$

$$Q = 2.5$$

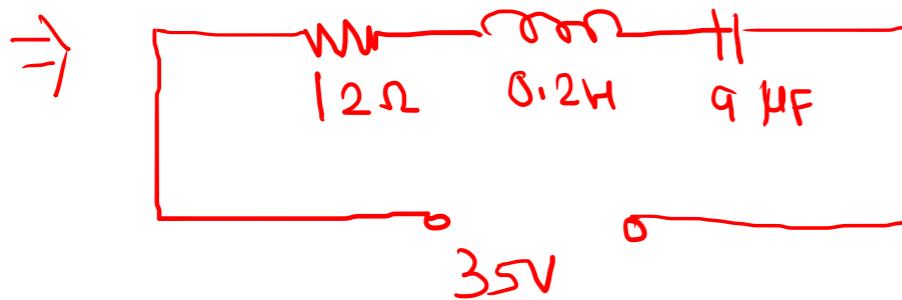Ex:2 : An non-inductive resistance of 12 ohms, an inductance of 0.2 H and capacitor of 9 uF are connected in series calculate (i) resonance frequency (ii) current at resonance (iii) voltage across each component , when a voltage of 35 V at resonance frequency is applied to the whole circuit.



$$\text{i)} f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{0.2 \times 9 \times 10^{-6}}}$$

$$f_r = 118.6 \approx 119 \text{ Hz}$$

ii) Current at resonance (I_r)

$Z = R$ at resonance

$$Z = R = 12 \therefore I_r = \frac{35}{12} = 2.9 \text{ A}$$

iii) Voltage across each Component

$$V_R = I_r \times R = 2.9 \times 12 = 34.8 \text{ V}$$


$$V_L = I_r \times X_L = 2.9 \times (2\pi \times 0.2 \times 10^6)$$

$$V_L = 433.65 \text{ V}$$

$$V_C = I_r \times X_C = 2.9 \times \frac{1}{2\pi \times 119 \times 9 \times 10^{-6}}$$

$$V_C = 432.35 \text{ V}$$

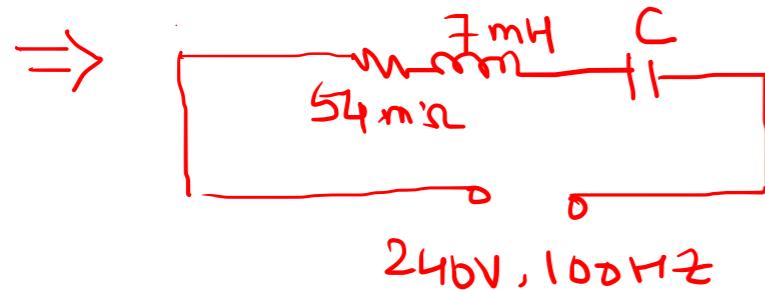Ex-3: A series R-L-C circuit consisting of capacitor and a coil connected across 240 V, 100 Hz AC supply. If the coil has 54 milli-ohm resistance and 7 mH inductance. Calculate (i) value of the capacitor at 100 Hz resonance frequency (ii) quality factor of the coil (III) Half power frequencies



$$\text{i)} \quad f_r = 100 \text{ Hz}$$

$$f_r = \frac{1}{2\pi \sqrt{LC}}$$

$$f_r^2 = \frac{1}{4\pi^2 LC}$$

$$C = \frac{1}{4\pi^2 f_r^2 L}$$

$$C = \frac{1}{4\pi^2 \times (100)^2 \times (7 \times 10^{-3})}$$

$$C = 3.62 \times 10^{-4} \approx 362 \mu\text{F}$$

$$\text{ii)} Q = \frac{\omega_r L}{R} = \frac{2\pi \times 100 \times 7 \times 10^{-3}}{54 \times 10^{-3}}$$

$$Q = 81.45$$


iii) Half power Frequencies

$$f_1 = f_r - \frac{R}{4\pi L} = 100 - \frac{54 \times 10^{-3}}{4\pi \times 7 \times 10^{-3}} = 99.38 \text{ Hz}$$

$$f_2 = f_r + \frac{R}{4\pi L} = 100 + \frac{54 \times 10^{-3}}{4\pi \times 7 \times 10^{-3}} = 100.61 \text{ Hz}$$

$$\Delta\omega = f_2 - f_1 = 100.61 - 99.38 = 1.23 \text{ Hz}$$

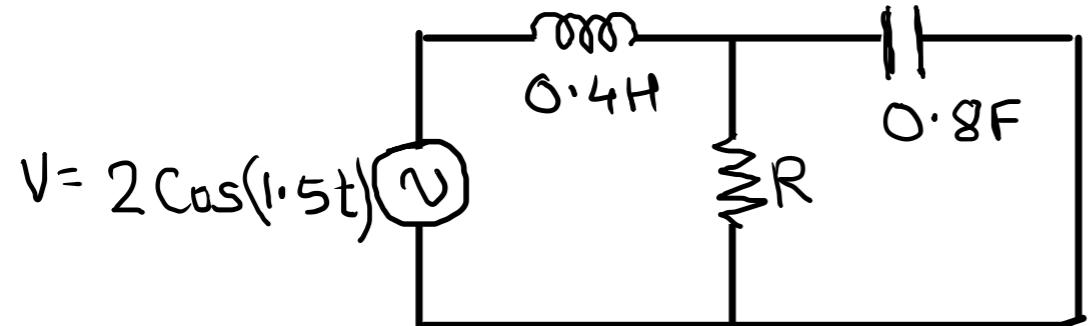Ex-4: Find value of R such that circuit below is at resonance.



Impedance of the circuit
 \Rightarrow

$$Z = X_L + \frac{R \times C}{R + X_C}$$

$$Z = j\omega(0.4) + \frac{R \times \frac{1}{j\omega(0.8)}}{R + \frac{1}{j\omega(0.8)}}$$

$$\text{given } \omega = 1.5$$

$$Z = j(1.5 \times 0.4) + \frac{R \times \frac{1}{j1.5 \times 0.8}}{R + \frac{1}{j1.5 \times 0.8}}$$

$$Z = j0.6 + \frac{R}{j1.5 \times 0.8 + 1}$$

$$Z = j0.6 + \frac{R}{j + j1.2R}$$

$$Z = j0.6 + \frac{R(1 - j1.2R)}{1 + (1.2R)^2}$$

$$Z = \frac{R}{1 + (1.2R)^2} + j \left[0.6 - \frac{1.2R^2}{1 + 1.44R^2} \right]$$

At resonance Reactive terms \rightarrow zero.

At resonance

$$0.6 - \frac{1.2R^2}{1+1.44R^2} = 0$$

$$\frac{0.6 + 0.86R^2 - 1.2R^2}{1+1.44R^2} = 0$$

$$0.6 - 0.34R^2 = 0$$


$$0.34R^2 = 0.6$$

$$R^2 = \frac{0.6}{0.34} =$$

$$\boxed{R = 1.33 \Omega}$$

Q5. Find i) Value of capacitor (ii) quality factor (iii) Impedance at resonance (iv) Total current , in the network below is at resonance.

\Rightarrow

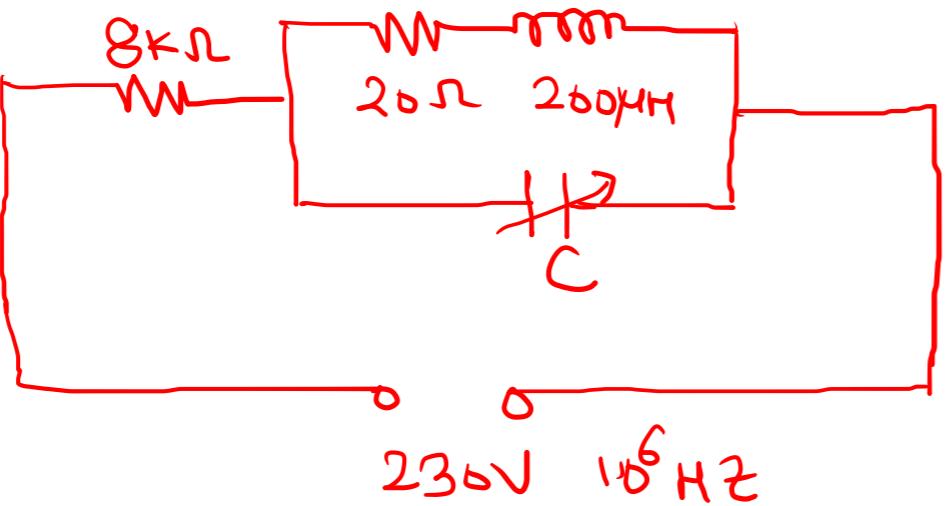

$$\text{i) } \Rightarrow f_r = 10^6 \text{ Hz}$$

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}}$$

$$10^6 = \frac{1}{2\pi} \sqrt{\frac{1}{200 \times 10^{-6} C} - \frac{(20)^2}{2(200 \times 10^{-6})^2}}$$

$$(10^6)^2 = \frac{1}{4\pi^2} \left[\frac{1}{200 \times 10^{-6} C} - \frac{20^2}{2(200 \times 10^{-6})^2} \right]$$

$$C \approx 126.5 \text{ pF}$$

$$\text{ii) } Q = \frac{2\pi f L}{R} = \frac{2\pi \times 10^6 \times 200 \times 10^{-6}}{20}$$

iii) Impedance at resonance

$$\text{dynamic impedance} = Z_D = \frac{L}{CR}$$

$$Z_D = \frac{200 \times 10^{-6}}{127 \times 10^{-2} \times 20}$$

$$Z_D = 78740 \Omega$$

$$Z_T = 8000 + 78740 = 86740 \Omega$$

iv) Total Current

$$I_T = \frac{230}{86740} = 2.65 \text{ mA}$$