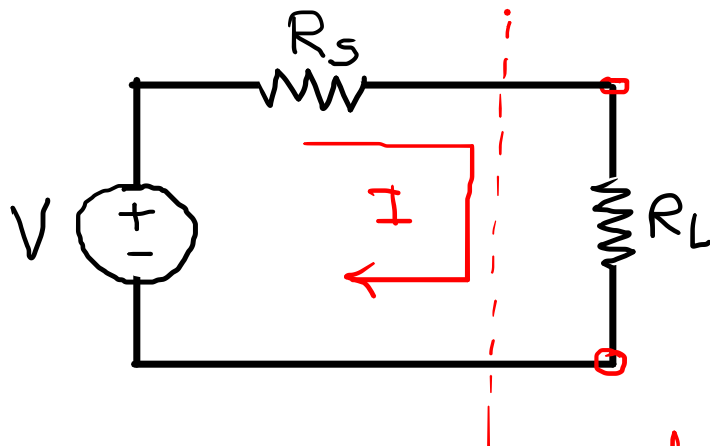


Maximum Power transfer Theorem

Statement:

The maximum power is delivered from a source to a load when load resistance is equal to source resistance.



$$I = \frac{V}{R_S + R_L} \quad \text{--- (1)}$$

$$\underline{R_L = R_S}$$

Power delivered to load

$$P_L = I^2 R_L = \frac{V^2 \times R_L}{(R_S + R_L)^2}$$

to determine value of R_L for which maximum power is delivered

$$\frac{dP_L}{dR_L} = 0 \quad \checkmark$$

$$\frac{dP_L}{dR_L} = \frac{d}{dR_L} \left(\frac{V^2 R_L}{(R_S + R_L)^2} \right) = \frac{V^2 (R_S + R_L)^2 - V^2 \cdot R_L \cdot 2(R_S + R_L)}{(R_S + R_L)^4} = 0$$

$$(R_S + R_L)^2 - 2R_L(R_S + R_L) = 0$$

$$R_S^2 + R_L^2 + 2R_L R_S - 2R_L R_S - 2R_L^2 = 0$$


$$R_S^2 - R_L^2 = 0$$

$R_S = R_L$ is condition
for maximum power transfer

Maximum Power transfer Theorem

Statement:

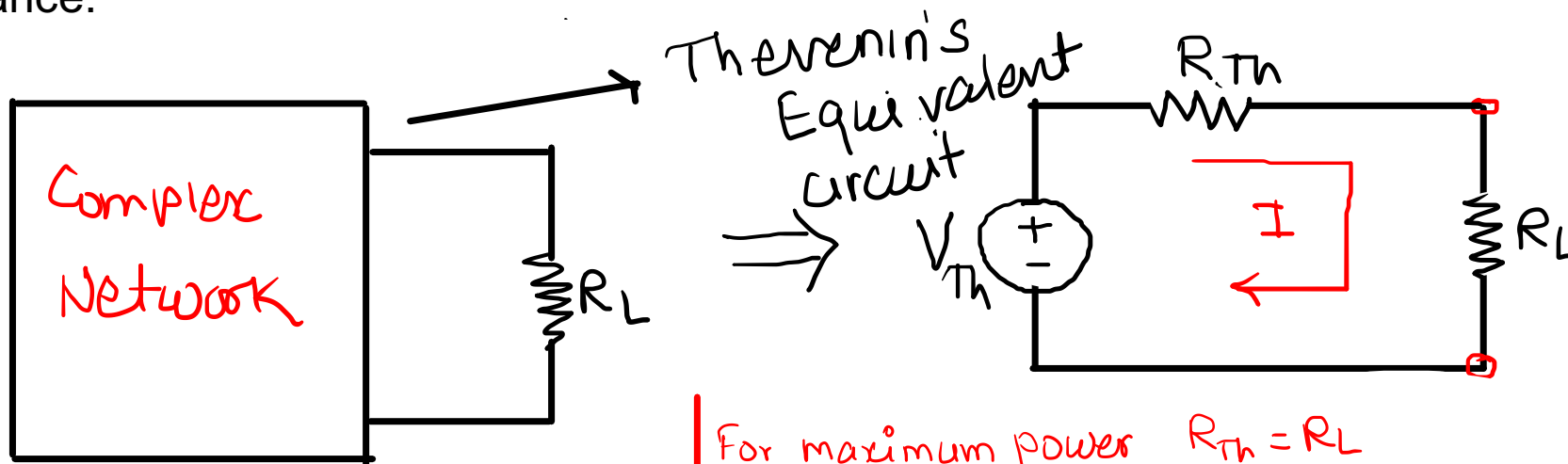The maximum power is delivered from a source to a load when load resistance is equal to source resistance.



Steps:


1. Remove Load ✓
2. Find Open circuit Voltage V_{th} ✓
3. Find R_{th} ✓
4. Find R_L for Maximum power transfer ($R_L = R_{th}$) ✓
5. Find Maximum Power

$$P_{max} = \frac{(V_{th})^2}{4R_{th}} \checkmark$$


For maximum power $R_{Th} = R_L$

$$P_L = \frac{(V_{th})^2}{(R_L + R_{th})^2} \times R_L \quad \text{OR} \quad P_{max} = \frac{(V_{th})^2}{(R_{th} + R_{th})^2} \times R_{th}$$
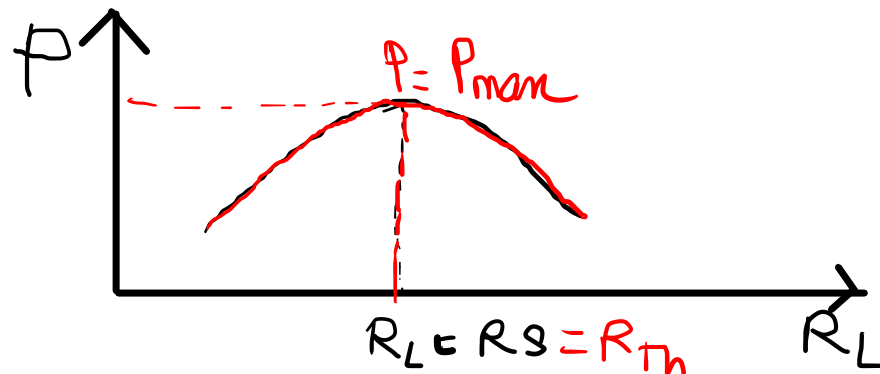
$$P_{max} = \frac{V_{th}^2}{4R_{th}^2} \times R_{th} \quad \therefore P_{max} = \frac{(V_{th})^2}{4R_{th}}$$



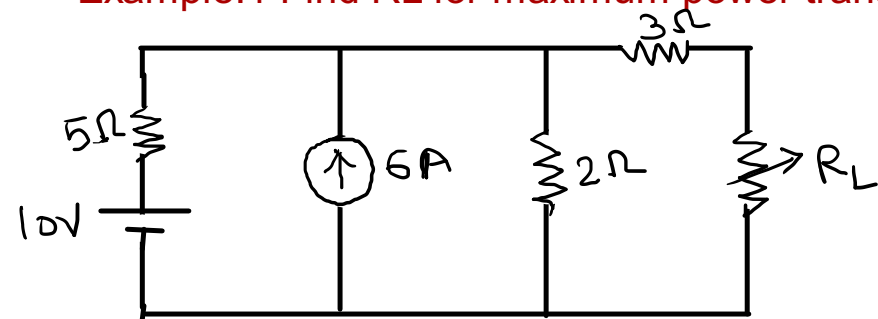Example:1 Find R_L for maximum power transfer. Also find maximum power



$$\frac{2V - 20 + 5V}{10} = 6$$

$$7V = 60 + 20$$

$$V = \frac{80}{7}$$

$$V_{th} = V_{2\Omega} = V = 11.43V$$



② Find R_{th} .

$$V_{th} = 11.43V$$

$$R_{th} = 4.43\Omega$$

$$P = \underline{7.33W}$$

① Remove load R_L & find V_{th}

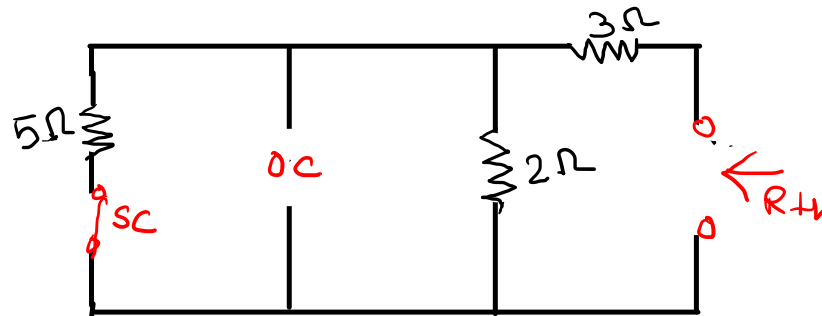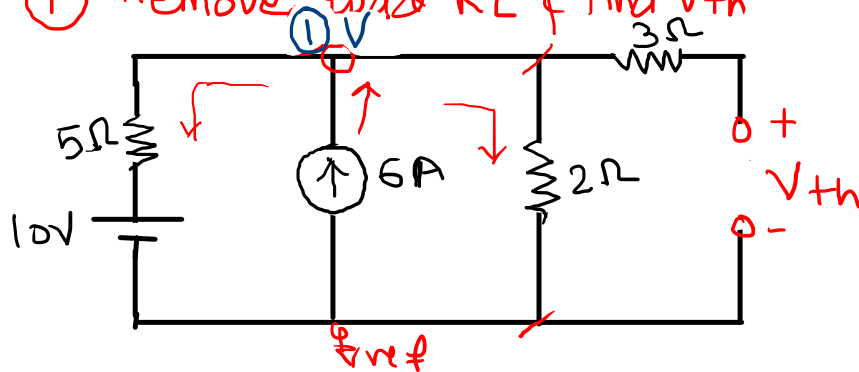

Here $V_{th} = V_{2\Omega}$

using Nodal Analysis so KCL at node


$$\frac{V-10}{5} + \frac{V}{2} = 6$$

$$R_{th} = (5 \parallel 2) + 3 = 4.43\Omega$$

$$R_L = R_{th} = 4.43\Omega$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{(11.43)^2}{4 \times 4.43} = 7.37 \text{ watt} \pm s.$$

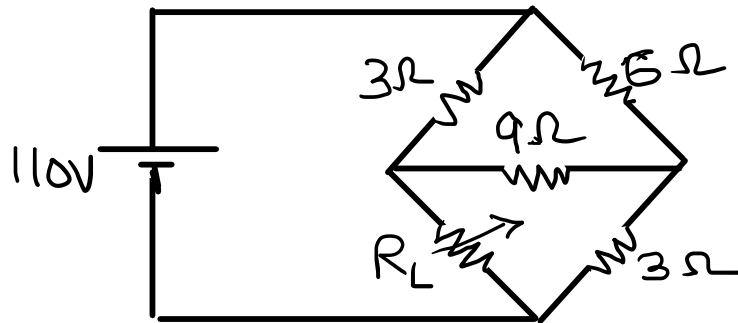Example:2 Find RL for maximum power transfer. Also find maximum power



Using mesh Analysis

KVL to mesh (I)

$$110 - 3(I_1 - I_2) - 9(I_1 - I_2) - 3I_1 = 0$$

$$15I_1 - 12I_2 = 110 \quad \text{--- (1)}$$

KVL to mesh (II)

$$-3(I_2 - I_1) - 6I_2 - 9(I_2 - I_1) = 0$$

$$12I_1 - 18I_2 = 0 \quad \text{--- (2)}$$

Solving (1) & (2)

$$I_1 = 15.71 \text{ A}, I_2 = 10.48 \text{ A}$$

$$V_{9\Omega} = 9(I_1 - I_2) = 9(15.71 - 10.48) = 47.07 \text{ V}$$

$$V_{3\Omega} = 3(I_1) = 3 \times 15.71 = 47.13$$


$$V_{th} = 47.07 + 47.13 = 94.2 \text{ V}$$

$$R_{th} = 2.35 \Omega$$

$$V_{th} = 94.2 \text{ V}$$

$$P = 945.8 \text{ W}$$

① Remove RL & find Vth



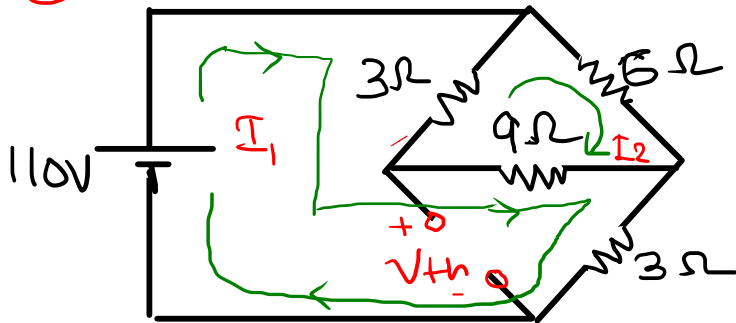


$$V_{th} - V_{9\Omega} - V_{3\Omega} = 0$$

$$V_{th} = V_{9\Omega} + V_{3\Omega}$$

Example:2 Find RL for maximum power transfer. Also find maximum power

③ To Find R_{th} .

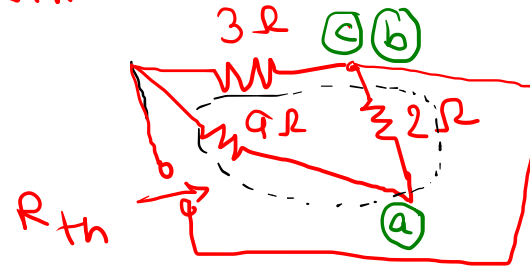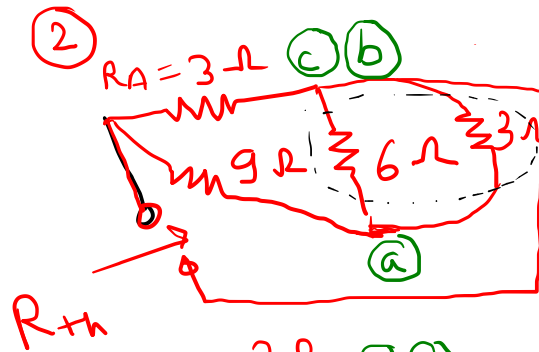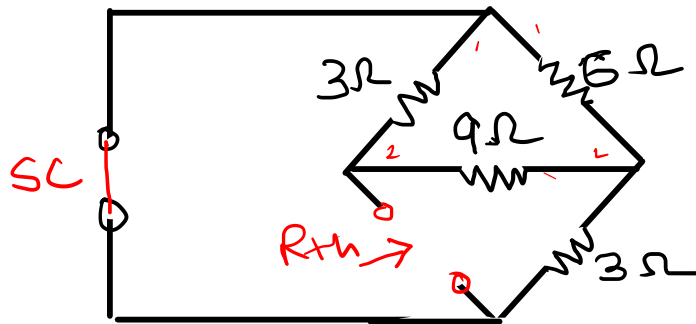

$$R_{th} = 3 \parallel 11$$

$$R_{th} = 2.36 \Omega$$

$$R_{th} = 2.36 \Omega$$

$$V_{th} = 94.29$$

$$P = 945.8W$$

$$R_L = R_{th} = 2.36 \Omega$$

$$P_{max} = \frac{V_{th}^2}{4 \cdot R_{th}} = \frac{(94.2)^2}{4 \times 2.36} = 940 \text{ Watts.}$$