

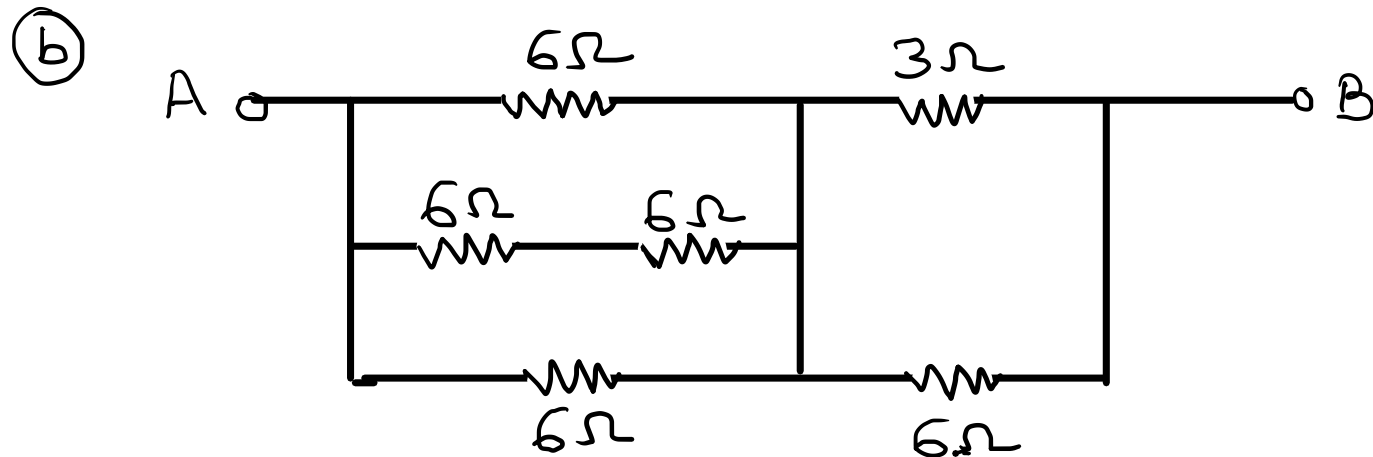


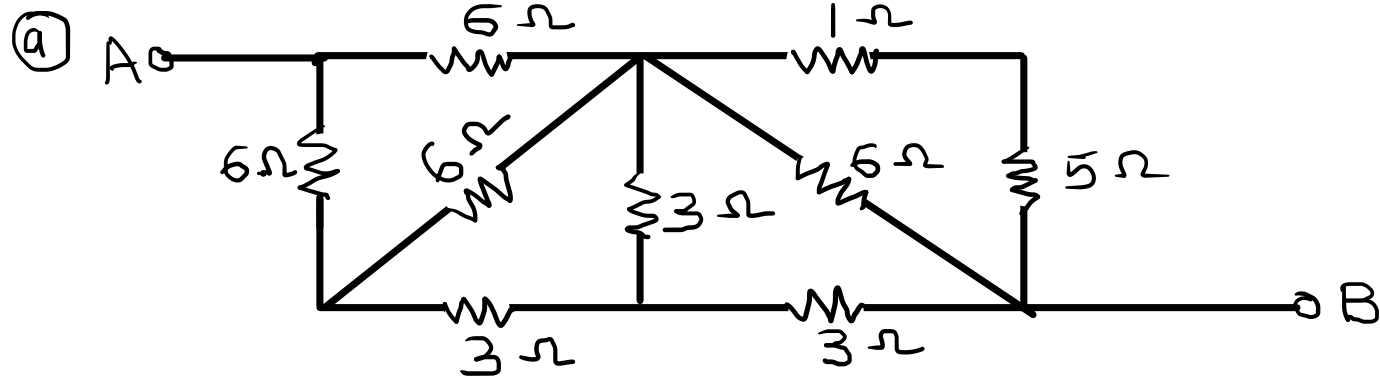Q1. Find the resistance between terminals A and B in the following networks.



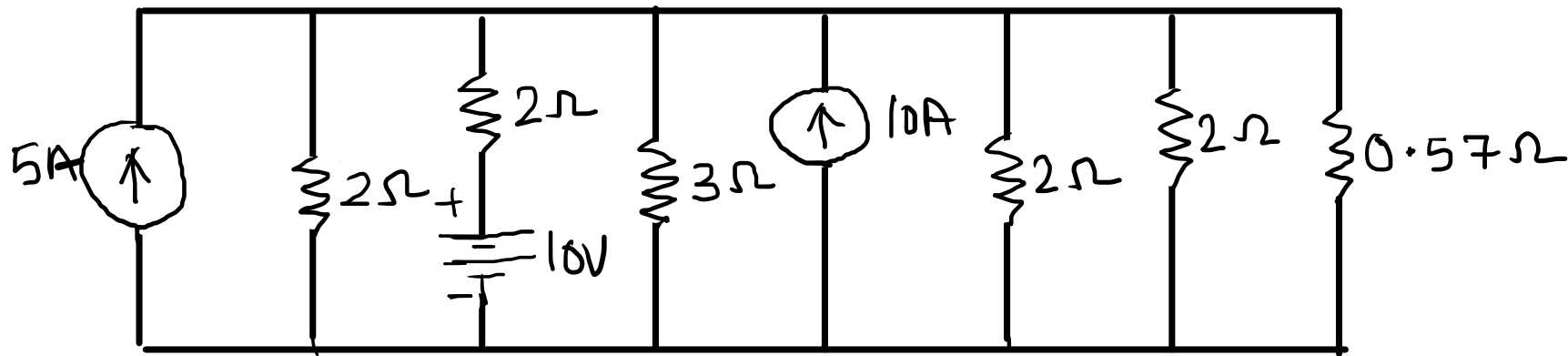Q2. Find current flowing through  $0.57\Omega$  resistor using source transformation.



Q.3 Find the Voltage between terminals A and B and terminals C and D.

